

## ***LECTURE 3. POWER AMPLIFIER DESIGN FUNDAMENTALS***

***3.1. Main characteristics (two-port networks, gain, delivered power )***

***3.2. Gain and stability***

***3.3. Stabilization circuit technique***

***3.4. Class-A,-B,-C operation modes***

***3.5. Linearity***


***3.6. DC biasing***

***3.7. Push-pull amplifiers***

***3.8. Practical aspect of RF and microwave power amplifiers***

### 3.1. Main characteristics

 
#### Generalized single-stage power amplifier circuit



**Two-port active device is characterized by immittance  $W$ -parameters which means system of impedance  $Z$ -parameters or admittance  $Y$ -parameters**

**Matching circuits are necessary to transform source  $W_S$  and load  $W_L$  immittances into definite values between points 1-2 and 3-4, respectively**

 
**If source of input signal is presented by current source with internal admittance  $Y_S$**



**$\Rightarrow$  device is characterized by  $Y$ -parameters**

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases}$$

 **If source of input signal is presented by voltage source with internal impedance  $Z_S$**



**$\Rightarrow$  device is characterized by  $Z$ -parameters**

$$\begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{cases} \quad 2$$

### 3.1. Main characteristics

#### Power amplifier gain (in terms of Y-parameters)

- **Operating power gain  $G_P = P_L/P_{in}$  - ratio of power dissipated in active load  $G_L$  to power delivered to input port of active device with admittance  $Y_{in}$  : this gain is independent of  $G_S$  but is strongly dependent on  $G_L$**
- **Available power gain  $G_A = P_{out}/P_S$  - ratio of power available at output port of active device with admittance  $Y_{out}$  to power available from source  $G_S$  : this gain depends on  $G_S$  but is independent of  $G_L$**
- **Transducer power gain  $G_T = P_L/P_S$  - ratio of power dissipated in active load  $G_L$  to power available from source  $G_S$  : this gain strongly depends on both  $G_S$  and  $G_L$**
- **Maximum available gain MAG - theoretical power gain of active device when its reverse transfer function  $Y_{12}$  is set equal to zero : represents theoretical gain limit that can be achieved with given device under assumption of conjugate input and output impedance matching**


### 3.1. Main characteristics

#### Operating power gain

Two types of power gain are widely used: operating power gain  $G_P$  and transducer power gain  $G_T$

- operating power gain to characterize device amplifying capability and multistage power amplifier

 - transducer power gain to evaluate input matching and stability



Power flowing from input port

$$P_{in} = 0.5 V_1^2 \operatorname{Re} Y_{in}$$

From

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases}$$

in view of

$$I_2 = -Y_L V_2$$



input admittance

$$Y_{in} = \frac{I_1}{V_1} = Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22} + Y_L}$$

Output power dissipated in load

$$P_L = 0.5 V_2^2 \operatorname{Re} Y_L$$




operating power gain

$$G_P = \frac{P_L}{P_{in}} = \frac{|Y_{21}|^2 \operatorname{Re} Y_L}{|Y_{22} + Y_L|^2 \operatorname{Re} Y_{in}}$$

### 3.1. Main characteristics

#### Transducer power gain

 **Transducer power gain  $G_T$  includes assumption of conjugate matching both load and source**



**Power flowing from input port**

$$P_S = \frac{I_S^2}{8\text{Re}Y_S}$$

**From**

$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 \\ I_2 = Y_{21}V_1 + Y_{22}V_2 \end{cases}$$

**in view of**

$$I_S = Y_S V_1 + I_1$$



**source current**

$$I_S = \frac{(Y_{11} + Y_S)(Y_{22} + Y_L) - Y_{12}Y_{21}}{Y_{22} + Y_L} V_1$$

**Output power dissipated in load**

$$P_L = 0.5 V_2^2 \text{Re}Y_L$$



**transducer power gain**


$$G_T = \frac{P_L}{P_S} = \frac{4 |Y_{21}|^2 \text{Re}Y_S \text{Re}Y_L}{|(Y_{11} + Y_S)(Y_{22} + Y_L) - Y_{12}Y_{21}|^2}$$

**Maximum available gain**  
( $Y_{12} = 0, Y_S = Y_{11}^*, Y_L = Y_{22}^*$ )

$$\text{MAG} = \frac{|Y_{21}|^2}{4 \text{Re}Y_{11} \text{Re}Y_{22}}$$

### 3.1. Main characteristics

#### Small-signal FET power amplifier

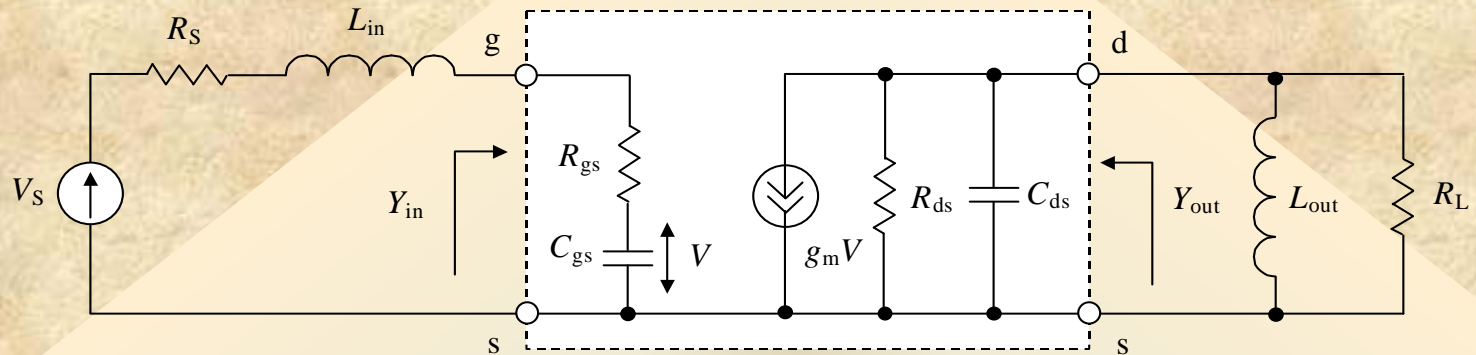

**Equivalent circuit with  $C_{gd} = 0$**

$$Y_{11} = j\omega C_{gs} / (1 + j\omega R_{gs} C_{gs})$$

$$Y_{12} = 0$$

$$Y_{21} = g_m / (1 + j\omega R_{gs} C_{gs})$$

$$Y_{22} = (1/R_{ds}) + j\omega C_{ds}$$

**Input and output conjugate matching**

$$R_S = R_{gs} \quad R_L = R_{ds}$$

$$L_{in} = 1/\omega^2 C_{gs} \quad L_{out} = 1/\omega^2 C_{ds}$$

$$G_T(C_{gd} = 0) = MAG = \left( \frac{f_T}{f} \right)^2 \frac{R_{ds}}{4R_{gs}}$$

$$f_T = g_m / 2\pi C_{gs} \quad \text{- transition frequency}$$

$$f_{max} = \frac{f_T}{2} \sqrt{\frac{R_{ds}}{R_{gs}}} \quad \text{- maximum frequency where } MAG = 1$$

$$G_T(f) = G_T(f_T) \left( \frac{f_T}{f} \right)^2 \quad \text{- gain estimation at any frequency vs gain at transition frequency}$$

### 3.2. Gain and stability

**Principle of power amplifier design - to provide maximum power gain and efficiency for given output power with predictable degree of stability**

**Main reasons of instability:**

- **positive feedback from output to input through intrinsic feedback capacitance or inductance of common-grounded terminal**
- **oscillation conditions due to external elements forming positive feedback loop**

**In terms of immittance approach, circuit will be unconditionally stable if for both hypothetical conditions of open-circuited input and output ports:**

$$\begin{cases} \operatorname{Re} [W_S(\omega) + W_{\text{in}}(\omega)] > 0 \\ \operatorname{Im} [W_S(\omega) + W_{\text{in}}(\omega)] = 0 \end{cases} \quad \begin{cases} \operatorname{Re} [W_L(\omega) + W_{\text{out}}(\omega)] > 0 \\ \operatorname{Im} [W_L(\omega) + W_{\text{out}}(\omega)] = 0 \end{cases}$$

**In case of opposite signs, active two-port network can be treated as unstable or potentially unstable (having negative input or output immittance)**

**When**  $\operatorname{Re} [W_S(\omega)] > 0$        $\operatorname{Re} [W_L(\omega)] > 0$

**Requirements of power amplifier stability can be simplified to**

$$\operatorname{Re} [W_{\text{in}}(\omega)] > 0 \quad \operatorname{Re} [W_{\text{out}}(\omega)] > 0$$

## 3.2. Gain and stability

### Device stability

In common case, value of  $\text{Re}W_{\text{out}}$  depends on  $W_S \Rightarrow$  within definite values of  $W_S$ ,  $\text{Re}W_{\text{out}} < 0$  and two-port network will be potentially unstable

$$W_{\text{out}} = W_{22} - \frac{W_{12} W_{21}}{W_{11} + W_S}$$

To provide unconditional stability  $\text{Re}[W_{\text{out}}(\omega)]|_{\min} > 0$

$$\frac{\partial \text{Re}W_{\text{out}}}{\partial \text{Im}W_S} = 0 \quad \Rightarrow \quad \text{Re}W_{\text{out}} = \text{Re}W_{22} - \frac{|W_{12} W_{21}| + \text{Re}(W_{12} W_{21})}{2\text{Re}(W_{11} + W_S)}$$

Minimum positive value when  $\text{Re}W_S = 0$  :

$$\text{Re}W_{\text{out}} = \text{Re}W_{22} - \frac{|W_{12} W_{21}| + \text{Re}(W_{12} W_{21})}{2\text{Re}(W_{11})}$$

$$2\text{Re}W_{11} \text{Re}W_{22} - |W_{12} W_{21}| - \text{Re}(W_{12} W_{21}) > 0$$

$$K = \frac{2 \text{Re}W_{11} \text{Re}W_{22} - \text{Re}(W_{12} W_{21})}{|W_{12} W_{21}|}$$

- device stability factor

Unconditional stability:  $K > 1$

Potential instability:  $-1 < K < 1$



## 3.2. Gain and stability

### Circuit stability

When active device is potentially unstable, power amplifier stability can be improved with proper choice of source and load immittances,  $W_S$  and  $W_L$ :

$$K_T = \frac{2 \operatorname{Re}(W_{11} + W_S) \operatorname{Re}(W_{22} + W_L) - \operatorname{Re}(W_{12} W_{21})}{|W_{12} W_{21}|} > 1$$

### Maximum gain with unconditionally stable device

When  $K > 1$ , it is necessary to choose load immittance  $W_L$  to maximize finite value of operating power gain  $G_P$ :

$$G_P = \frac{P_L}{P_{in}} = \frac{|W_{21}|^2 \operatorname{Re}W_L}{|W_{22} + W_L|^2 \operatorname{Re}W_{in}}$$

$$\frac{\partial G_P}{\partial \operatorname{Re}W_L} = 0$$

$$\frac{\partial G_P}{\partial \operatorname{Im}W_L} = 0$$



$$\operatorname{Re}W_L^o = \frac{|W_{12} W_{21}|}{2 \operatorname{Re}W_{11}} \sqrt{K^2 - 1}$$

$$\operatorname{Im}W_L^o = \frac{\operatorname{Im}(W_{12} W_{21})}{2 \operatorname{Re}W_{11}} - \operatorname{Im}W_{22}$$

$$G_{P_{\max}} = \left| \frac{W_{21}}{W_{12}} \right| / \left( K + \sqrt{K^2 - 1} \right) \quad \text{- maximum gain (maximum achievable value at } K = 1)$$

### 3.3. Stabilization circuit technique

#### Frequency domains of BJT potential instability

**Stability factor through Z-parameters:**

$$K = \frac{2 R_{11} R_{22} - \operatorname{Re}(Z_{12} Z_{21})}{|Z_{12} Z_{21}|}$$


**BJT equivalent circuit Z-parameters:**

$$Z_{11} = r_b + \frac{1}{g_m} / \left( 1 + j \frac{\omega}{\omega_T} \right)$$

$$Z_{12} = \frac{1}{g_m} / \left( 1 + j \frac{\omega}{\omega_T} \right)$$

$$Z_{21} = \left( \frac{1}{g_m} - \frac{1}{j\omega C_\mu} \right) / \left( 1 + j \frac{\omega}{\omega_T} \right)$$
 
$$Z_{22} = \left( \frac{1}{g_m} + \frac{1}{\omega_T C_\mu} \right) / \left( 1 + j \frac{\omega}{\omega_T} \right)$$



**BJT stability factor**

$$K = 2r_b g_m \frac{1 + \frac{g_m}{\omega_T C_\mu}}{\sqrt{1 + \left( \frac{g_m}{\omega C_\mu} \right)^2}}$$

**Maximum value at higher frequencies:**

$$K = 2r_b g_m \left( 1 + \frac{g_m}{\omega_T C_\mu} \right)$$

### 3.3. Stabilization circuit technique

#### Frequency domains of BJT potential instability

At low frequencies if to take into account dynamic base-emitter resistance  $r_\pi$  and Early collector-emitter resistance  $r_o \Rightarrow K > 1$



Only one unstable frequency domain with low  $f_{p1}$  and high  $f_{p2}$  boundary frequencies


$$\text{For } K = 1 \quad f_{p2} = \frac{g_m}{2\pi C_\mu} / \sqrt{(2r_b g_m)^2 \left(1 + \frac{g_m}{\omega_T C_\mu}\right)^2 - 1} \quad \text{or} \quad f_{p2} \cong \frac{1}{4\pi r_b C_\pi}$$

In common case, at higher frequencies with parasitic emitter lead inductance  $L_e$  :

Expression for low  $f_{p3}$  and high  $f_{p4}$  boundary frequencies of second domain of BJT potential instability

$$f_{p3,4} = f_T \sqrt{\frac{1 - 4\omega_T r_b C_\mu}{8\omega_T r_b C_\mu} \mu} \sqrt{\left(\frac{1 - 4\omega_T r_b C_\mu}{8\omega_T r_b C_\mu}\right)^2 - \frac{1 + \kappa}{\omega_T r_b C_\mu \kappa^2}}$$

where  $\kappa = \omega_T L_e / r_b$

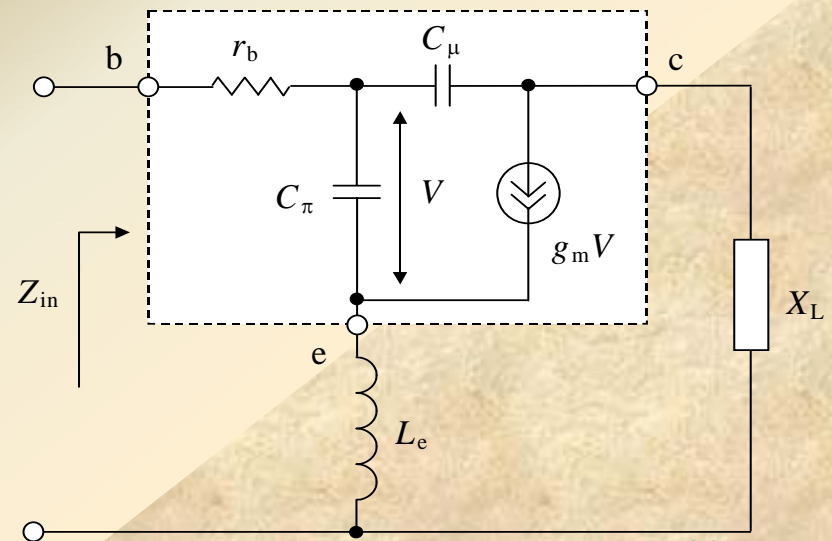

### 3.3. Stabilization circuit technique

#### Frequency domains of BJT potential instability


Appearance of second frequency domain of BJT potential instability is result of simultaneous effect of feedback capacitance  $C_\mu$  and emitter lead inductance  $L_e$

- first case for  $L_e = 0$  and reactive load  $X_L$ :  
one frequency domain of potential instability

$$Z_{in} = r_b + \frac{1}{g_m} \cdot \frac{1}{1 + j \frac{\omega}{\omega_T}} \cdot \frac{1 + \frac{g_m}{\omega C_\mu}}{1 + \frac{g_m}{\omega_T C_\mu} (1 - \omega C_\mu X_L) + j g_m X_L}$$



Hartley oscillator

 

Boundary condition of first potential instability domain:

$$\frac{L_L}{L_S} \approx \frac{1}{\omega_T r_b C_\mu}$$



to prevent oscillations  $\Rightarrow$  reduce value of collector choke inductance and increase value of base choke inductance

### 3.3. Stabilization circuit technique


#### Frequency domains of BJT potential instability

Appearance of second frequency domain of BJT potential instability is result of simultaneous effect of feedback capacitance  $C_{\mu}$  and emitter lead inductance  $L_e$

- second case for  $L_e \neq 0$  and reactive load  $X_L$ : two frequency domains of potential instability

 
#### first frequency domain

- parasitic oscillator with inductive source and load reactances


 
#### second frequency domain

- parasitic oscillator with capacitive source and inductive load reactances



### 3.3. Stabilization circuit technique

#### Frequency domains of MOSFET potential instability

Stability factor through Y-parameters:

$$K = \frac{2 G_{11} G_{22} - \operatorname{Re}(G_{12} G_{21})}{|Y_{12} Y_{21}|}$$


MOSFET equivalent circuit Y-parameters:

$$Y_{11} = \frac{j\omega C_{gs}}{1 + j\omega R_{gs} C_{gs}} + j\omega C_{gd}$$

$$Y_{12} = -j\omega C_{gd}$$

$$Y_{21} = \frac{g_m}{1 + j\omega R_{gs} C_{gs}} - j\omega C_{gd}$$
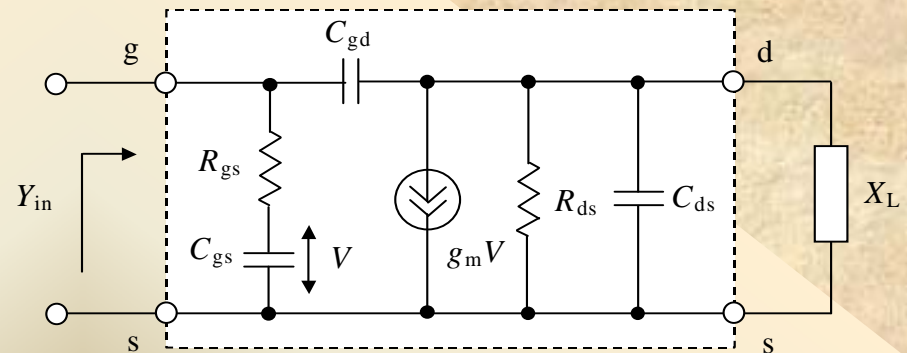
$$Y_{22} = \frac{1}{R_{ds}} + j\omega (C_{ds} + C_{gd})$$



MOSFET stability factor:

$$K = \left[ 1 + \frac{2}{g_m R_{ds}} \left( 1 + \frac{C_{gs}}{C_{gd}} \right) \right] \frac{\omega R_{gs} C_{gs}}{\sqrt{1 + (\omega R_{gs} C_{gs})^2}}$$

Maximum value at higher frequencies:

$$K = \left[ 1 + \frac{2}{g_m R_{ds}} \left( 1 + \frac{C_{gs}}{C_{gd}} \right) \right]$$

### 3.3. Stabilization circuit technique

#### Frequency domains of MOSFET potential instability

At low frequencies if to take into account gate leakage resistance  $\Rightarrow K > 1$




Only one unstable frequency domain with low  $f_{p1}$  and high  $f_{p2}$  boundary frequencies


For  $K = 1$

$$f_{p2} = \frac{1}{4\pi R_{gs} C_{gs}} \cdot \frac{g_m R_{ds}}{\sqrt{1 + \frac{C_{gs}}{C_{gd}}}} \cdot \frac{1}{\sqrt{1 + \frac{C_{gs}}{C_{gd}} + g_m R_{ds}}} \quad \text{or} \quad f_{p2} \approx \frac{1}{4\pi R_{gs} C_{gs}}$$

 In common case, parasitic emitter lead inductance  $L_e$  creates second frequency domain of potential instability at higher frequencies



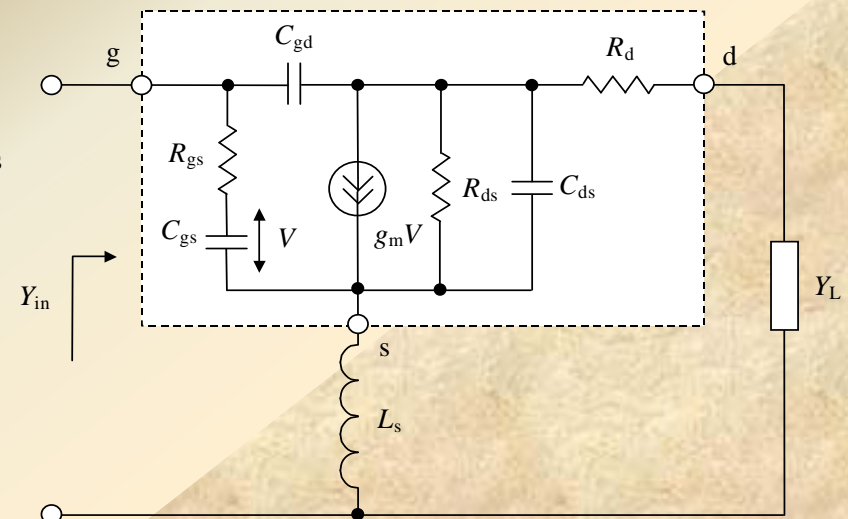When  $\kappa = 3.5 \Rightarrow$  second frequency domain disappears




### 3.3. Stabilization circuit technique

#### Frequency domains of MOSFET potential instability

Appearance of second frequency domain of MOSFET potential instability is result of simultaneous effect of feedback capacitance  $C_{gd}$  and source lead inductance  $L_s$

- first case for  $L_s = 0$  and reactive load  $X_L$ : one frequency domain of potential instability
 
$$Y_{in} = \frac{j\omega C_{gs}}{1 + j\omega R_{gs} C_{gs}} \left[ 1 + g_m R_{ds} \frac{1 - j\frac{\omega}{\omega_T} (1 + j\omega R_{gs} C_{gs})}{1 + j\omega R_{ds} C_{ds} \left( 1 + \frac{C_{gd}}{C_{ds}} + \frac{B_L}{\omega C_{ds}} \right)} \right]$$



Hartley oscillator



### 3.3. Stabilization circuit technique


#### Frequency domains of MOSFET potential instability

Appearance of second frequency domain of MOSFET potential instability is result of simultaneous effect of feedback capacitance  $C_{gd}$  and source lead inductance  $L_s$

- second case for  $L_s \neq 0$  and reactive load  $X_L$ : two frequency domain of potential instability

 
#### first frequency domain

- parasitic oscillator with inductive source and load reactances


 
#### second frequency domain

- parasitic oscillator with capacitive source and inductive load reactances



### **3.3. Stabilization circuit technique**

#### **General requirements to provide stable operation of power amplifier:**


- use active device with stability factor  $K > 1$**
- if it is impossible to choose active device with  $K > 1$ , provide circuit stability factor  $K_T > 1$  on operating frequency by appropriate choice of real parts of source and load immittances**
- disrupt equivalent circuit of possible parasitic oscillators**
- choose such reactive parameters of matching circuits adjacent to input and output of active device which are necessary to avoid self-oscillation conditions**

**In common case, it is difficult to propose unified approach to provide stable operation of different power amplifiers especially for multistage power amplifier**


### 3.3. Stabilization circuit technique

 **Stability analysis must be done in different frequencies ranges:**

- at lower frequencies when frequency of parasitic oscillations  $f_p$  is significantly smaller operating frequency  $f_0$  ( $f_p \ll f_0$ )




 
- using stabilizing resistor  $R_1$  in parallel to RF choke



- using stabilizing resistor  $R_1$  in parallel to additional RF choke to avoid degradation of RF performance

- using additional RF choke if impedance of series  $R_1C_2$  circuit is too high

 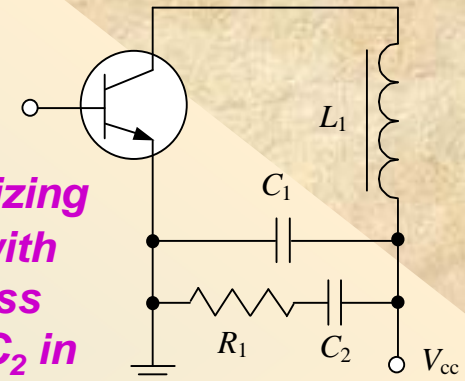
- using stabilizing resistor  $R_1$  with series bypass capacitance  $C_2$  in parallel to power supply



### 3.3. Stabilization circuit technique

 **Stability analysis must be done in different frequencies ranges:**

- at higher frequencies when frequency of parasitic oscillations  $f_p$  is significantly higher operating frequency  $f_0$  ( $f_p \gg f_0$ )





### 3.3. Stabilization circuit technique

**Stability analysis must be done in different frequencies ranges:**

- near operating frequency frequency when frequency of parasitic oscillations  $f_p$  is close to operating frequency  $f_0$  ( $f_p \approx f_0$ )

**series connection of stabilizing RLC circuit connected in series between active device and output matching circuit**

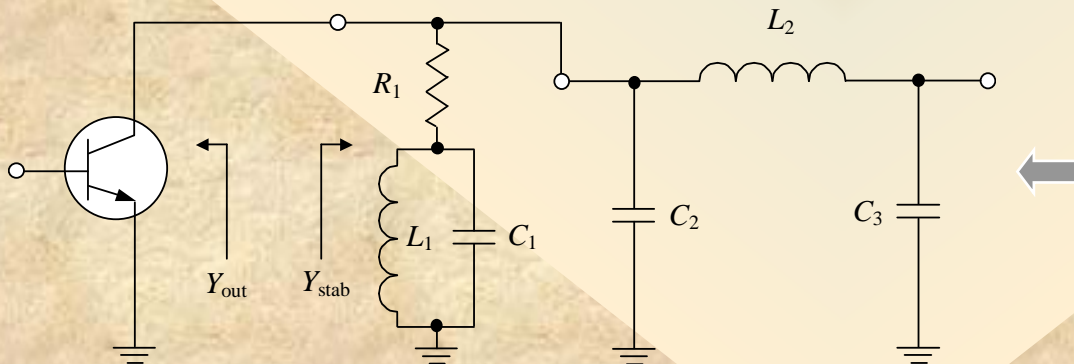 
**series  $L_1C_1$  circuit is tuned on operating frequency**




**parallel connection of stabilizing RLC circuit between active device and output matching circuit**

# Class A

## 3.4. Class-A,-B,-C operation modes

 

**Output voltage**

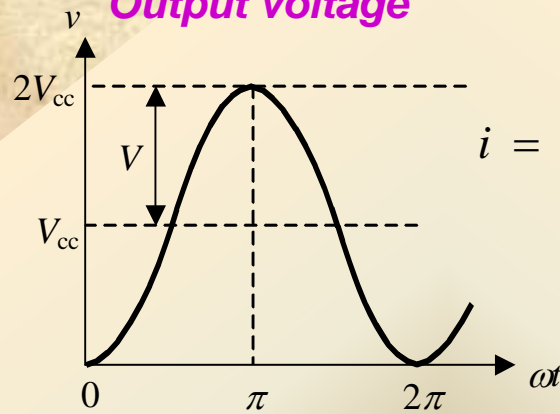

$$v_{in} = V_b + V_{in} \cos \omega t$$

- input sinusoidal voltage

$$i = I_q + I \cos \omega t$$

- output sinusoidal current

$$v = V_{cc} - V \cos \omega t$$

- output sinusoidal current

$$P_0 = I_q V_{cc}$$

- DC output power

$$P = 0.5 I V$$

- fundamental output power



$$\eta = \frac{P}{P_0} = \frac{1}{2} \frac{I}{I_q} \frac{V}{V_{cc}} = \frac{1}{2} \frac{I}{I_q} \xi$$

- collector efficiency

$$\xi = V / V_{cc}$$

- voltage peak factor

**Transfer characteristic**

  

**Output current**

For ideal condition of zero saturation voltage when

$$\begin{aligned} I / I_q &= 1 \\ \xi &= 1 \end{aligned}$$


$$\eta = 0.5$$

- maximum collector efficiency in Class A


**Input voltage**

# Class B

## 3.4. Class-A,-B,-C operation modes

 


Transfer characteristic

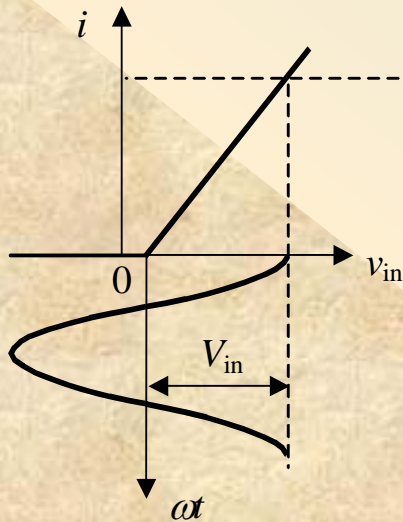


Input voltage

Output voltage

 

Output current

 

For moment with maximum current

$$i = I_{\max} = I(1 - \cos\theta)$$

$$v_{in} = V_b + V_{in} \cos\omega t$$

- input sinusoidal voltage

$$i = \begin{cases} I_q + I \cos\omega t, & -\theta \leq \omega t < \theta \\ 0, & \theta \leq \omega t < 2\pi - \theta \end{cases}$$

- output current  
conduction angle 2θ  
indicates its duty cycle

For moment with zero current

$$i = 0 = I_q + I \cos\theta$$

$$\cos\theta = -\frac{I_q}{I}$$

$$i = I(\cos\omega t - \cos\theta)$$

### 3.4. Class-A,-B,-C operation modes

$I_q = -I \cos \theta$  - quiescent current as function of half-conduction angle  $\theta$

- when  $\theta > 90^\circ \Rightarrow \cos \theta < 0 \Rightarrow I_q > 0$  - Class AB operation mode
- when  $\theta = 90^\circ \Rightarrow \cos \theta = 0 \Rightarrow I_q = 0$  - Class B operation mode
- when  $\theta < 90^\circ \Rightarrow \cos \theta > 0 \Rightarrow I_q < 0$  - Class C operation mode

$i = I_0 + I_1 \cos \omega t + I_2 \cos 2\omega t + I_3 \cos 3\omega t + \dots$  - Fourier series

where  $I_0 = \frac{1}{2\pi} \int_{-\theta}^{\theta} I (\cos \omega t - \cos \theta) d(\omega t) = I \gamma_0$  - DC component

$I_1 = \frac{1}{\pi} \int_{-\theta}^{\theta} I (\cos \omega t - \cos \theta) \cos \omega t d(\omega t) = I \gamma_1$  - fundamental component

where  $\gamma_0 = \frac{1}{\pi} (\sin \theta - \theta \cos \theta)$ ,  $\gamma_1 = \frac{1}{\pi} (\theta - \sin \theta \cos \theta)$  - current coefficients

$\eta = \frac{P_1}{P_0} = \frac{1}{2} \frac{I_1}{I_0} \xi = \frac{1}{2} \frac{\gamma_1}{\gamma_0} \xi$  - collector efficiency


When  $\theta = 90^\circ$  and  $\xi = 1$  

$$\eta = \frac{\pi}{4} \cong 0.785$$

- maximum collector efficiency in Class B



### 3.4. Class-A,-B,-C operation modes

 

$$i = \left( I_q + \frac{V_{cc}}{\gamma_1 R} \right) - \frac{v}{\gamma_1 R}$$

- dynamic characteristic of power amplifier or load line function within


$$-\theta \leq \omega t < \theta$$

$$\tan \beta = \frac{I}{V(1 - \cos \theta)} = \frac{1}{\gamma_1 R}$$

- slope of load line

## Class B


### 3.4. Class-A,-B,-C operation modes

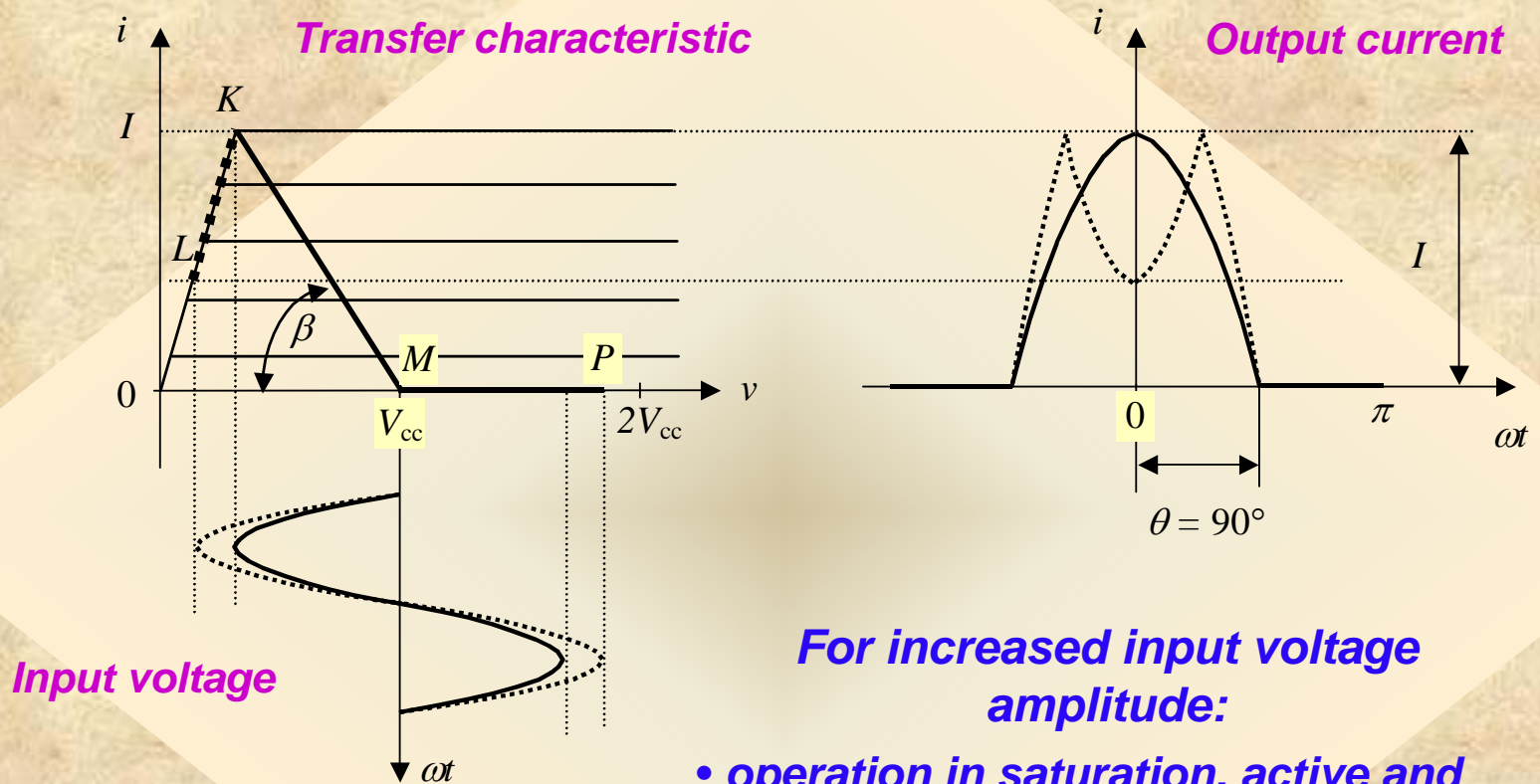


**For increased input voltage amplitude:**

- operation in saturation, active and pinch-off regions
- load line represents broken line with three sections:
  - $KL$  - saturation region (depression in collector current waveform)
  - $KM$  - active region
  - $MP$  - pinch-off region

### 3.4. Class-A,-B,-C operation modes

 

a).

 

b).

- collector current becomes asymmetrical for complex load impedance



asymmetrical load line

- for inductive load impedance, depression in collector current waveform is shifted to the left (a)
- for capacitive load impedance, depression in collector current waveform is shifted to the right (b)

**Reason: different phase conditions for higher-order harmonics**

### 3.5. Linearity

To evaluate nonlinear properties of power amplifier, consider transfer function of active device in common form of  $i = f(v)$  where  $i$  - output current,  $v$  - input voltage

$$f(v) = f(V_0) + \sum_{n=1}^{\infty} \frac{1}{n!} \left. \frac{\partial^{(n)} f(v)}{\partial v^n} \right|_{v=V_0} (v - V_0)^n \quad \text{where } V_0 - \text{DC bias voltage}$$

Usual method to determine nonlinear properties is to apply two-tone excitation test signal


For two signals with equal amplitudes  $V_1 = V_2 = V$ :

$$v = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t \\ = 2V \cos \omega t \cos \Omega t$$

where

$$\omega = (\omega_1 + \omega_2)/2$$

$$\Omega = (\omega_1 - \omega_2)/2$$

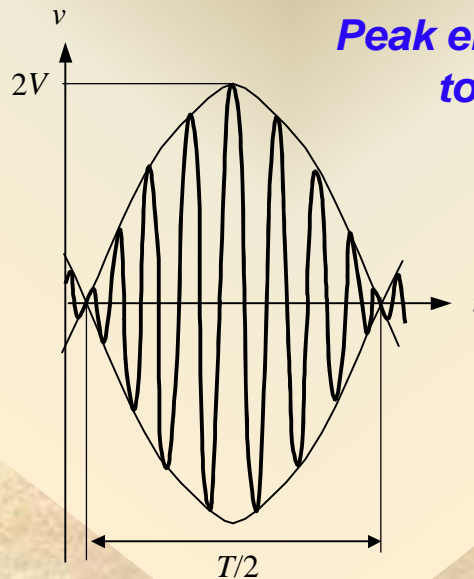

Peak envelope power PEP corresponds to maximum amplitude of 2V:

$$P_{\text{PEP}} = (2V)^2 / 2R$$

Total power due to each tone:

$$P_{\text{total}} = P_{\omega_1} + P_{\omega_2} = V^2 / R$$

$$P_{\text{PEP}} = 2P_{\text{out}} = 4P$$

where  $P = P_{\omega_1} = P_{\omega_2}$  28

### 3.5. Linearity

**For two-tone excitation test signal**  $v = V_0 + V_1 \cos \omega_1 t + V_2 \cos \omega_2 t$

**Taylor's expansion of output current for first three derivatives results in**  $i = f(v) = f(V_0) + \frac{1}{4} \frac{\partial^2 f(v)}{\partial v^2} \Big|_{v=V_0} (V_1^2 + V_2^2)$

$$\begin{aligned}
 & + \left[ f'(V_0) + \frac{1}{4} \frac{\partial^3 f(v)}{\partial v^3} \Big|_{v=V_0} \left( \frac{1}{2} V_1^2 + V_2^2 \right) \right] V_1 \cos \omega_1 t + \left[ f'(V_0) + \frac{1}{4} \frac{\partial^3 f(v)}{\partial v^3} \Big|_{v=V_0} \left( V_1^2 + \frac{1}{2} V_2^2 \right) \right] V_2 \cos \omega_2 t \\
 & + \frac{1}{4} \frac{\partial^2 f(v)}{\partial v^2} \Big|_{v=V_0} (V_1^2 \cos 2\omega_1 t + V_2^2 \cos 2\omega_2 t) + \frac{1}{24} \frac{\partial^3 f(v)}{\partial v^3} \Big|_{v=V_0} (V_1^3 \cos 3\omega_1 t + V_2^3 \cos 3\omega_2 t) \\
 & + \frac{1}{2} \frac{\partial^2 f(v)}{\partial v^2} \Big|_{v=V_0} V_1 V_2 \cos (\omega_1 \pm \omega_2) t \\
 & + \frac{1}{8} \frac{\partial^3 f(v)}{\partial v^3} \Big|_{v=V_0} [V_1^2 V_2 \cos (2\omega_1 \pm \omega_2) t + V_1 V_2^2 \cos (\omega_1 \pm 2\omega_2) t] K
 \end{aligned}$$

### **3.5. Linearity**

#### **Main conclusions:**

- **variation of DC bias point is directly proportional to second derivative (in common case - even derivatives) of transfer function**
- **device transfer function will be linear only if third derivative (in common case - odd derivatives) is equal to zero**
- **even harmonic components are result of even derivatives of transfer function; odd harmonic components are result of odd derivatives of transfer function**
- **first-order mixing products (total and differential) depend on even derivatives of transfer function**
- **mixing products of third and higher order are mainly determined by odd derivatives of transfer function**

**Distortions which are determined by second derivatives of device transfer function are called second-order intermodulation distortions; distortion which are determined by third-order derivatives are called third-order intermodulation distortions**

### 3.5. Linearity

Output current amplitude of fundamental, second and third harmonic or intermodulation components depends on first, second and third degree of input voltage, respectively



Consequently, output powers of linear, second- or third-order component show straight-line behavior and vary by 1 dB, 2 dB and 3 dB, respectively, with 1-dB variation of input power

These straight lines intersect at some points which are called intercept points  $IP_n$

$$P_{IM_n} = nP_{\omega_1} - (n - 1)IP_n \text{ (dBm)}$$


**Second harmonic component**

$$P_{2\omega_1} = 2P_{\omega_1} - IP_2 \text{ (dBm)}$$

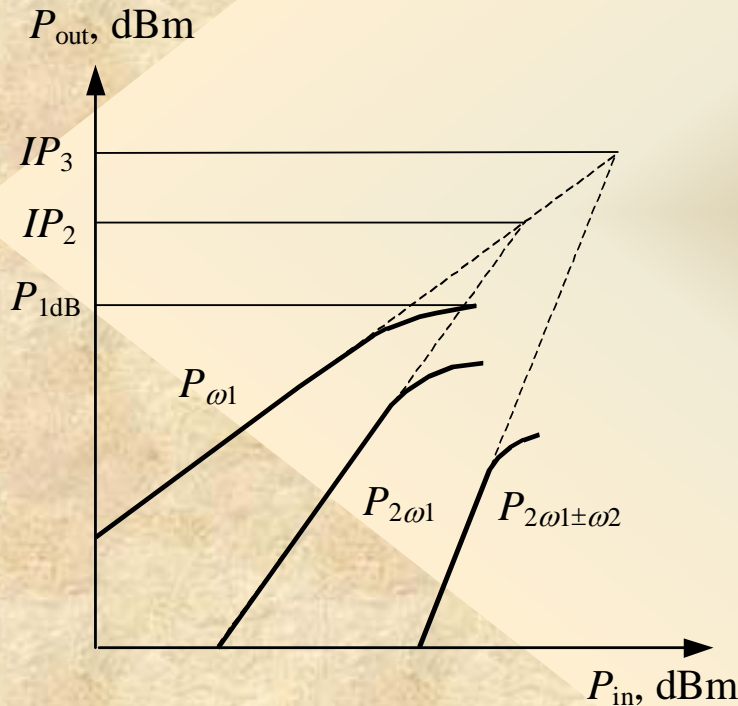**Third-order intermodulation component**

$$P_{2\omega_1-\omega_2} = 3P_{\omega_1} - 2IP_3 \text{ (dBm)}$$



$$P_{1dB} = IP_3 - 9 \text{ (dBm)} - \text{1-dB gain compression point}$$


  
### 3.5. Linearity

For MOSFET device, there is optimum bias point with drain quiescent current  $I_{dq}$  in limits of  $0.1...0.15 I_{dss}$  when  $IM_3$  can be minimized providing high-power and high-efficiency operation because of quadratic transfer function in this region

Output spectrum containing n-order intermodulation components



$$IM_3 = 10 \log_{10} \left( P_{2\omega_1 - \omega_2} / P \right) = P_{2\omega_1 - \omega_2} - P \text{ (dBc)} \quad \text{- third-order intermodulation product}$$

$$IM_5 = 10 \log_{10} \left( P_{3\omega_1 - 2\omega_2} / P \right) = P_{3\omega_1 - 2\omega_2} - P \text{ (dBc)} \quad \text{- fifth-order intermodulation product}$$


where  $P = P_{\omega_1} = P_{\omega_2}$





### 3.6. DC biasing

**DC biasing of active device provides required operation condition which should be stable over input power, temperature or technology process variations**

 **For MOSFETs as voltage controlled devices, at normal conditions it is enough to use resistive divider to set gate bias voltage**



  **However, in wide temperature range when device threshold voltage varies with temperature ( $2 \text{ mV}/^\circ\text{C}$ ), to reduce quiescent current variation, it is possible to use silicon diode in series to variable resistor**





**When device threshold voltage is too high, it is best to connect several silicon diodes in series**

**Such simple bias circuit configurations for MOSFETs become possible in view of extremely small gate DC current equal to its leakage current only**

## 3.6. DC biasing
  
### Current mirror bias circuits

For bipolar transistor as current-controlled device, to stabilize quiescent current it is best to use current-mirror type of bias circuits where reference diode is formed using same diode-connected transistor with substantially smaller area



To minimize quiescent current variations over temperature, ratio of ballast resistors  $R_1/R_0$  must be equal to device area ratio  $Q_0/Q_1$



However, to fix current flowing from reference source through resistor  $R_2$ , its value should be much higher than base current of RF device  $Q_0$

To reduce current from reference source and to increase current driving capability for high power RF device, driving transistor  $Q_3$  is used to feed DC base current for RF device  $Q_0$


### 3.6. DC biasing
 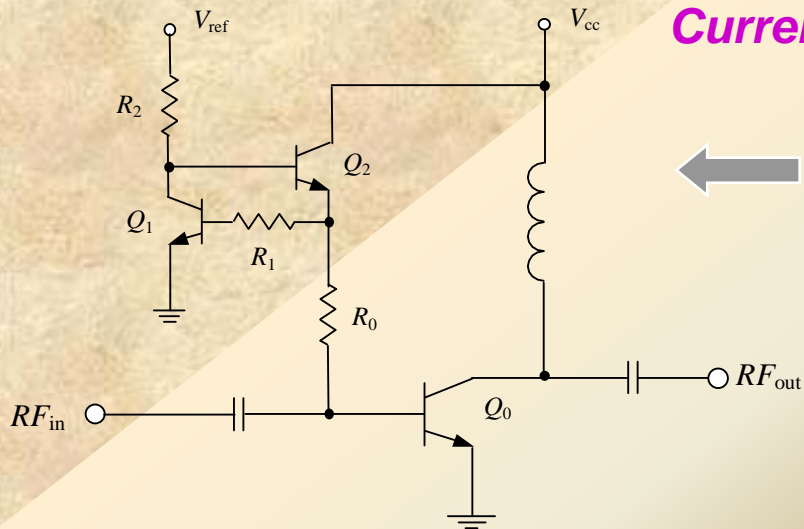
#### Current mirror bias circuits

Popular configuration of temperature compensated bias circuit contains one reference transistor and one driving device



 It is very important to provide ratio of ballast resistors  $R_1/R_0$  equal to ratio of device areas  $Q_0/Q_1$  which minimizes variations over temperature as well as stabilizes DC bias point over input power



1 - required value of ballast resistor  $R_1$


2 -  $R_1 = 0$

To minimize current from reference voltage source, emitter follower configuration can be used where this current is equal to extremely small base current of emitter follower device  $Q_0$
 
### 3.7. Push-pull amplifiers

Push-pull operation helps to increase values of input and output impedances and to additionally suppress even harmonics

For 50% duty cycle of each device (ideal Class B) with driving sinusoidal voltage:



first transistor collector current

$$i_{c1} = \begin{cases} +I_c \sin \theta, & 0 \leq \theta < \pi \\ 0, & \pi \leq \theta < 2\pi \end{cases}$$

second transistor collector current


$$i_{c2} = \begin{cases} 0, & 0 \leq \theta < \pi \\ -I_c \sin \theta, & \pi \leq \theta < 2\pi \end{cases}$$

Being transformed through output transformer  $T_2$ , total collector current:


$$i_L(\theta) = i_{c1}(\theta) - i_{c2}(\theta) = I_c \sin(\theta)$$

Current flowing in center tap of primary winding of transformer  $T_2$ :

$$i_{cc}(\theta) = i_{c1}(\theta) + i_{c2}(\theta) = I_c |\sin(\theta)|$$

 

### 3.7. Push-pull amplifiers

 

*Ideally, even-order harmonics are canceled as they are in-phase and combined in center tap of primary winding of output transformer*

*To eliminate losses, it is necessary to connect bypass capacitance to this center point*

*As for 50% duty cycle, third- and higher-order odd harmonics do not exist, ideally sinusoidal signal will appear in load*

**Total DC collector current**

$$I_{co} = \frac{1}{2\pi} \int_0^{2\pi} i_{cc}(\theta) d\theta = \frac{2}{\pi} I_c$$

**For zero saturation resistance when collector voltage amplitude  $V_c = V_{cc}$  and equal turns of winding when  $V_L = V_c$ , DC and fundamental output powers**

$$P_0 = \frac{2}{\pi} I_c V_{cc} \quad P_{out} = \frac{1}{2} I_c V_{cc}$$

$$v_L(\theta) = I_c R_L \sin(\theta) = V_L \sin(\theta)$$

**Maximum theoretical collector efficiency that can be achieved in Class B operation**

$$\eta = \frac{P_{out}}{P_0} = \frac{\pi}{4} \cong 78.5\%$$

### 3.7. Push-pull amplifiers

*In balanced circuit, identical sides carry 180° out-of phase signals of equal amplitude*



*If perfect balance is maintained, there are midpoints where signal amplitudes are zero*

*Such a condition is called virtual grounding*

*Being inside device package with two balanced transistors, virtual ground reduces common-mode inductance and simplify matching circuit*


*Simplification for balanced transistors where matching parallel capacitances are combined and DC blocking capacitances are not required*

  *Matching conditions for single-ended transistor*


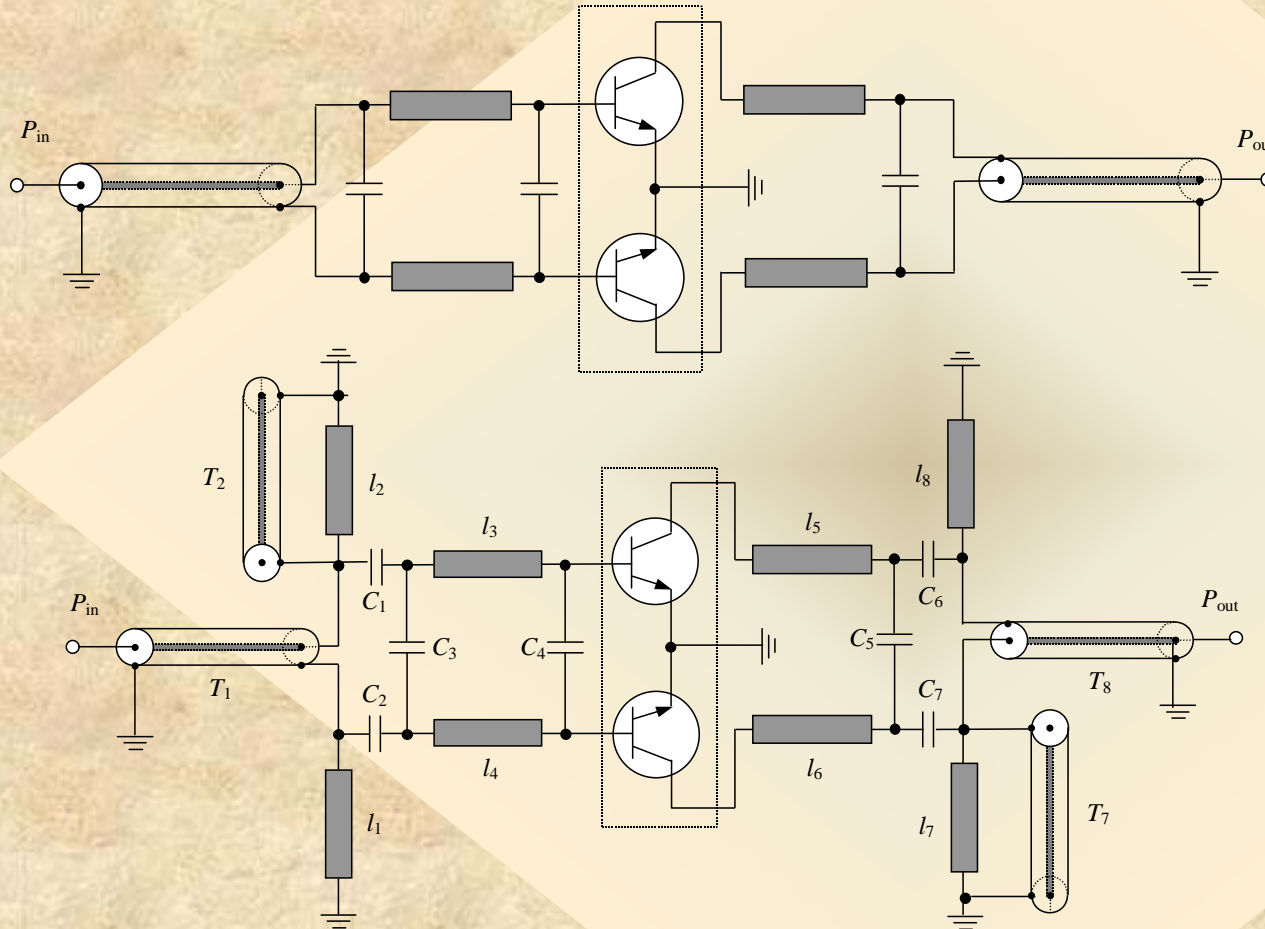
### 3.7. Push-pull amplifiers

For push-pull operation, unbalance-to-balance transformation is required




- most suitable approach is to use 1:1 coaxial transformer
- for 50-ohm source and load, its characteristic impedance = 50 Ohm and each balanced part sees 25 Ohm

- to minimize transformer size and provide broadband operation with minimum return loss, coaxial transformers are mounted and soldered along shortened microstrip lines and additional shortened stubs are added for symmetry

• as shortened stubs produce inductive impedances, series capacitors  $C_1$  and  $C_2$  are used forming high-pass matching sections

### 3.8. Practical aspect of RF and microwave power amplifiers
 
#### Typical microwave power amplifier topology




- **matching circuits in form of L-transformers: parallel microstrip open stubs represent capacitive reactances, series microstrip lines represent inductive reactances**
- **bias circuits contain quarterwave loaded and opened microstrip lines for RF signal isolation**



### 3.8. Practical aspect of RF and microwave power amplifiers
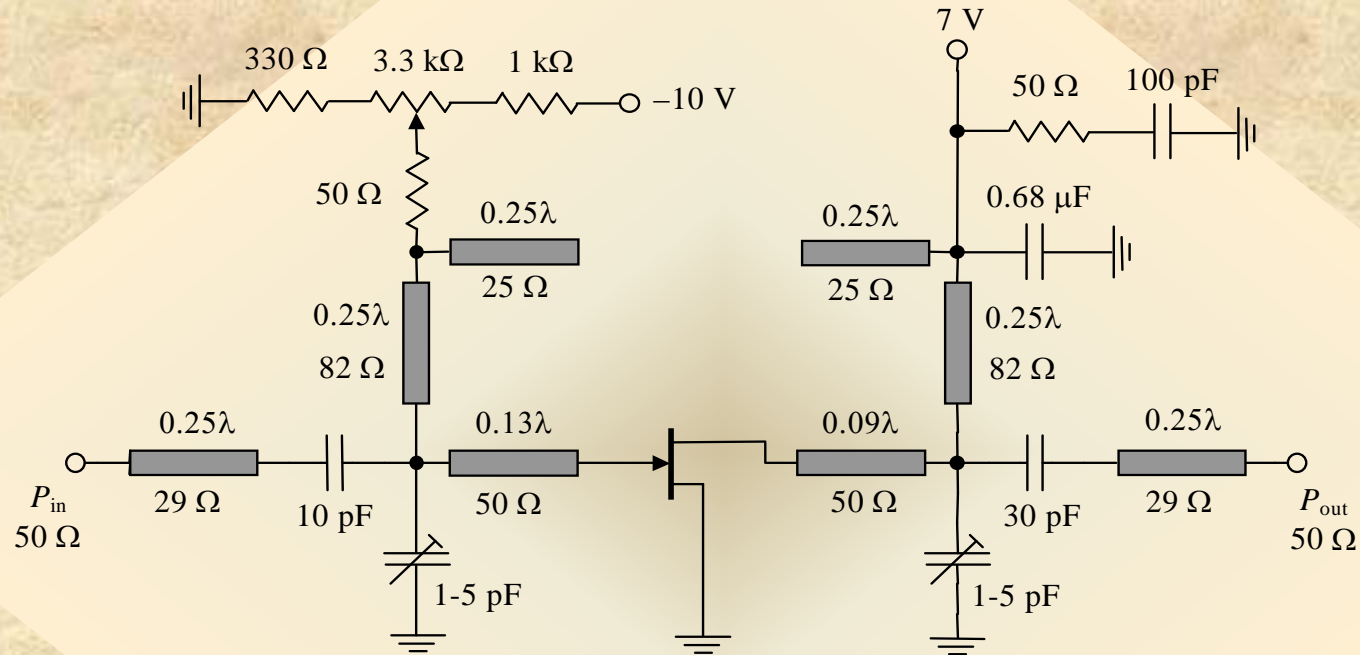
#### Microwave 2.5-2.7 GHz 5 W GaAs MESFET power amplifier topology



- **matching circuits are combinations of L-transformers (parallel capacitors and series microstrip lines) and quarterwave lines with different characteristic impedances**
- **drain bias circuit contains additional RC-circuit to prevent high-frequency oscillations and large capacitance to prevent low-frequency oscillations**


### 3.8. Practical aspect of RF and microwave power amplifiers

#### Microwave balanced power amplifier

- to combine output powers from two or more transistors at microwaves, 90-degree branch-line hybrids are widely used where active devices are isolated from each other

- at equal reflection coefficients from loads connected to output terminals, reflection wave is absent at input terminal and flowing to 50-ohm ballast resistor

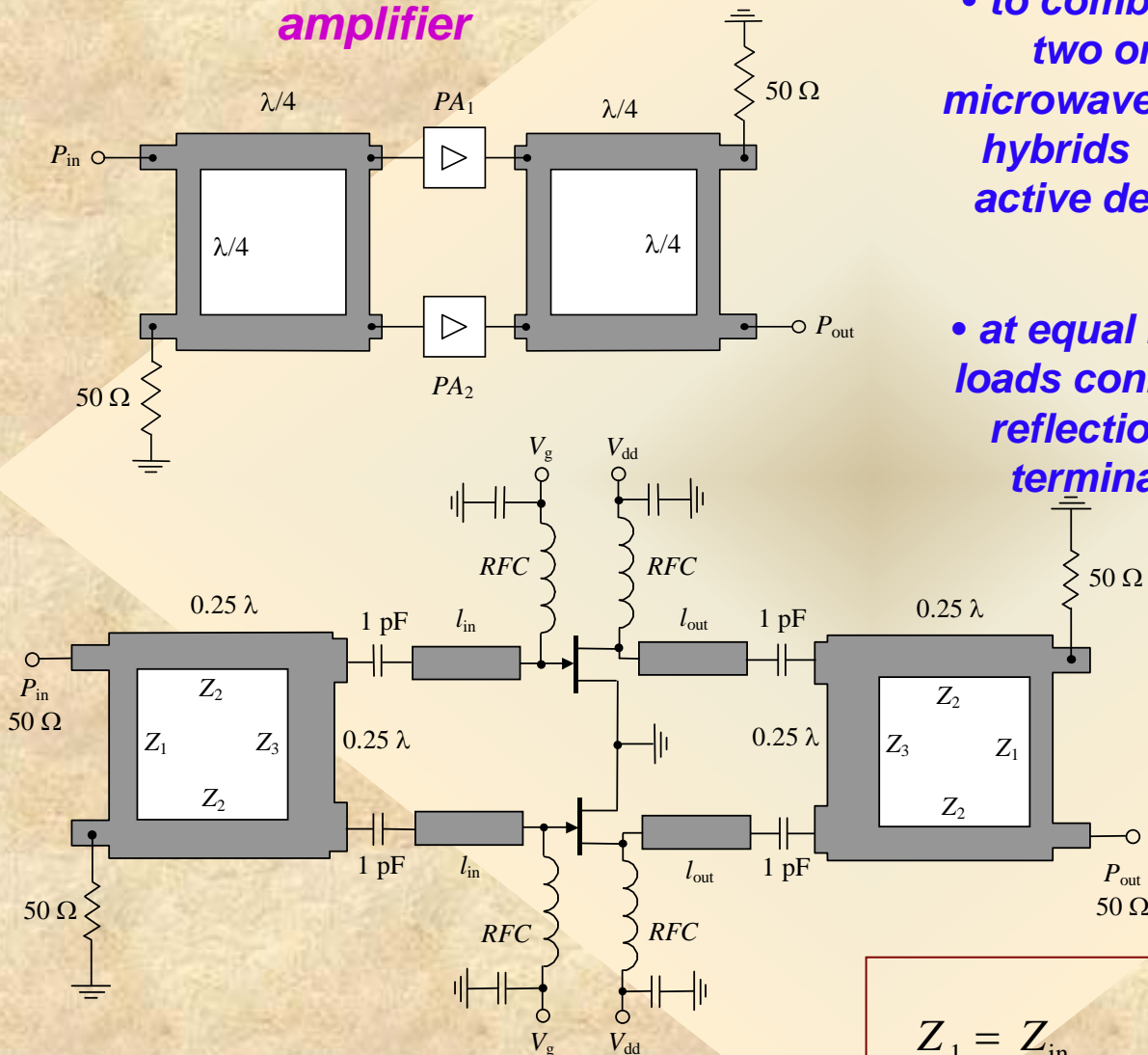
- branch-line hybrid also can work as impedance transformer with characteristic impedances of its microstrip branches as



$$Z_1 = Z_{in} \quad Z_3 = Z_{out} \quad Z_2 = \sqrt{\frac{Z_{in} Z_{out}}{4}}$$

## 3.8. Practical aspect of RF and microwave power amplifiers
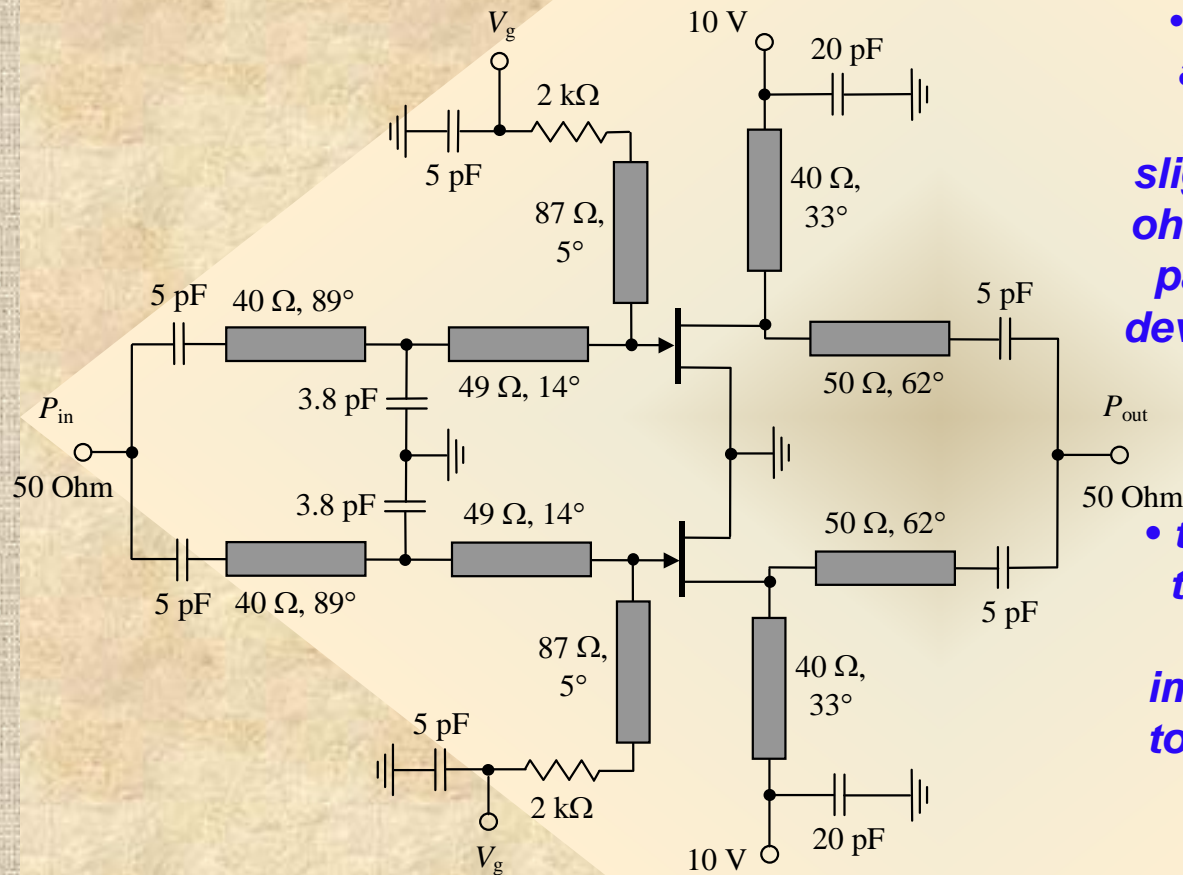
### Microwave 5.5 GHz 2.5 W GaAs MESFET power amplifier topology



- for monolithic microwave applications, when output resistance of transistor is slightly less or higher than 50-ohm, it is convenient to realize parallel connection of active devices (easy to provide circuit symmetry for packaged devices)

- to combine power from two transistors, it is necessary simply to transform impedance from each device to 100 Ohm and then parallel connection results in required 50-ohm load

- input matching circuits represent quarterwave microstrip line transformer and L-transformer with series microstrip line and parallel capacitance each