

Exercise 4.1:

$$OUT = IN1 + \overline{IN2 \cdot IN3}$$

IN1	IN2	IN3	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


De Morgan's Theorem
 $\overline{X+Y} = \overline{X} \cdot \overline{Y}$

$$OUT = \overline{IN1 + \overline{IN2 \cdot IN3}}$$


$$OUT = \overline{IN1} \cdot \overline{IN2 \cdot IN3}$$

$$OUT = \overline{IN1} \cdot \overline{IN2} \cdot \overline{IN3}$$

Using logic symbols:

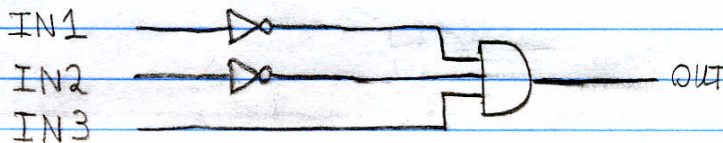

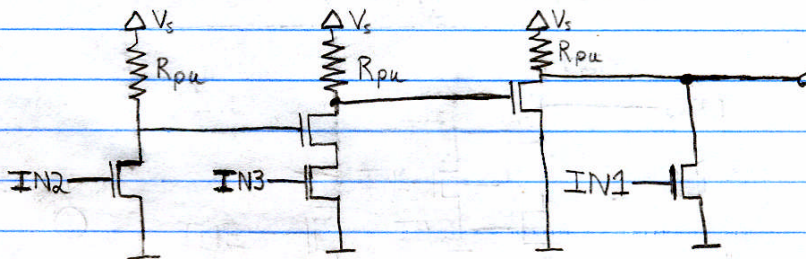
Using n-channel MOSFETs and pull-up resistors: (One of many possible ccts)



6.002 Pset 4
Solutions

Pg. 2

Exercise 4.2:

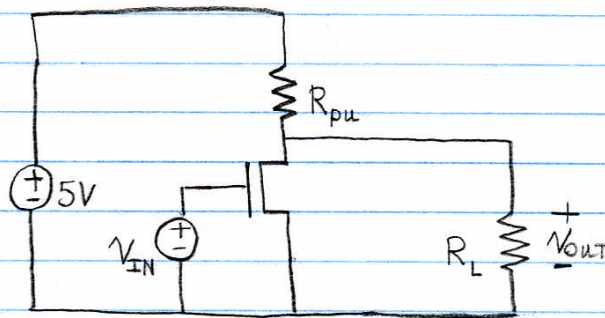

$$R_L \geq 8 \text{ M}\Omega$$


$$V_{OL} = 1 \text{ V}, V_{IL} = 2 \text{ V}$$

$$V_{IH} = 3 \text{ V}, V_{OH} = 4 \text{ V}$$

$$V_{IL} < V_T < V_{IH}$$

$$\underline{2 < V_T < 3}$$

$$V_{IN} < V_T$$

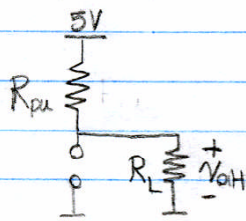

$$V_{OH} = 4 < \frac{R_L}{R_{pu} + R_L} (5 \text{ V})$$

$$\frac{R_L}{R_{pu} + R_L} > \frac{4}{5} = 0.8$$

$$R_L > 0.8(R_{pu} + R_L)$$

$$0.2 R_L > 0.8 R_{pu}$$

$$R_L > 4 R_{pu} \Rightarrow R_{pu} < \frac{1}{4} R_L$$

Given: $R_L \geq 8 \text{ M}\Omega$


$$\Rightarrow R_{pu} \leq 2 \text{ M}\Omega$$

Need to minimize power dissipation so must maximize the resistance

$$P = \frac{V^2}{R} = \frac{(5)^2}{R_{pu} + R_L}$$

$$\Rightarrow \underline{R_{pu} = 2 \text{ M}\Omega}$$

$$V_{IN} > V_T$$

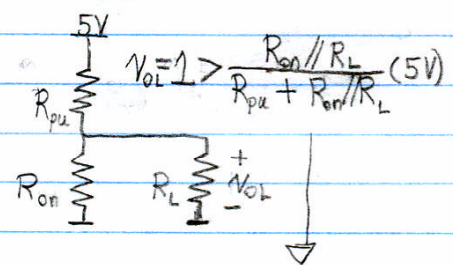

$$\frac{R_{on} // R_L}{R_{pu} + R_{on} // R_L} < \frac{1}{5} = 0.2$$

$$R_{on} // R_L < 0.2(R_{pu} + R_{on} // R_L)$$

$$0.8 R_{on} // R_L < 0.2 R_{pu}$$

$$R_{on} // R_L < \frac{1}{4} R_{pu}$$

$$R_{on} // R_L < 0.5 \text{ M}\Omega$$

$$\frac{R_{on} R_L}{R_{on} + R_L} < 0.5 \text{ M}\Omega$$

$$R_{on} R_L < 0.5 \text{ M}\Omega (R_{on} + R_L)$$

$$R_{on} < 0.5 \text{ M}\Omega \left(\frac{R_{on}}{R_L} + 1 \right)$$


Worst case: $R_L \rightarrow \infty$

$$\Rightarrow R_{on} < 0.5 \text{ M}\Omega$$

$$P = \frac{V^2}{R} = \frac{(5)^2}{R_{pu} + R_{on} // R_L}$$

$$\Rightarrow \underline{R_{on} = 0.5 \text{ M}\Omega}$$

Problem 4.1:

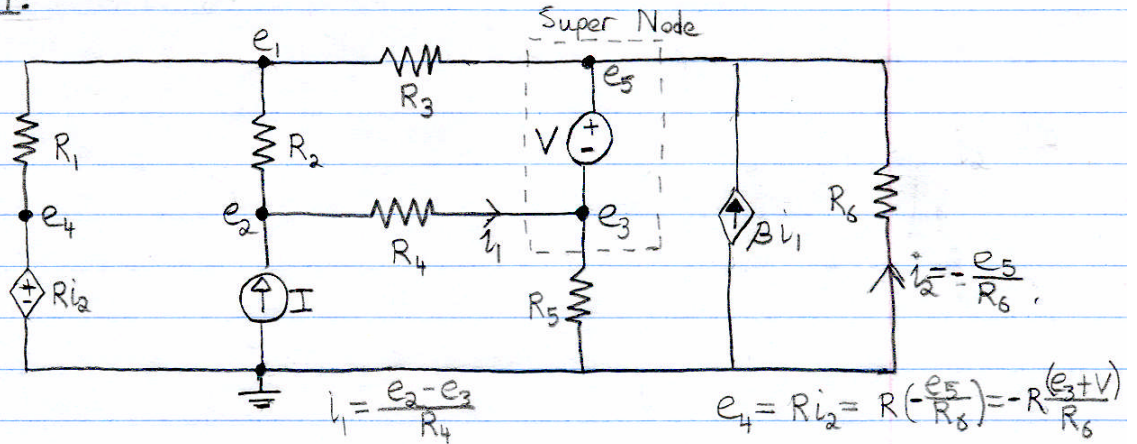

KCL @ e_1 :

$$\frac{e_1 - e_4}{R_1} + \frac{e_1 - e_2}{R_2} + \frac{e_1 - e_5}{R_3} = 0$$

$$e_5 = e_3 + V$$

$$\frac{e_1 + \frac{R}{R_6}(e_3 + V)}{R_1} + \frac{e_1 - e_2}{R_2} + \frac{e_1 - e_3 - V}{R_3} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) e_1 - \frac{1}{R_2} e_2 + \left(\frac{R}{R_1 R_6} - \frac{1}{R_3} \right) e_3 = - \left(\frac{R}{R_1 R_6} - \frac{1}{R_3} \right) V$$

KCL @ e_2 :

$$\frac{e_2 - e_1}{R_2} + \frac{e_2 - e_3}{R_4} = I$$

$$-\frac{1}{R_2} e_1 + \left(\frac{1}{R_2} + \frac{1}{R_4} \right) e_2 - \frac{1}{R_4} e_3 = I$$

KCL @ e_3 :

$$\frac{e_3 - e_2}{R_4} + \frac{e_3}{R_5} + \frac{e_5 - e_1}{R_3} + \frac{e_5}{R_6} - \beta i_1 = 0$$

$$\frac{e_3 - e_2}{R_4} + \frac{e_3}{R_5} + \frac{e_3 + V - e_1}{R_3} + \frac{e_3 + V}{R_6} - \beta \frac{(e_2 - e_3)}{R_4} = 0$$

$$-\frac{1}{R_3} e_1 - \left(\frac{1}{R_4} + \frac{\beta}{R_4} \right) e_2 + \left(\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_6} + \frac{\beta}{R_4} \right) e_3 = - \left(\frac{1}{R_3} + \frac{1}{R_6} \right) V$$

6.002 Pset 4
Solutions

pg. 4


Problem 4.1: (Continued)

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} & \frac{R}{RR_6} - \frac{1}{R_3} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_3} & -\left(\frac{1}{R_4} + \frac{R}{R_4}\right) & \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_6} + \frac{R}{R_4} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{R_3} - \frac{R}{R_1 R_6}\right)V \\ I \\ -\left(\frac{1}{R_3} + \frac{1}{R_6}\right)V \end{bmatrix}$$


$$e_4 = -\frac{R}{R_6}(e_3 + V)$$

Problem 4.2:

Ⓐ Left ckt.:

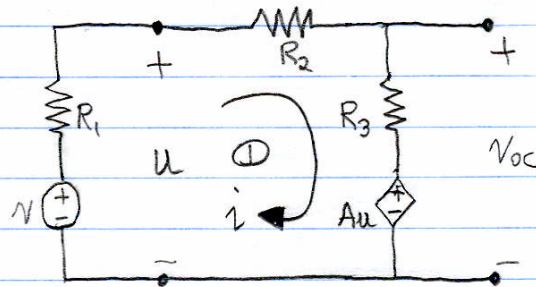

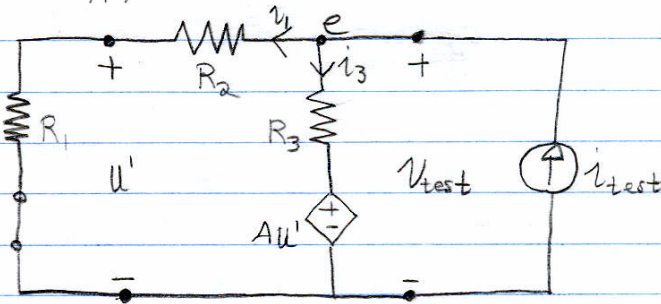Turn off sources and apply a test current to find R_{th} :



$$R_{TH} = \frac{V_{test}}{i_{test}}$$

KCL @ node e:

$$e = V_{test}$$

$$\frac{e}{R_1 + R_2} + \frac{e - Au'}{R_3} = i_{test}$$

$$u' = i_1 R_1 = \frac{V_{test}}{R_1 + R_2} R_1$$

$$\frac{V_{test}}{R_1 + R_2} + \frac{V_{test}}{R_3} - \frac{AR_1 V_{test}}{R_3(R_1 + R_2)} = i_{test}$$

$$\left[\frac{1}{R_1 + R_2} + \frac{1}{R_3} - \frac{AR_1}{R_3(R_1 + R_2)} \right] V_{test} = i_{test}$$

$$R_{th} = \frac{V_{test}}{i_{test}} = \frac{R_3(R_1 + R_2)}{R_3 + R_1 + R_2 - AR_1}$$

KVL around loop ⓐ:

$$V = R_1 i + R_2 i + R_3 i + Au \quad \text{where } u = V - R_1 i$$

$$V = R_1 i + R_2 i + R_3 i + AV - AR_1 i$$

$$(R_1 + R_2 + R_3 - AR_1) i = (1 - A)V$$

$$i = \frac{(1 - A)V}{(1 - A)R_1 + R_2 + R_3}$$

Problem 4.2: (Continued)

Calculate $V_{th} = V_{oc}$:

$$\begin{aligned} V_{oc} &= Au + iR_3 \\ &= AV - AR_1i + iR_3 \\ &= AV - (AR_1 - R_3)i \end{aligned}$$


$$= AV - \frac{(AR_1 - R_3)(1-A)V}{(1-A)R_1 + R_2 + R_3}$$

$$= \frac{[(1-A)R_1 + R_2 + R_3]AV - (AR_1 - R_3)(1-A)V}{(1-A)R_1 + R_2 + R_3}$$


$$= \frac{ACI - AR_1V + AR_2V + AR_3V - A(1-A)R_1V + R_3V - AR_3V}{(1-A)R_1 + R_2 + R_3}$$

$$V_{th} = V_{oc} = \frac{(AR_2 + R_3)V}{(1-A)R_1 + R_2 + R_3}$$

③ Right cct.:

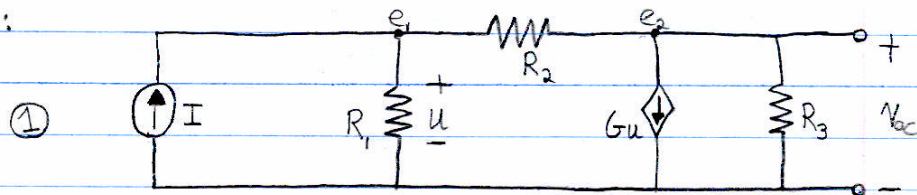

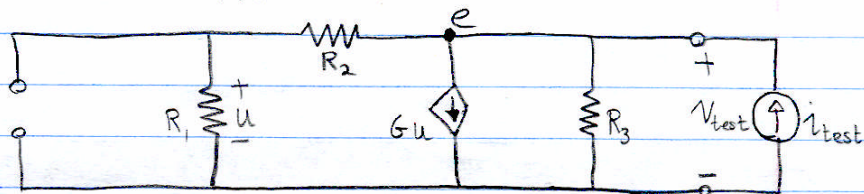Turn off sources and apply a test current to find R_{th} :



$$R_{TH} = \frac{V_{test}}{i_{test}}$$

KCL @ node e:

$$\frac{e}{R_1 + R_2} + Gu + \frac{e}{R_3} = i_{test}$$

$$\begin{aligned} e &= V_{test} \\ u &= \frac{R_1}{R_1 + R_2} e \end{aligned}$$

$$\frac{V_{test}}{R_1 + R_2} + \frac{GR_1 V_{test}}{R_1 + R_2} + \frac{V_{test}}{R_3} = i_{test}$$

$$\left[\frac{1 + GR_1}{R_1 + R_2} + \frac{1}{R_3} \right] V_{test} = i_{test}$$

Problem 4.2: (Continued)

$$R_{TH} = \frac{V_{test}}{I_{test}} = \frac{(R_1 + R_2)R_3}{(1 + GR_1)R_3 + R_1 + R_2}$$

Calculate $V_{th} = V_{oc}$:

KCL @ node e_1 in ckt ①:

$$\frac{e_1}{R_1} + \frac{e_1 - e_2}{R_2} = I$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)e_1 - \frac{1}{R_2}e_2 = I$$

$$\frac{R_1 + R_2}{R_1 R_2} e_1 = I + \frac{e_2}{R_2}$$

$$e_1 = \frac{R_1 R_2}{R_1 + R_2} \left[I + \frac{e_2}{R_2} \right]$$

KCL @ node e_2 in ckt ①:

$$\frac{e_2 - e_1}{R_2} + Gu + \frac{e_2}{R_3} = 0$$

$$u = e_1$$

$$\left[\frac{1}{R_2} + \frac{1}{R_3}\right]e_2 + \left[G - \frac{1}{R_2}\right]e_1 = 0$$

$$\left[\frac{R_2 + R_3}{R_2 R_3}\right]e_2 + \left[G - \frac{1}{R_2}\right]\left[\frac{R_1 R_2}{R_1 + R_2}\right]\left[I + \frac{e_2}{R_2}\right] = 0$$


$$\left[\frac{R_2 + R_3}{R_2 R_3} + \left[G - \frac{1}{R_2}\right]\left[\frac{R_1 R_2}{R_1 + R_2}\right]\frac{1}{R_2}\right]e_2 = -\left[G - \frac{1}{R_2}\right]\left[\frac{R_1 R_2}{R_1 + R_2}\right]I$$

$$V_{TH} = V_{oc} = e_2 = \frac{\left[\frac{1}{R_2} - G\right]\left[\frac{R_1 R_2}{R_1 + R_2}\right]I}{\frac{R_2 + R_3}{R_2 R_3} + \left[G - \frac{1}{R_2}\right]\left[\frac{R_1 R_2}{R_1 + R_2}\right]\frac{1}{R_2}}$$

Problem 4.3:

(a) See page 9.

(b)

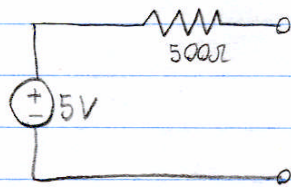

Looks like Thevenin equivalent circuit where

$$V_{TH} = 5V$$

$$R_{TH} = 500\Omega$$

$$I_N = \frac{5}{500} = 0.01A$$

See page 9 for $V_{DS} - I_D$ load line.


Table of resulting input-output relations:


$V_{IN} = V_{GS}(V)$	2.50	2.45	2.40	2.35	2.30	2.25	2.20	2.15	2.10
$V_{OUT} = V_{DS}(V)$	0.40	1.35	2.35	3.20	3.75	4.20	4.50	4.70	4.80

(c) See page 10.

(d) See page 10. The input-output relations found in Part (B) and (C) are identical, as expected.


Problem 4.3(a) & (b):

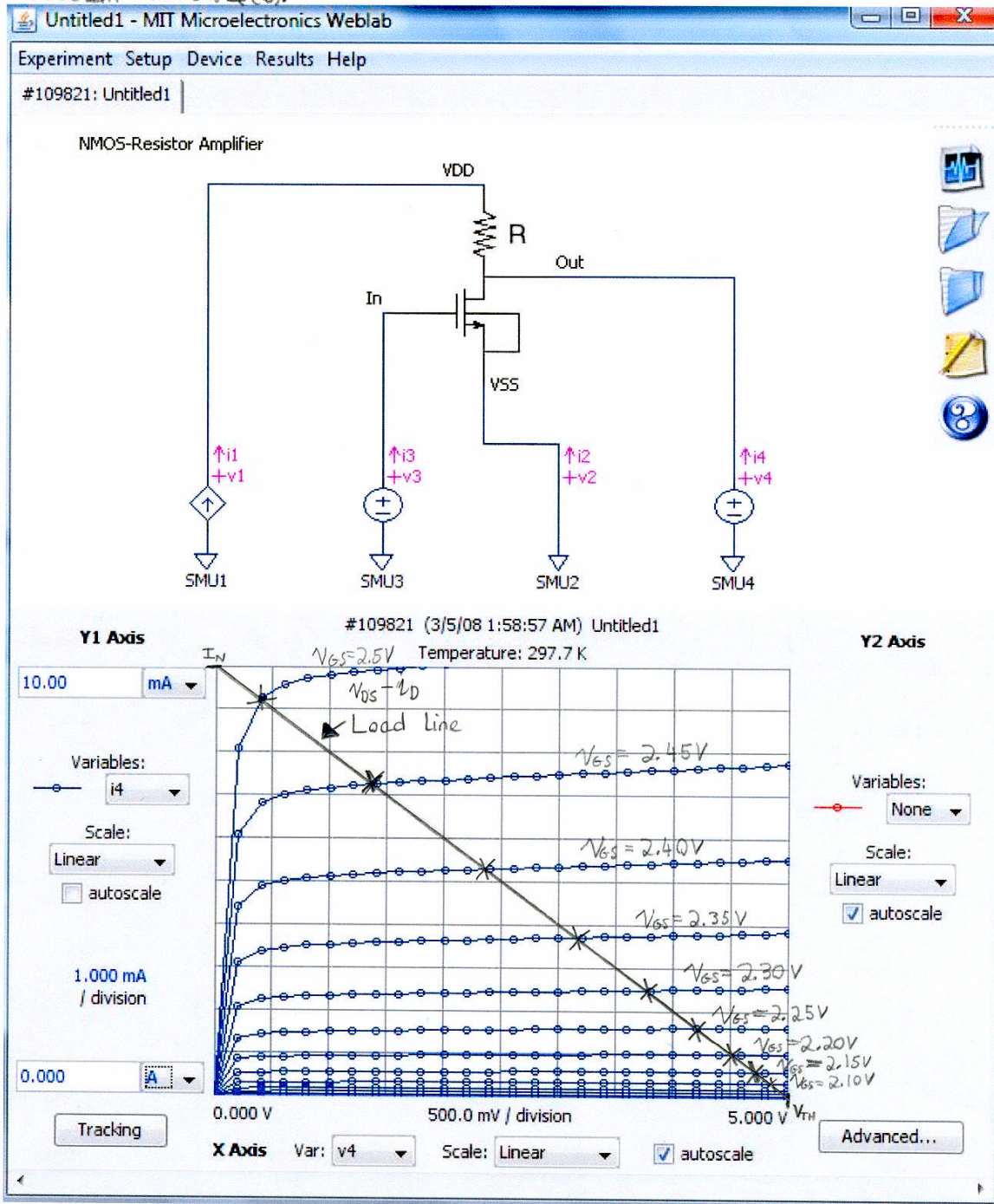

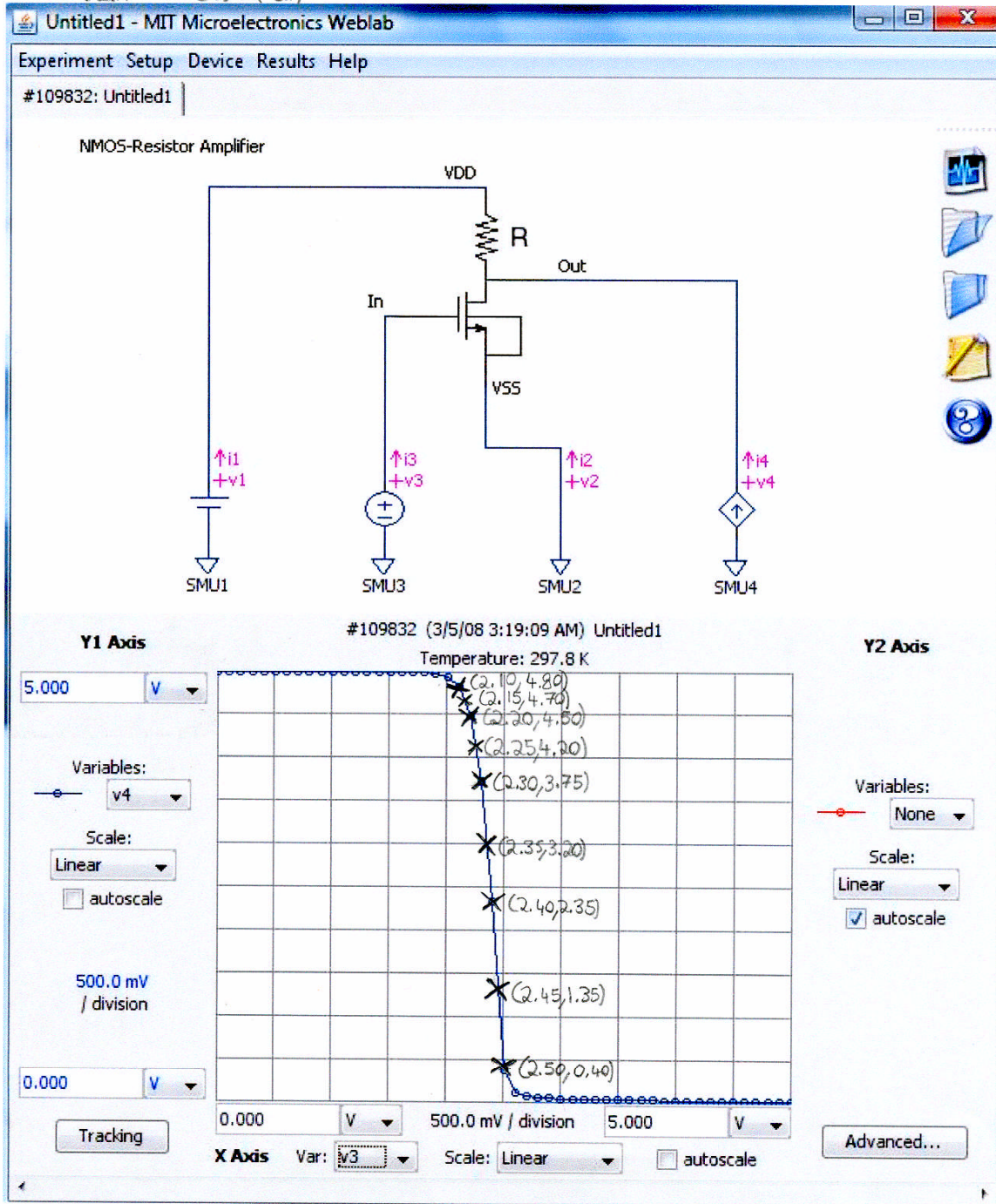


Problem 4.4:

Given =

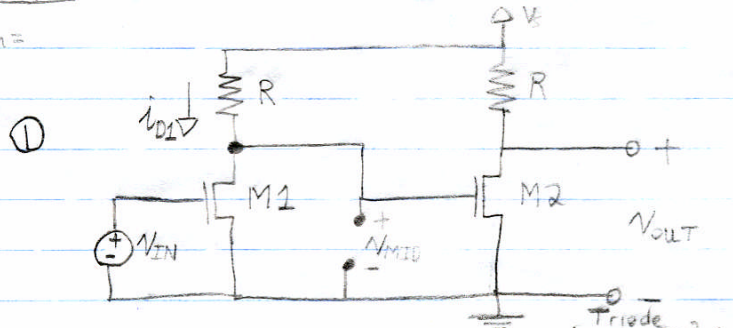

②

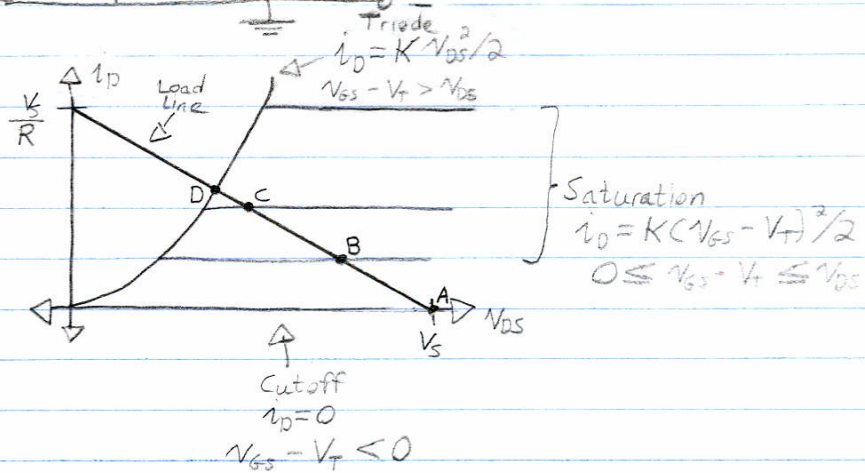

(a) M1 will be in cutoff when $V_{IN} < V_T$. In this range $i_{D1} = 0$ so $V_{DS1} = V_{MID} = V_S$

(b) Assuming M1 in saturation ($V_{IN} > V_T$) then a current i_{D1} will be flowing through pull-up resistor and M1. So $V_{MID} = V_S - i_{D1}R$ where $i_{D1} = \frac{K}{2}(V_{IN} - V_T)^2$ (M1 in saturation)
 $\Rightarrow V_{MID} = V_S - \frac{RK}{2}(V_{IN} - V_T)^2$

To determine the range of V_{MID} and the range of V_{IN} that correspond to the saturated operation of M1 need to perform load line analysis, see load line on figure ② above. At point A M1 is in cutoff, As $V_{IN} = V_{GS1}$ is increased, it moves up the load line into saturation (point B). It will remain in saturation as V_{IN} is increased a bit more (point C), until it hits

6.002 Pset 4
Solutions

pg. 12

Problem 4.4: (Continued)

(B) the triode boundary (point D). So to find ranges of V_{IN} , V_{MID} of saturation need to find point D.

Can find point D by equating load line to triode/saturation boundary:

$$i_{D1} = \frac{k}{2} V_{MID,D}^2 = \frac{V_S}{R} - \frac{V_{MID,D}}{R}$$

$$\frac{k}{2} V_{MID,D}^2 + \frac{V_{MID,D}}{R} - \frac{V_S}{R} = 0 \quad \leftarrow \text{Quadratic Equation}$$

$$V_{MID,D} = \frac{-\left(\frac{1}{R}\right) \pm \sqrt{\left(\frac{1}{R}\right)^2 - 4\left(\frac{k}{2}\right)\left(-\frac{V_S}{R}\right)}}{2\left(\frac{k}{2}\right)}$$

$$\begin{aligned} a &= \frac{k}{2} \\ b &= \frac{1}{R} \\ c &= -\frac{V_S}{R} \end{aligned}$$

$$V_{MID,D} = \frac{1}{RK} (-1 + \sqrt{1 + 2RK V_S})$$

Pick positive solution ($V_{MID,D}$ is positive)
This is lower bound for V_{MID} to still be in saturation.

The corresponding $V_{IN,D}$ can be found at the triode/saturation boundary:

$$V_{GS} - V_T = V_{DS} = V_{MID,D}$$

$$V_{IN,D} - V_T = V_{MID,D}$$

$$V_{IN,D} = V_{MID,D} + V_T$$

Max V_{IN} can go is V_T above $V_{MID,D}$

The other boundary to saturation is cutoff: $V_{IN} > V_T$.
Therefore the ranges of V_{MID} and V_{IN} in saturation:

$$\frac{1}{RK} (\sqrt{1 + 2RK V_S} - 1) \leq V_{MID} \leq V_S$$

$$V_T \leq V_{IN} \leq \frac{1}{RK} (\sqrt{1 + 2RK V_S} - 1) + V_T$$

Problem 4.4: (Continued)

(C) If V_{IN} is increased beyond limits stated in part B then the operating point stays at point D. It can't go up along triode curve because it must intersect with load line. Thus for $V_{IN} \geq \frac{1}{RK}(\sqrt{1+2RKV_S} - 1) + V_T$
 $V_{MID} = V_{MID0} = \frac{1}{RK}(\sqrt{1+2RKV_S} - 1)$

(D) In the case of M2 ($V_{GS2} = V_{MID}$ (output of M1 is input of M2)). Since R's and MOSFETs are identical the V_{out} and V_{MID} relationship is the same as that of V_{MID} and V_{IN} .

M2 in cutoff: $V_{MID} < V_T$, $V_{out} = V_S$

M2 in saturation: $V_T \leq V_{MID} \leq \frac{1}{RK}(\sqrt{1+2RKV_S} - 1) + V_T$
 $\frac{1}{RK}(\sqrt{1+2RKV_S} - 1) \leq V_{out} \leq V_S$

M2 in triode: $V_{MID} \geq \frac{1}{RK}(\sqrt{1+2RKV_S} - 1) + V_T$
 $V_{out} = \frac{1}{RK}(\sqrt{1+2RKV_S} - 1)$

(E) Assuming that both M1 and M2 operate in saturation. From part B and D it is possible to determine V_{out} as a function of V_{IN} :

From part D: $V_{out} = V_S - \frac{RK}{2}(V_{MID} - V_T)^2$

From part B: $V_{MID} = V_S - \frac{RK}{2}(V_{IN} - V_T)^2$

$$\Rightarrow V_{out} = V_S - \frac{RK}{2}\left(V_S - \frac{RK}{2}(V_{IN} - V_T)^2 - V_T\right)^2$$

Problem 4.4: (Continued)

(E) To find the range of V_{MID} :

From part B: $\frac{1}{RK} (\sqrt{1+2RKV_S} - 1) \leq V_{MID} \leq V_S$

From part D: $V_T \leq V_{MID} \leq \frac{1}{RK} (\sqrt{1+2RKV_S} - 1) + V_T$

$$\Rightarrow \text{MAX} \left\{ V_T, \frac{1}{RK} (\sqrt{1+2RKV_S} - 1) \right\} \leq V_{MID} \leq \text{MIN} \left\{ V_S, \left(\frac{1}{RK} (\sqrt{1+2RKV_S} - 1) + V_T \right) \right\}$$

To find the range of V_{IN} :

From part B: $V_{MID} = V_S - \frac{RK}{2} (V_{IN} - V_T)^2$

$$(V_{IN} - V_T)^2 = \frac{2}{RK} (V_S - V_{MID})$$

$$\Rightarrow V_{IN} = V_T + \sqrt{\frac{2}{RK} (V_S - V_{MID})}$$

$$\begin{aligned} V_{MID,MIN} &\rightarrow V_{IN,MAX} \\ V_{MID,MAX} &\rightarrow V_{IN,MIN} \end{aligned}$$

$$V_{IN,MIN} \leq V_{IN} \leq V_{IN,MAX}$$

where $V_{IN,MIN} = V_T + \sqrt{\frac{2}{RK} (V_S - \text{MIN} \left\{ V_S, \left(\frac{1}{RK} (\sqrt{1+2RKV_S} - 1) + V_T \right) \right\})}$

$$V_{IN,MAX} = V_T + \sqrt{\frac{2}{RK} (V_S - \text{MAX} \left\{ V_T, \left(\frac{1}{RK} (\sqrt{1+2RKV_S} - 1) \right) \right\})}$$

(F) To find the small-signal gain = $\frac{dV_{OUT}}{dV_{IN}}$:

From part E: $V_{OUT} = V_S - \frac{RK}{2} \left(V_S - \frac{RK}{2} (V_{IN} - V_T)^2 - V_T \right)^2$

$$\frac{dV_{OUT}}{dV_{IN}} = -\frac{RK}{2} \left(2 \left(V_S - \frac{RK}{2} (V_{IN} - V_T)^2 - V_T \right) \cdot \left(-\frac{RK}{2} (2) (V_{IN} - V_T) \right) \right)$$

$$\frac{dV_{OUT}}{dV_{IN}} = (RK)^2 \left(V_S - \frac{RK}{2} (V_{IN} - V_T)^2 - V_T \right) (V_{IN} - V_T)$$

Since: $V_{MID} = V_S - \frac{RK}{2} (V_{IN} - V_T)^2$

$$\frac{dV_{OUT}}{dV_{IN}} = (RK)^2 (V_{MID} - V_T) (V_{IN} - V_T)$$

Problem 4.4: (Continued)

(G) Let:

$$K = 0.01 \text{ A/V}^2$$

$$R = 2 \text{ k}\Omega$$

$$V_S = 10 \text{ V}$$

$$V_T = 1 \text{ V}$$

$$0 \leq V_{IN} \leq 3 \text{ V}$$

① M1 Cutoff:

$$0 \leq V_{GS} \leq V_T$$

$$0 \leq V_{IN} \leq 1 \quad i_{D1} = 0$$

② M1 Saturation:

$$V_T \leq V_{GS} \leq \frac{1}{RR} (\sqrt{1 + 2RKV_S} - 1) + V_T$$

$$1 \leq V_{IN} \leq \frac{1}{(2000)(0.01)} (\sqrt{1 + 2(2000)(0.01)(10)} - 1) + 1$$

$$1 \leq V_{IN} \leq 1.95 \text{ V}$$

$$i_{D1} = \frac{K}{2} (V_{IN} - V_T)^2$$

$$i_{D1} = 0.005 (V_{IN} - V_T)^2$$

③ M1 Triode:

$$V_{IN} \geq V_{IN,D}$$

$$V_{IN} \geq 1.95 \text{ V}$$

$$i_{D1} = i_{D1,D} = \frac{K}{2} (V_{IN,D} - V_T)^2$$

$$i_{D1} = 0.005 (1.95 - 1)^2 = 4.5 \text{ mA}$$

V_{MID} is obtained from: $V_{MID} = V_S - i_{D1} R$
 Steps ①-③ can be repeated with $V_{IN} = V_{MID}$ to obtain equations for M2.
 A MATLAB script was used to plot V_{MID} and V_{out} versus V_{IN} , which is shown on the next page.

Problem 4.4: (Continued)

(G)

