

6.002 Problem set #5 - Solution

Exercise 5.1

MOSFET in saturation $\therefore V_s > v_{in} - v_{out} - V_T$

$$i_D = \frac{k}{2} (v_{in} - v_{out} - V_T)^2$$

$$v_{out} = R i_D = \frac{KR}{2} (v_{in} - v_{out} - V_T)^2$$

Expanding to solve for v_{out}

$$v_{out} = \frac{KR}{2} \left[(v_{in} - V_T)^2 - 2(v_{in} - V_T)v_{out} + v_{out}^2 \right]$$

$$\frac{KR}{2} v_{out}^2 - [KR(v_{in} - V_T) + 1] v_{out} + \frac{KR}{2} (v_{in} - V_T)^2 = 0$$

Solve using the quadratic formula,

$$v_{out} = \frac{KR(v_{in} - V_T) + 1 \pm \sqrt{2KR(v_{in} - V_T) + 1}}{KR}$$

$$v_{out} = (v_{in} - V_T) + \frac{1}{KR} \pm \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}}$$

For MOSFET in saturation,

$$0 \leq v_{GS} - V_T \leq v_{DS}$$

$$0 \leq v_{in} - v_{out} - V_T \leq V_s \quad (*)$$

$$v_{in} - V_T - V_s \leq v_{out} \leq v_{in} - V_T$$

\Rightarrow We choose the negative sign in the solution for v_{out} above.

$$v_{out} = (v_{in} - V_T) + \frac{1}{KR} - \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}}$$

From (*), $v_{in} \leq v_{out} + V_T + V_s$

$$0 \leq v_{in} - (v_{in} - V_T) + \frac{1}{KR} - \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} - V_T \leq V_s$$

$$\therefore 0 \leq \frac{1}{KR} - \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} \leq V_s$$

For MOSFET to be in saturation.

6.002 Pset 5 Sol'n

Exercise 5.2

$$M1: i_D = \frac{k_1}{2} (v_{in} - V_{T1})^2$$

$$M2: i_D = \frac{k_2}{2} (V_S - v_{out} - V_{T2})^2$$

Because of the circuit configuration, these two currents are equal.

$$\frac{k_1}{2} (v_{in} - V_{T1})^2 = \frac{k_2}{2} (V_S - v_{out} - V_{T2})^2$$

$$\sqrt{\frac{k_1}{k_2}} (v_{in} - V_{T1}) = V_S - v_{out} - V_{T2}$$

$$\therefore v_{out} = -\sqrt{\frac{k_1}{k_2}} (v_{in} - V_{T1}) + V_S - V_{T2}$$

Note that this is more linear than the expression in ES.1

For M1 to be in saturation,

$$0 \leq v_{in} - V_{T1} \leq v_{out}$$

$$\Rightarrow v_{in} \geq V_{T1} \text{ and } v_{in} \leq v_{out} + V_{T1}$$


For M2 to be in saturation,

$$0 \leq V_S - v_{out} - V_{T2} \leq V_S - v_{out}$$

$$\Rightarrow V_S - v_{out} \geq V_{T2} \text{ and } -V_{T2} \leq 0 \text{ (always true)}$$


Recall:

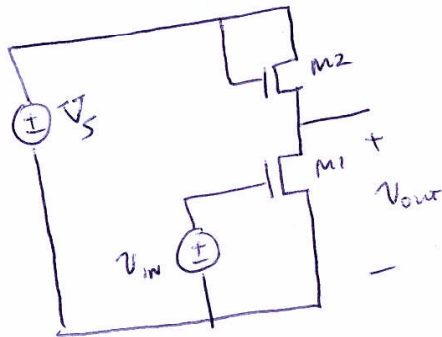In general, M is in saturation if $0 \leq v_{GS} - V_T \leq v_{DS}$.




M2 \Rightarrow "diode-connected" MOSFET, i.e. drain and gate are connected. The condition for M2 to be in saturation is less stringent than for M1 because M2 is diode-connected.

6.002 Pset 5 Sol'n

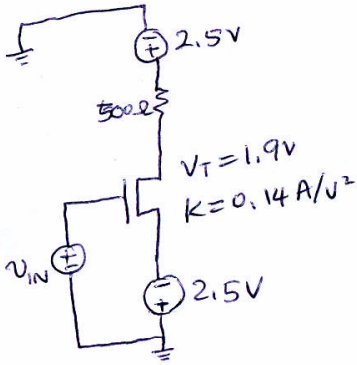


Problem 5.1 (A)

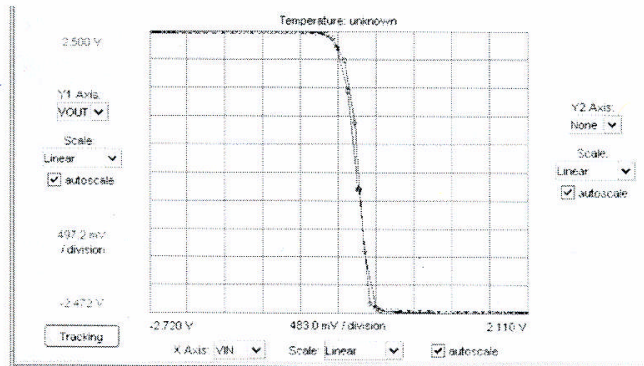

Using Tracking, we measure the input bias voltage of 83 mV which gives V_{out} close to zero.

Problem 5.1 (B)

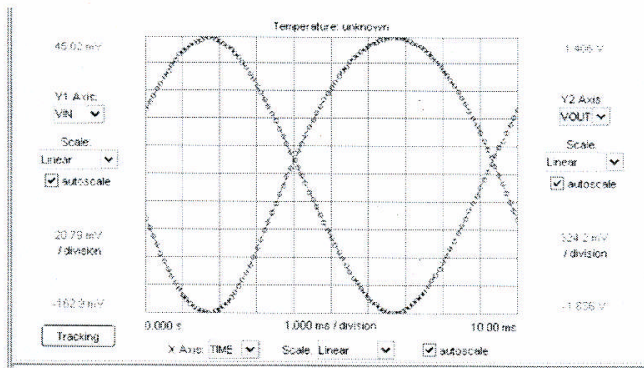

With an offset of 30 mV on the input, we get a small-signal gain of


$$A_{ss} = \frac{-3.242}{208 \text{ m}} = \underline{\underline{-16 \text{ V/V}}}$$

as shown above.

cont'd. on next page. →


6.002 Pset 5 Sol'n

Problem 5.1 (C)

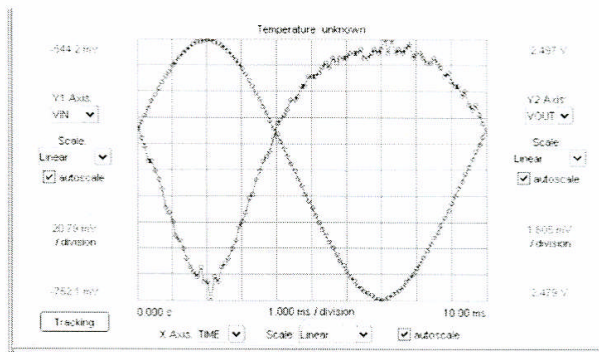

Offset = -0.56V
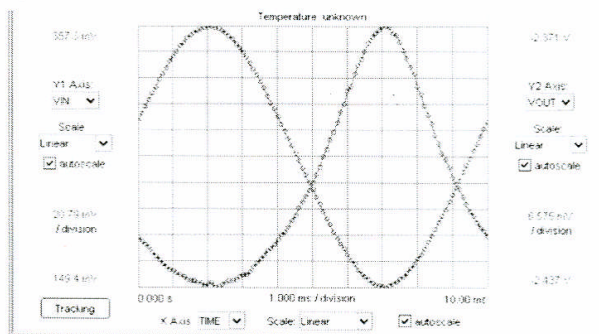
$$A_{SS} = -8.8 \times 10^{-6} \text{ V/V}$$



Offset = 0.34 V

$$A_{SS} = -0.3175 \text{ V/V}$$

For an offset of -0.56V , we notice some distortion and greatly reduced gain. In this case,

$$V_{IN} = -0.56\text{V} \quad \therefore V_{GS} = V_{IN} + 2.5\text{V} = 1.9\text{V}$$

Since $V_T = 1.9\text{V}$, the transistor is in cutoff, so the output current is very low. The distortion is less for the upper-half of the sine wave as expected.

For an offset of 0.34V , the gain is also greatly reduced. In this case

$$V_{IN} = 0.34\text{V} \quad \therefore V_{GS} = V_{IN} + 2.5\text{V} = 2.84\text{V}$$

For saturation, we require,

$$V_{GS} - V_T < V_{DS}$$

but in our case, $V_{GS} - V_T = 2.84 - 1.9 = 0.94\text{V}$ and


$$V_{DS} = V_{OUT} + 2.5 = -2.4\text{V} + 2.5 = 100\text{mV}$$

so the transistor is not in saturation and has entered the triode region of operation

6.002 Pset 5 Sol'n

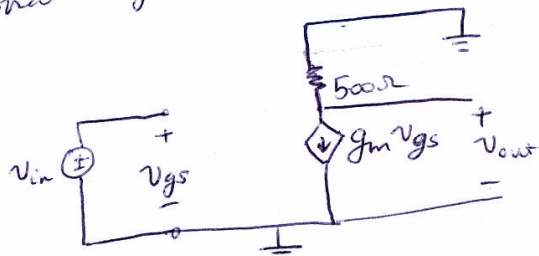Problem 5.1 (D)

Small-signal model of our amplifiers:
We set all voltage sources as short circuits except for the small-signal input.



$$\begin{aligned} \text{Where } g_m &= K(V_{GS} - V_T) \\ &= 0.14(V_{GS} - V_T) \\ &= 0.14(30\text{mV} - (-2.5\text{V}) - 1.9\text{V}) \\ &= 0.084 \text{ A/V} \end{aligned}$$

Small-signal gain given by

$$A_{ss} = \frac{v_{out}}{v_{in}} = \frac{-g_m R v_{gs}}{v_{gs}} = -g_m R$$

$$\therefore A_{ss} = -0.084(500) = \boxed{-42 \text{ V/V}}$$


Note that this is larger than the small-signal gain measured in part (b). The difference is likely due to the fact that k is less than 0.14 A/V which can be seen by measuring the slope of the graph in part (A) and noting that

$$g_m = K(V_{GS} - V_T)$$

From this measurement, we get a value of k closer to 0.05 A/V . Using this value we get an expected gain of 15.75 V/V which is much closer to the value we obtained.

6.002 Pset 5 Sol'n

Problem 5.2

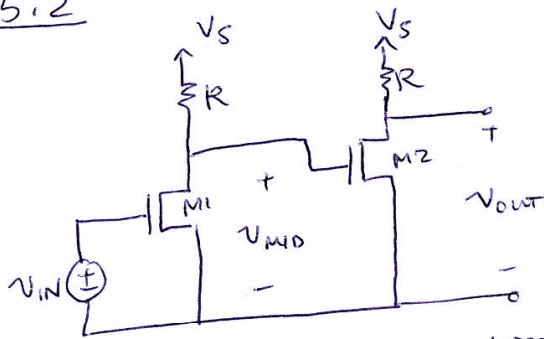


(A) Both MOSFETS are in saturation,

$$v_{M1D} = V_S - i_{D1}R = V_S - \frac{Rk}{2}(v_{IN} - V_T)^2$$

$$i_{D2} = \frac{k}{2}(v_{M1D} - V_T)^2 = \frac{k}{2}\left(V_S - \frac{Rk}{2}(v_{IN} - V_T)^2 - V_T\right)^2$$

$$g_{m2} = \frac{\partial i_{D2}}{\partial v_{M1D}} \Big|_{v_{M1D} = v_{M1D}} = k(v_{M1D} - V_T) = k\left(V_S - \frac{Rk}{2}(v_{IN} - V_T)^2 - V_T\right)$$

$$g_{m1} = \frac{\partial i_{D1}}{\partial v_{IN}} \Big|_{v_{IN} = v_{IN}} = k(v_{IN} - V_T)$$

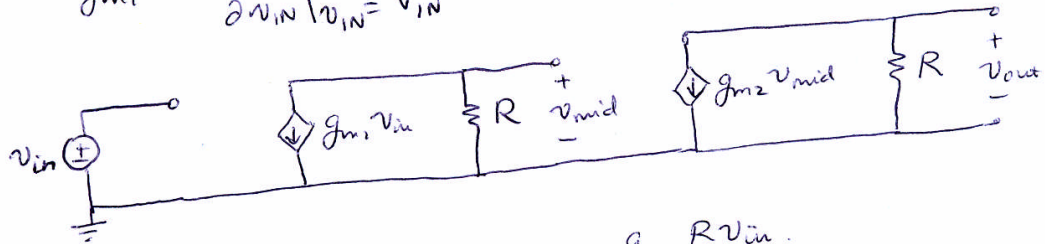


(B) $v_{out} = -g_{m2}R v_{mid}$ $v_{mid} = -g_{m1}R v_{in}$

∴ Small-signal voltage gain:

$$\boxed{\frac{v_{out}}{v_{in}} = g_{m1}g_{m2}R^2}$$


(C) The gain expression given above is identical to that found in problem 4.3.

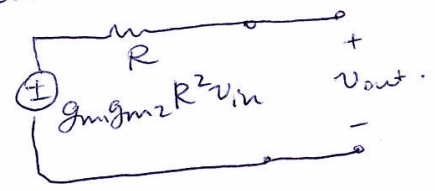(D) To determine the Thevenin resistance, we set all independent sources to zero and find that we get resistor R as shown in the diagram above. The open-circuit voltage was found in (B), so our Thevenin circuit is



6.062 Pset 5 Sol'n

Problem 5.3

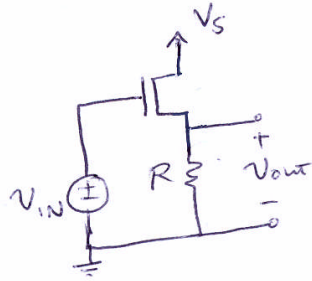

(A) From E5.1,

$$v_{out} = (v_{in} - V_T) + \frac{1}{KR} - \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}}$$

$$\left. \frac{dv_{out}}{dv_{in}} \right|_{v_{in}=V_{in}} = \left| -\frac{1}{2} \left(\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2} \right)^{-1/2} \left(\frac{2}{KR} \right) \right|_{v_{in}=V_{in}}$$

$$\boxed{\frac{v_{out}}{v_{in}} = 1 - \frac{1}{KR \sqrt{\frac{1}{(KR)^2} + \frac{2(v_{in} - V_T)}{KR}}}}$$

(B)



$$v_{gs} = v_{in} - v_{out}$$

$$g_m = K(v_{GS} - V_T)$$

From above,

$$v_{GS} = v_{in} - v_{out}$$

$$= v_{in} - \left[(v_{in} - V_T) + \frac{1}{KR} - \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} \right]$$

$$v_{GS} = V_T - \frac{1}{KR} + \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}}$$

(C) From above, $v_{out} = R g_m v_{gs}$

$$= RK \left(V_T - \frac{1}{KR} + \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} - V_T \right) (v_{in} - v_{out})$$

$$v_{out} \left(1 - 1 + RK \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} \right) = \left(-1 + RK \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}} \right) v_{in}$$


$$\boxed{\frac{v_{out}}{v_{in}} = 1 - \frac{1}{RK \sqrt{\frac{2(v_{in} - V_T)}{KR} + \frac{1}{(KR)^2}}}}$$

same as that found in part (B).

6.002 Pset 5 Sol'n

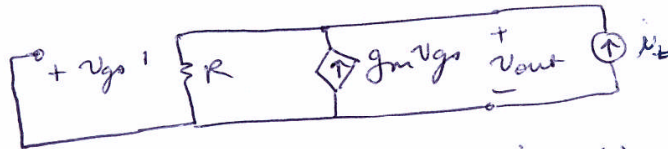Problem 5.3 (D)

To find the Thevenin resistance, we set all independent sources to zero, making v_{in} a short circuit.



Node @ v_{out} : $\frac{v_{out}}{R} = g_m v_{gs} + i_{L_t}$ (1)

$v_{gs} = 0 - v_{out} = -v_{out}$

Substitute into (1), $v_{out} \left(\frac{1}{R} + g_m \right) = i_{L_t}$

$$\frac{v_{out}}{i_{L_t}} = \frac{R}{1 + Rg_m} = R_{Th}$$

From Part (C), a simpler expression for the small-signal gain can be found from

$v_{out} = g_m R v_{gs}$ (1)


$v_{gs} = v_{in} - v_{out} \Rightarrow$ substitute into (1)

$v_{out} (1 + g_m R) = g_m R v_{in} \Rightarrow \frac{v_{out}}{v_{in}} = \frac{g_m R}{1 + g_m R} \approx 1$

assuming $g_m R \gg 1$.

This derivation for the small-signal gain explains the name "source-follower" for this amplifier configuration i.e. the source follows the gate.

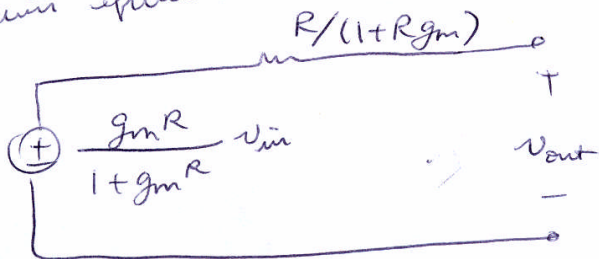
The Thevenin equivalent small-signal circuit is:



6.002 PSet 5 - Sol'n

Problem 5.4

(A)

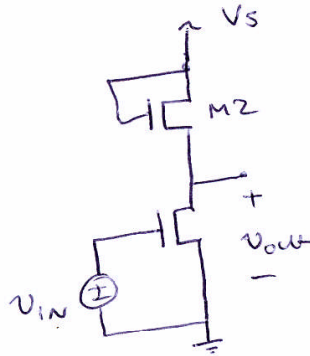


From E5.2, $v_{out} = -\sqrt{\frac{k_1}{k_2}} (v_{in} - V_{T1}) + V_S - V_{T2}$


$$\frac{v_{out}}{v_{in}} = \left. \frac{dv_{out}}{dv_{in}} \right|_{v_{in}=V_{in}} = -\sqrt{\frac{k_1}{k_2}}$$

small-signal voltage gain.


(B) M2:

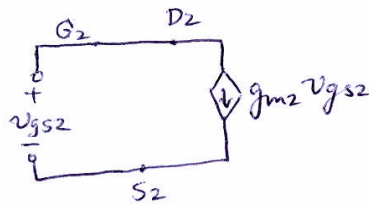

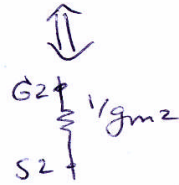Since M2 is connected so that the current through G_{S2} is directly proportional to the voltage across these terminals, it looks like a resistor $1/g_{m2}$.



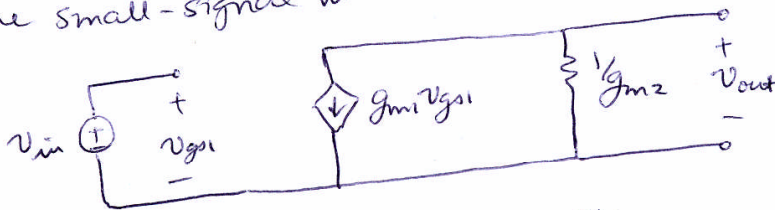∴ The small-signal model of the amplifier reduces to



$$g_{m1} = k_1 (V_{in} - V_{T1})$$

$$g_{m2} = k_2 (V_S - V_{out} - V_{T2})$$

(C) $v_{out} = -g_{m1} \left(\frac{1}{g_{m2}} \right) v_{gs1} \Rightarrow v_{gs1} = v_{in}$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{-g_{m1}}{g_{m2}} = \frac{-k_1 (V_{in} - V_{T1})}{k_2 (V_S - V_{out} - V_{T2})}$$

cont'd. on next page

6.002 Pset 5 Sol'n

Problem 5.4 cont'd.


(C) Substituting v_{out} from E5.2, we have

$$\frac{v_{out}}{v_{in}} = \frac{-k_1 (V_{IN} - V_{T1})}{k_2 \left[V_S - \left(-\sqrt{\frac{k_1}{k_2}} (V_{IN} - V_{T1}) + V_S - V_{T2} \right) - V_{T2} \right]}$$

$$\boxed{\frac{v_{out}}{v_{in}} = -\sqrt{\frac{k_1}{k_2}}}$$

as found in part (A).

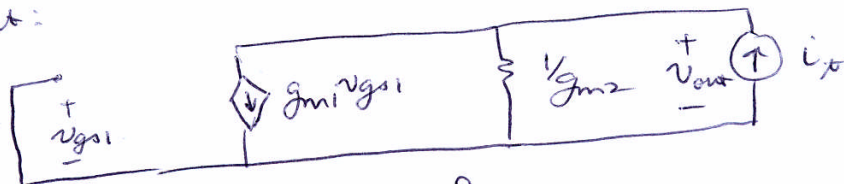(D) To find Thevenin resistance, we set the independent input source to zero and apply a test source at the output:



Since $v_{gs1} = 0$, $g_{m1} v_{gs1} = 0$.

$$\therefore R_{TH} = \frac{v_{out}}{i_x} = \frac{1}{g_{m2}}$$

The Thevenin small-signal circuit for our amplifier is

