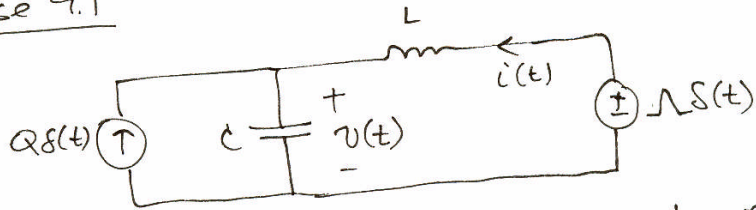


6.002 Problem Set #9 - Solutions

Exercise 9.1



Since the current through L does not want to change instantaneously, the impulse $Q\delta(t)$ in current will appear across the capacitor as

$$v(0^+) = \frac{1}{C} \int_{0^-}^{0^+} Q\delta(t) dt + V = \frac{Q}{C} + V.$$

Since the voltage across the capacitor does not want to change instantaneously, the impulse $I\delta(t)$ in voltage will appear across the inductor,

$$i(0^+) = \frac{1}{L} \int_{0^-}^{0^+} I\delta(t) dt + I = \frac{I}{L} + I.$$

The system will oscillate at $\omega_0 = \frac{1}{\sqrt{LC}}$ rad/s.

$$v_1(t) = \left(\frac{Q}{C} + V\right) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_1(t) = C \frac{dv_1}{dt} = -C \left(\frac{Q}{C} + V\right) \frac{1}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

v_1 and i_1 are the responses due to $Q\delta(t)$ and $v(0) = V$.

$$v_2(t) = \left(\frac{I}{L} + I\right) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$v_2(t) = -L \frac{di_2}{dt} = -L \left(\frac{I}{L} + I\right) \left(-\frac{1}{\sqrt{LC}}\right) \sin\left(\frac{t}{\sqrt{LC}}\right).$$

$$v(t) = v_1(t) + v_2(t) = \left(\frac{Q}{C} + V\right) \cos\left(\frac{t}{\sqrt{LC}}\right) + \sqrt{\frac{L}{C}} \left(\frac{I}{L} + I\right) \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$i(t) = i_1(t) + i_2(t) = \left(\frac{I}{L} + I\right) \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} \left(\frac{Q}{C} + V\right) \sin\left(\frac{t}{\sqrt{LC}}\right)$$

6.002 Pset 9 - Solus

Exercise 9.2

$$R = 600 \Omega$$

$$\text{From KCL: } C \frac{dv}{dt} + \frac{v}{R} + \frac{1}{L} \int v dt = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad 2\alpha = \frac{1}{RC} \Rightarrow \alpha = \frac{1}{2RC}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{\frac{1}{LC} - \frac{1}{4(RC)^2}}$$

From the given response (see Appendix I), we measure

$$f_d = \frac{1}{0.62 \text{ ms}} = 1.61 \text{ kHz} \Rightarrow \omega_d = 2\pi f_d \quad \therefore \omega_d = 10.13 \text{ kHz}$$

$$\frac{1}{\alpha} = 1.2 \text{ ms}$$

$$1.2 \text{ ms} = 2RC \Rightarrow \boxed{C = 1 \mu\text{F}}$$

$$10.13 \text{ k} = \sqrt{\frac{1}{LC} - \frac{1}{4(RC)^2}}$$

$$10.13 \text{ k} = \sqrt{\frac{1}{L(\mu)} - \frac{1}{(1.2 \text{ m})^2}}$$

$$\frac{1}{L(\mu)} = 102.6 \text{ M} + 694.4 \text{ k} \Rightarrow \boxed{L = 9.7 \text{ mH}}$$

6.002 Pset 9 - Solus

Problem 9.1

(A) 1) $v_{in} = \text{Im} \{ V_{in} e^{j\omega t} \}$ $v_{out} = \text{Im} \{ \hat{V}_{out} e^{j\omega t} \}$

2) $v_{in} = L \frac{di}{dt} + iR + v_{out}$

$$i = \frac{v_{out}}{R_M} = \frac{v_{out}}{100}$$

$$\frac{L}{R_M} \frac{dv_{out}}{dt} + \frac{R}{R_M} v_{out} + v_{out} = v_{in}$$

$$\boxed{\frac{dv_{out}}{dt} + \frac{R+R_M}{L} v_{out} = \frac{R_M}{L} v_{in}}$$



3) $j\omega \hat{V}_{out} e^{j\omega t} + \frac{R+R_M}{L} \hat{V}_{out} e^{j\omega t} = \frac{R_M}{L} V_{in} e^{j\omega t}$

$$\hat{V}_{out} = \frac{(R_M/L) V_{in}}{\frac{R+R_M}{L} + j\omega}$$

$$\boxed{\hat{V}_{out} = \frac{R_M(R+R_M) V_{in}}{1 + \frac{L}{R+R_M} j\omega}}$$

4) $V_{out} = |\hat{V}_{out}| = \frac{R_M}{R+R_M} \cdot \frac{V_{in}}{\sqrt{1 + \omega^2 \left(\frac{L}{R+R_M}\right)^2}}$
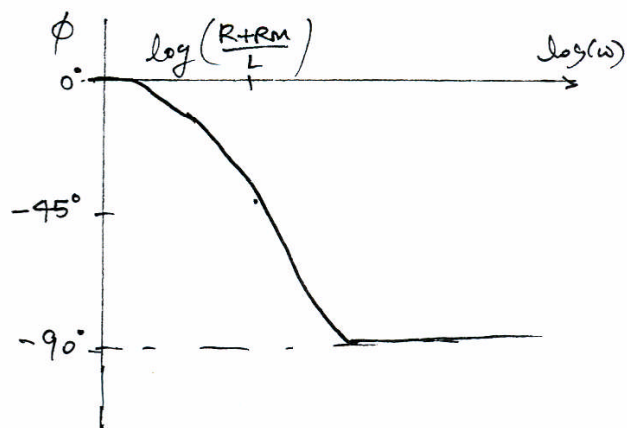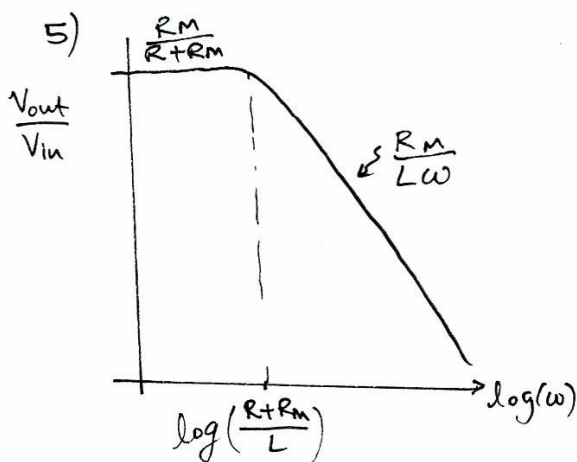
$$\boxed{\phi = -\tan^{-1} \left(\frac{L\omega}{R+R_M} \right)}$$





6.002 Problem Set 9 - Solus

Problem 9.1 contd.

(B) See below for plotted data. Please note that measurements could only be made up to $f=10\text{kHz}$ because of the maximum sampling rate on the oscilloscope.

f (Hz)	v_i (V)	v_{out} (V)	v_{out}/v_{in}	phi (s)	theta
10	0.79	0.38	0.48	4.40E-04	-1.58E+00
30	0.8	0.38	0.48	4.90E-04	-5.29E+00
100	0.8	0.37	0.46	4.80E-04	-1.73E+01
300	0.86	0.3	0.35	3.90E-04	-4.21E+01
1000	0.96	0.14	0.15	1.97E-04	-7.09E+01
3000	1	0.05	0.05	7.20E-05	-7.78E+01
10000	0.96	0.02	0.02	1.90E-05	-6.84E+01

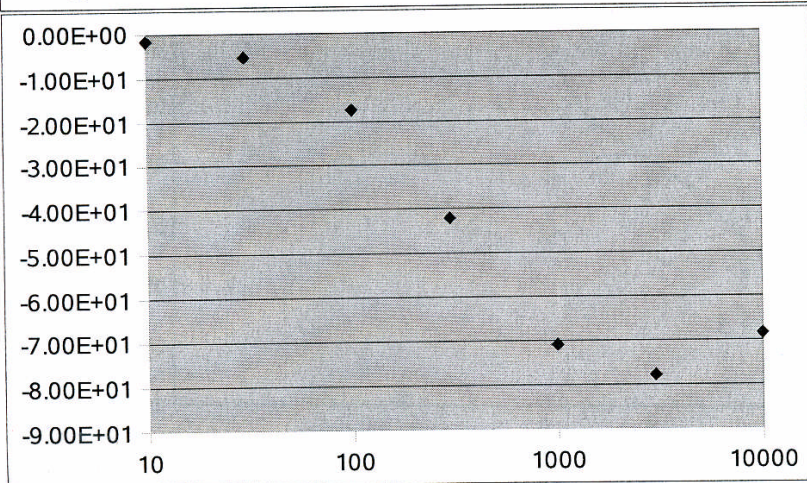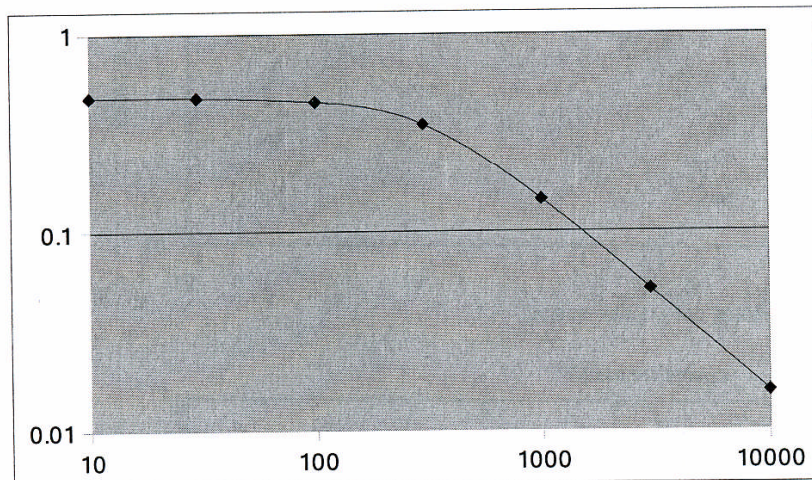

6.002 Pset #9 - Sol'ns

Problem 9.1 cont'd.

(c) At low f , the inductor acts as a short circuit, so the gain is


$$\frac{v_{out}}{v_{in}} = \frac{R_M}{R + R_M} = \frac{100}{R + 100} = \frac{0.381 V}{0.79 V}$$

$$79 = 0.381R + 38.1 \Rightarrow \boxed{R = 107 \Omega}$$

From P9.1(A), the corner frequency of the circuit is

$$\omega_c = \frac{R + R_M}{L} = \frac{100 + 107}{L} = 1.885 \text{ krad/s} \Rightarrow \boxed{L = 0.1 \text{ H}}$$


Problem 9.2

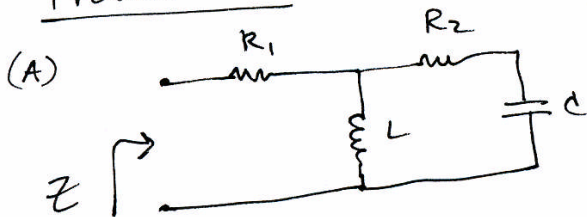

$$Z = \left(R_2 + \frac{1}{j\omega C} \right) \parallel j\omega L + R_1$$

$$= \frac{(j\omega R_2 C + 1) / j\omega C \cdot j\omega L}{j\omega L + \frac{j\omega R_2 C + 1}{j\omega C}} + R_1$$
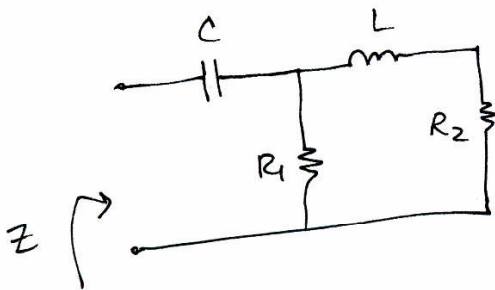
$$\boxed{Z = \frac{j\omega L (j\omega R_2 C + 1)}{j\omega R_2 C + 1 - \omega^2 LC} + R_1}$$




$$Z = (j\omega L + R_2) \parallel R_1 + \frac{1}{j\omega C}$$

$$\boxed{Z = \frac{(j\omega L + R_2) R_1}{j\omega L + R_2 + R_1} + \frac{1}{j\omega C}}$$

6.002 PSet #9 - Solutions

Problem 9.2 cont'd.

(B)

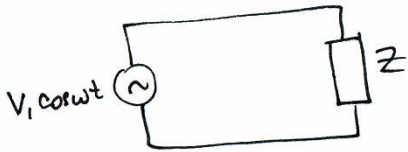

In both cases,

$$\hat{I} = \frac{V_1}{Z}$$

In the upper circuit,

$$\begin{aligned} \hat{I} &= \frac{V_1}{\frac{j\omega(j\omega R_2 C + 1)}{j\omega R_2 C + 1 - \omega^2 LC} + R_1} \\ &= \frac{V_1 (1 - \omega^2 LC + j\omega R_2 C)}{R_1 - \omega^2 LC R_1 - \omega^2 R_2 C + j\omega + j\omega R_1 R_2 C} \end{aligned}$$

$$I_1 \cos(\omega t + \phi) = |\hat{I}| \cos(\omega t + \angle \hat{I})$$

$$\begin{aligned} \therefore I_1 &= V_1 \frac{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R_2^2 C^2}}{\sqrt{(R_1 - \omega^2 LC R_1 - \omega^2 R_2 C)^2 + (\omega + \omega R_1 R_2 C)^2}} \\ \phi &= \tan^{-1} \left(\frac{\omega R_2 C}{1 - \omega^2 LC} \right) - \tan^{-1} \left(\frac{\omega + \omega R_1 R_2 C}{R_1 - \omega^2 LC R_1 - \omega^2 R_2 C} \right) \end{aligned}$$

For the lower circuit,

$$\begin{aligned} \hat{I} &= \frac{V_1}{\frac{j\omega C(j\omega L R_1 + R_2 R_1) + j\omega L + R_1 + R_2}{(j\omega L + R_1 + R_2) j\omega C}} \\ &= \frac{V_1 (-\omega^2 LC + j\omega C(R_1 + R_2))}{R_1 + R_2 - \omega^2 LC R_1 + j\omega(L + C R_1 R_2)} \end{aligned}$$


$$I_1 \cos(\omega t + \phi) = |\hat{I}| \cos(\omega t + \angle \hat{I})$$

$$\begin{aligned} \therefore I_1 &= V_1 \omega C \frac{\sqrt{\omega^2 L^2 + (R_1 + R_2)^2}}{\sqrt{(R_1 + R_2 - \omega^2 LC R_1)^2 + (\omega L + C R_1 R_2 \omega)^2}} \\ \phi &= \frac{\pi}{2} + \tan^{-1} \left(\frac{\omega L}{R_1 + R_2} \right) - \tan^{-1} \left(\frac{\omega(L + C R_1 R_2)}{R_1 + R_2 - \omega^2 LC R_1} \right) \end{aligned}$$

6.002 Pset #9 - Solutions

Problem 9.2 cont'd.

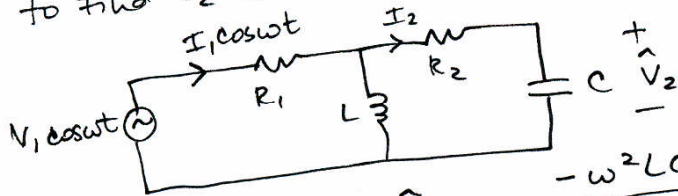(c) In part (B), we calculated $I_1 \cos(\omega t + \phi_1)$, the current in Port #1. Now, we can use a current divider expression to find V_2 and ϕ_2 .



$$\hat{I}_2 = \frac{j\omega L}{j\omega L + R_2 + j\omega C} \hat{I}_1 = \frac{-\omega^2 LC}{1 - \omega^2 LC + j\omega R_2 C} \hat{I}_1$$


$$\hat{V}_2 = \frac{1}{j\omega C} \cdot \hat{I}_2 = \frac{j\omega L \hat{I}_1}{1 - \omega^2 LC + j\omega R_2 C}$$

$$V_2 \cos(\omega t + \phi_2) = |\hat{V}_2| \cos(\omega t + \angle \hat{V}_2)$$

$$|\hat{V}_2| = \frac{\omega L}{\sqrt{(1 - \omega^2 LC)^2 + (\omega^2 R_2^2 C^2)}} |\hat{I}_1| = \frac{\omega L V_1}{\sqrt{(R_1 - \omega^2 LC R_1 - \omega^2 R_2 C)^2 + (\omega + \omega R_1 R_2 C)^2}}$$

$$\phi_2 = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega R_2 C}{1 - \omega^2 LC}\right) + \angle \hat{I}_1 = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega + \omega R_1 R_2 C}{R_1 - \omega^2 LC R_1 - \omega^2 R_2 C}\right)$$

Similarly for the second circuit

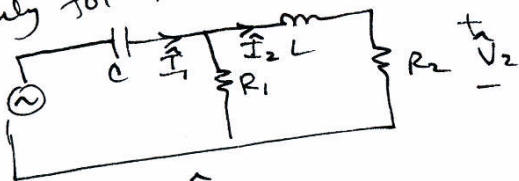

$$\hat{I}_2 = \frac{R_1}{R_1 + R_2 + j\omega L} \hat{I}_1$$

$$\hat{V}_2 = R_2 \hat{I}_2 = \frac{R_1 R_2}{R_1 + R_2 + j\omega L} \hat{I}_1$$


$$|\hat{V}_2| = \frac{R_1 R_2}{\sqrt{(R_1 + R_2)^2 + (\omega L)^2}} |\hat{I}_1| = \frac{R_1 R_2 \omega C V_1}{\sqrt{(R_1 + R_2 - \omega^2 LC R_1)^2 + (\omega L + \omega C R_1 R_2)^2}}$$

$$\phi_2 = \angle \hat{I}_1 - \tan^{-1}\left(\frac{\omega L}{R_1 + R_2}\right) = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega(L + C R_1 R_2)}{R_1 + R_2 - \omega^2 LC R_1}\right)$$

6.002 Pset #9 - Solus

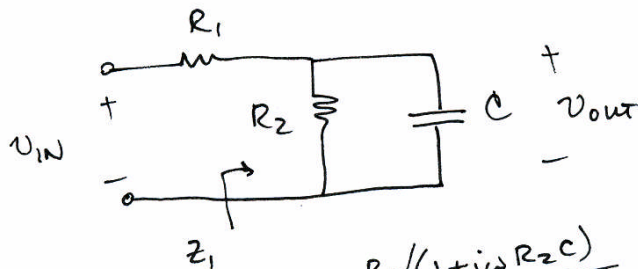Problem 9.3

The low-frequency gain of the network is 0.8, and it is configured in a low-pass configuration with corner frequency $f_c = 700$ Hz. These details tell us that the three elements are configured



$$Z_1 = \frac{R_2/j\omega C}{R_2 + j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$$

$$\frac{v_{out}}{v_{in}} = \frac{Z_1}{Z_1 + R_1} = \frac{R_2/(1 + j\omega R_2 C)}{\frac{R_2}{1 + j\omega R_2 C} + R_1} = \frac{R_2}{R_1 + R_2 + j\omega R_1 R_2 C}$$

$$\text{At } \omega = 0 \quad \frac{v_{out}}{v_{in}} = \frac{R_2}{R_1 + R_2} = 0.8 \Rightarrow \begin{aligned} 0.8 R_1 &= 0.2 R_2 \\ R_2 &= 4 R_1 \end{aligned}$$

$$\omega_c = \frac{R_1 + R_2}{R_1 R_2 C} = \frac{R_1 + 4R_1}{4R_1^2 (0.1 \mu)} = 800$$

$$5 = (0.32 \text{ m}) R_1 \Rightarrow \begin{aligned} R_1 &= 15.625 \text{ k}\Omega \\ R_2 &= 62.5 \text{ k}\Omega \end{aligned}$$

(see Appendix II for values).


6.002 PSet #9 - Solutions

Problem 9.4

(A) Since the same laws apply as with purely resistive circuits, we get

$$\hat{V}_T = Z_N \hat{I}_N \quad \hat{I}_N = \frac{\hat{V}_T}{Z_T} \quad Z_T = Z_N$$

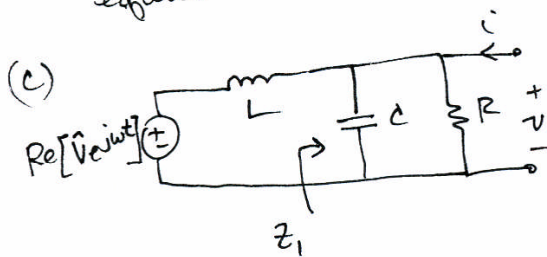(B) We see that each network has a sinusoidal source at frequency ω rad/s, and the output will have a magnitude and phase-shifted version of the same frequency sinusoidal source. Since both networks are equivalent as long as they obey the relationship in (A), they are Thevenin and Norton equivalents.



$$\hat{V}_T = \frac{Z_1}{j\omega L + Z_1} \hat{V}$$

$$Z_1 = \frac{R/j\omega C}{R + 1/j\omega C} = \frac{R}{1 + j\omega CR}$$

$$\hat{V}_T = \frac{R/(1 + j\omega CR) \hat{V}}{j\omega L + \frac{R}{(1 + j\omega CR)}}$$

$$\hat{V}_T = \frac{R \hat{V}}{R + j\omega L - \omega^2 LCR}$$

$$Z_T = Z_1 \parallel j\omega L = \frac{Rj\omega L / (1 + j\omega CR)}{j\omega L + \frac{R}{(1 + j\omega CR)}}$$

$$\Rightarrow Z_T = \frac{j\omega LR}{R - \omega^2 LCR + j\omega L}$$

(D) For network #4, $Z_T = R_T + \frac{1}{j\omega C_T} = R_T - \frac{j}{\omega C_T}$ (1)

From part (C), $Z_T = \frac{j\omega LR (R - \omega^2 LCR - j\omega L)}{(R - \omega^2 LCR)^2 + \omega^2 L^2}$

$$Z_T = \frac{\omega^2 L^2 R + j\omega LR^2 (1 - \omega^2 LC)}{(R - \omega^2 LCR)^2 + \omega^2 L^2}$$
 (2)

Equating the real and imaginary parts of (1) and (2), we get

$$R_T = \frac{\omega^2 L^2 R}{(R - \omega^2 LCR)^2 + \omega^2 L^2} \quad \text{and} \quad C_T = -\frac{\omega^2 L^2 + (R - \omega^2 LCR)^2}{\omega^2 L R^2 (1 - \omega^2 LC)}$$

6.002 Problem Set 9 Sol'us

Problem 9.4 cont'd.

(D) cont'd.

For network #5,

$$Z_T = R_T + j\omega L_T \quad (3)$$

Equating the real and imaginary parts of (2) and (3), we get


$$R_T = \frac{\omega^2 L^2 R}{(R - \omega^2 LC)^2 + \omega^2 L^2} \quad \text{and} \quad L_T = \frac{LR^2(1 - \omega^2 LC)}{(R - \omega^2 LC)^2 + \omega^2 L^2}$$

Network #4 is preferred when we do not want low frequency signals to pass since the capacitor behaves as an open circuit at low frequencies. Similarly, Network #5 is preferred when we do not want high frequency signals to pass since the inductor behaves as an open circuit at high frequencies.

6.002 Pset #9 - Solus

Appendix I

Exercise 9.2

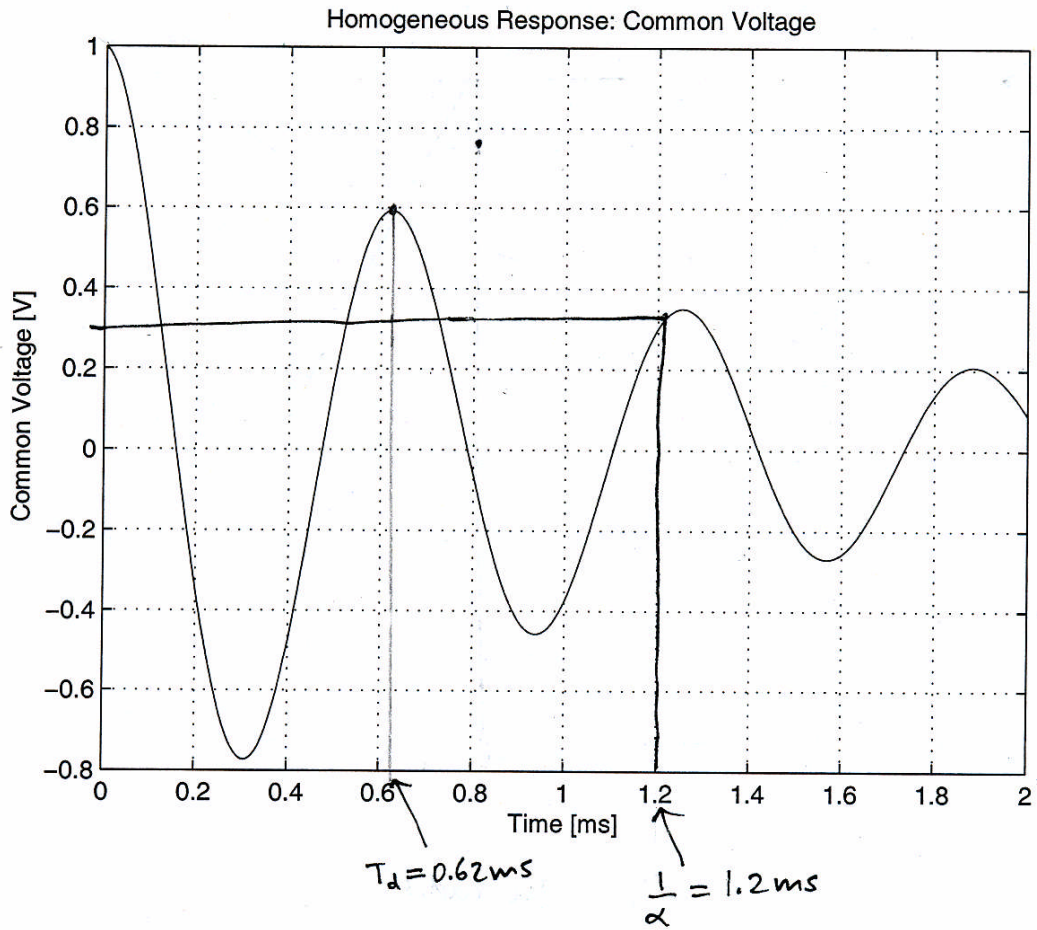

Appendix II

Problem 9.3

