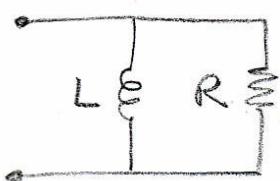


6.002 - Spring 2008 - PSET 10

Solutions - 4/23/08

Exercise 10.1




Parallel impedances combine like parallel

resistors:
$$Z_{tot} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{R}} = \frac{j\omega RL}{R + j\omega L}$$

For very low frequencies, $Z_{tot}(\omega \rightarrow 0) = 0$
as the inductor approaches a short circuit.

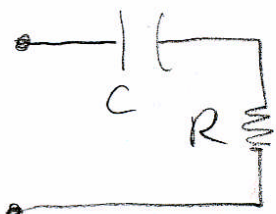For very high frequencies, $Z_{tot}(\omega \rightarrow \infty) = R$,
since $j\omega L \gg R$ and the inductor approaches an open circuit.



Series impedances combine like series


resistors:
$$Z_{tot} = R + \frac{1}{j\omega C}$$

At low frequencies, the capacitor impedance dominates,
approaching an open circuit and $Z_{tot}(\omega \rightarrow 0) \rightarrow \infty$

At high frequencies, the capacitor approaches a
short circuit and $Z_{tot}(\omega \rightarrow \infty) = R$

Exercise 10.2

2

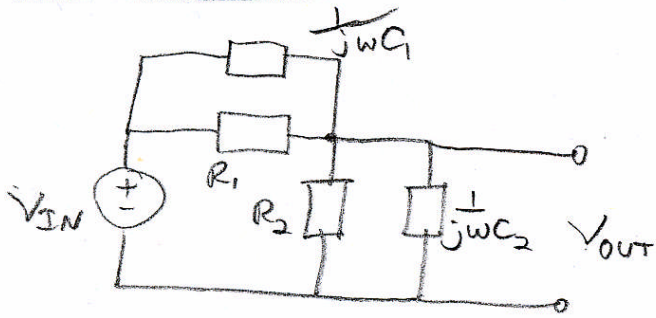

Combining // impedances:

$$\frac{1}{\frac{1}{R} + j\omega C} = \frac{R}{1 + j\omega RC}$$

Using a voltage divider with the 2 parallel combinations:

$$V_{OUT} = V_{IN} \left(\frac{\frac{R_2}{1 + j\omega R_2 C_2}}{\frac{R_2}{1 + j\omega R_2 C_2} + \frac{R_1}{1 + j\omega R_1 C_1}} \right)$$

and multiplying through by both denominators gives

OR

$$V_{OUT} = V_{IN} \frac{R_2 (1 + j\omega R_1 C_1)}{R_2 (1 + j\omega R_1 C_1) + R_1 (1 + j\omega R_2 C_2)}$$

If $R_1 C_1 = R_2 C_2$ then $(1 + j\omega R_1 C_1) = (1 + j\omega R_2 C_2)$ and

$$V_{OUT} = V_{IN} \left(\frac{R_2}{R_1 + R_2} \right) \text{ and } \phi = 0$$


for $V_{out} = 0.1 V_{in}$, $\frac{R_2}{R_1 + R_2} = \frac{1}{10}$ $R_1 = 9R_2$

using $R_1 C_1 = R_2 C_2$ and $R_1 = 9R_2$, $9R_2 C_1 = R_2 C_2$

$C_2 = 9C_1$

Problem 10.1

3

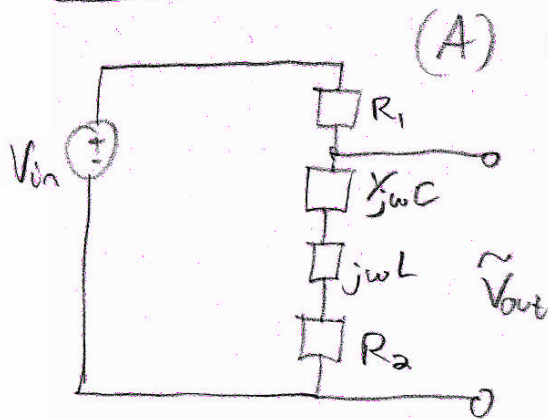

(A) Using a voltage divider


$$\tilde{V}_{out} = V_{in} \left(\frac{j\omega C + j\omega L + R_2}{(R_1 + R_2) + j\omega C + j\omega L} \right)$$

$$\tilde{V}_{out} = V_{in} \left(\frac{(1 - \omega^2 LC) + j\omega CR_2}{(1 - \omega^2 LC) + j\omega C(R_1 + R_2)} \right)$$


$$V_{out} = V_{in} \sqrt{\frac{(1 - \omega^2 LC)^2 + (\omega CR_2)^2}{(1 - \omega^2 LC)^2 + (\omega C(R_1 + R_2))^2}}$$

$$\phi = \tan^{-1} \left(\frac{\omega CR_2}{1 - \omega^2 LC} \right) - \tan^{-1} \left(\frac{\omega C(R_1 + R_2)}{1 - \omega^2 LC} \right)$$

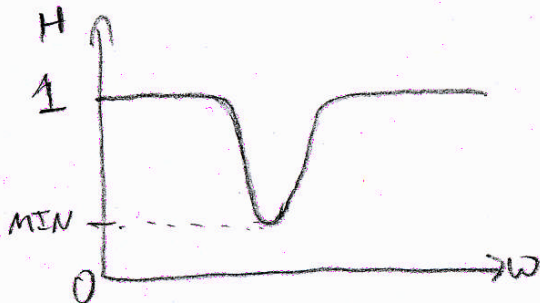(B) For the notch filter, $H = \frac{\tilde{V}_{out}}{V_{in}}$ has the general shape:



but if we define the gain $G = 1 - H$

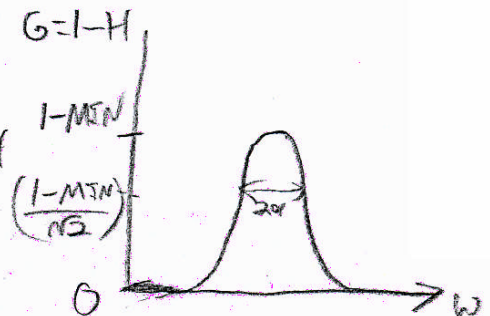

Now $G = 1 - H$ looks like a bandpass filter and we can use the bandpass definition of Q

Problem 10.1 (continued)

4

(B) so $G = 1 - H = \left| -\frac{\tilde{V}_{out}}{V_{in}} \right| = \left| -\frac{(1 - \omega^2 LC) + j\omega CR_2}{(1 - \omega^2 LC) + j\omega C(R_1 + R_2)} \right|$

$$G = \frac{(1 - \omega^2 LC) + j\omega C(R_1 + R_2) - (1 - \omega^2 LC) - j\omega CR_2}{(1 - \omega^2 LC) + j\omega C(R_1 + R_2)}$$



$$G = \frac{j\omega CR_1}{(1 - \omega^2 LC) + j\omega C(R_1 + R_2)}$$

this is the same form as a bandpass filter, and 2α is

the coefficient of the 1st order, $j\omega$, term, after dividing through by LC to give 1 for the coefficient of the highest, 2nd order, ω^2 term.

$$2\alpha = \frac{R_1 + R_2}{L} \quad \text{and} \quad Q \equiv \frac{\omega_0}{2\alpha} = \frac{1}{\sqrt{LC}} \frac{L}{R_1 + R_2}$$
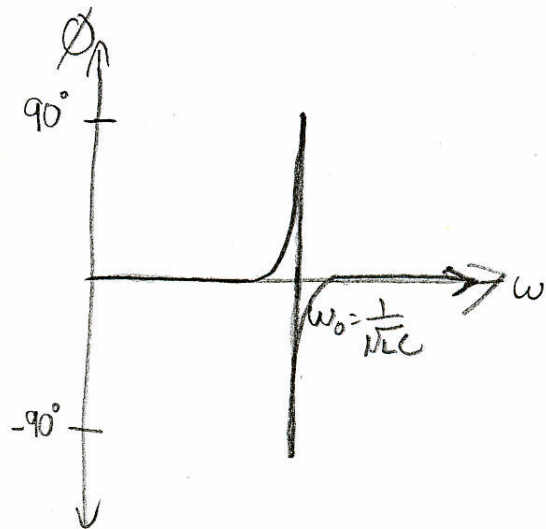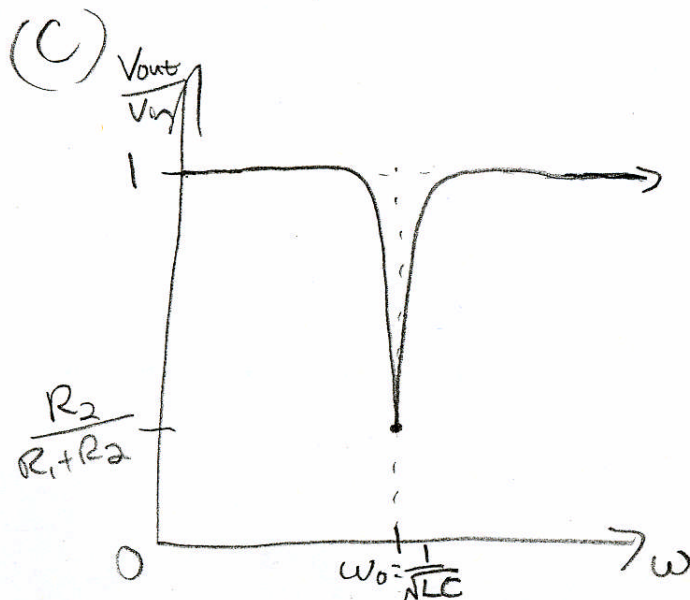
$$Q = \sqrt{\frac{L}{C}} \cdot \frac{1}{R_1 + R_2}$$



5

MIT Feedback Systems WebLab Client

File Measurement Results Help

Circuit Schematic

Test 2: Swept Sine Experiment

Source Level (Pk-to-Pk) (V/Pk):



2.0

Start Frequency (kHz):

1.0

Stop Frequency (kHz):

50000.0

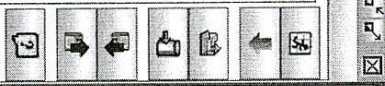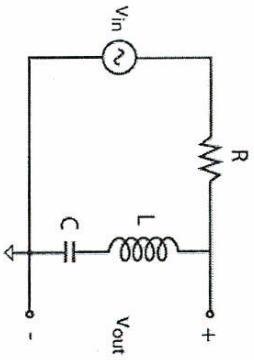

1.000E0

Y1 Axis:
magnitude

Scale:
Logarithmic

autoscale

1.0 decade / division

100.0E-3

Tracking


X Axis: Frequency

1.0 decade / division

Scale: Logarithmic

100000 Hz

autoscale

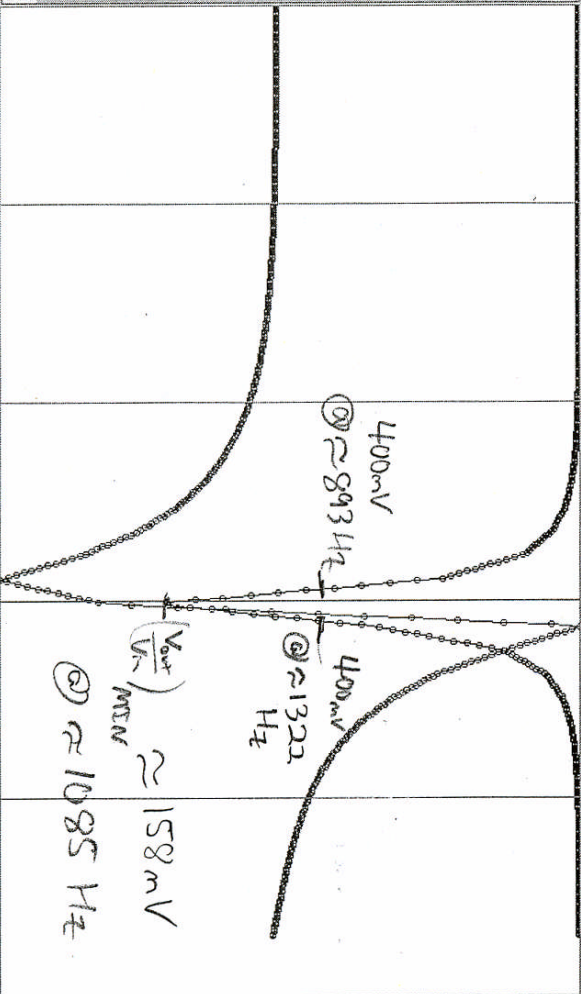

46.34 deg

Y2 Axis:
phase

Scale:
Linear

autoscale

88.6 deg / division

-42.25 deg

Problem 10.1 (continued)

6

(D) See attached screen shot

(E) given $L = 98 \text{ mH}$, the minimum output voltage occurs at the resonant frequency, $\omega_0 \approx 1085.2 \pi$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega_0^2 L} \approx \frac{1}{(2\pi \cdot 1085)^2 \cdot 98 \cdot 10^{-3}}$$

$$C \approx 0.22 \mu\text{F}$$

at $\omega = \omega_0$, the minimum value $\left(\frac{V_{out}}{V_{in}}\right)_{min} = \frac{\omega_0 C R_2}{\omega_0 C (R_1 + R_2)} = \frac{R_2}{R_1 + R_2}$

From the plot, $\left(\frac{V_{out}}{V_{in}}\right)_{min} \approx 158 \text{ mV}$

Can also graphically find the bandwidth, 2α , as the difference in frequency when $G = \frac{G_{max}}{\sqrt{2}} = 1 - H$, $H = \frac{V_{out}}{V_{in}}$

$$G_{max} = 1 - \left(\frac{V_{out}}{V_{in}}\right)_{min} \text{ so } 1 - \frac{V_{out}}{V_{in}} = \frac{1 - \left(\frac{V_{out}}{V_{in}}\right)_{min}}{\sqrt{2}} \text{ with } \left(\frac{V_{out}}{V_{in}}\right)_{min} = 0.158 \text{ V}$$

$$\left(\frac{V_{out}}{V_{in}}\right) = 1 - \frac{1 - \left(\frac{V_{out}}{V_{in}}\right)_{min}}{\sqrt{2}} \approx 0.40 \text{ V at } f \approx 1322 \text{ and } 893 \text{ Hz}$$

$$2\alpha \approx (1322 - 893) \cdot 2\pi = \text{and from (B) } 2\alpha = \frac{R_1 + R_2}{L}$$

$$\text{so (1) } \frac{R_2}{R_1 + R_2} = 0.158 \text{ and (2) } 2\alpha L = R_1 + R_2$$


$$R_2 = 0.158(2\alpha L) \approx 0.158(1322 - 893) \cdot 2\pi(98 \cdot 10^{-3}) \approx 42 \Omega$$

$$R_1 \approx 2\alpha L - R_2 \approx 222 \Omega$$

$$R_1 \approx 220 \Omega, R_2 \approx 42 \Omega$$

Problem 10.2

7

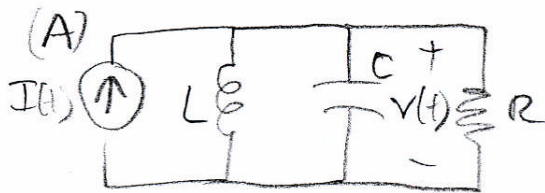

The voltage $V(t)$ is equal to the input current times the parallel combination of the three impedances:

$$\tilde{V} = I \left(\frac{1}{\frac{1}{j\omega L} + j\omega C + \frac{1}{R}} \right) = I \left(\frac{j\omega LR}{R(1 - \omega^2 LC) + j\omega L} \right)$$

$$V(\omega) = |\tilde{V}| = I \cdot \frac{\omega LR}{\sqrt{R^2(1 - \omega^2 LC)^2 + (\omega L)^2}}$$

$$\phi(\omega) = \frac{\pi}{2} - \tan^{-1} \left(\frac{\omega L}{R(1 - \omega^2 LC)} \right)$$

(B) To maximize V , minimize denominator

with $\omega^2 LC = 1$, $\omega = \frac{1}{\sqrt{LC}}$

(C) $L = 365 \mu\text{H}$, need

$$2\pi \cdot 540,000 \leq \omega = \frac{1}{\sqrt{LC}} \leq 2\pi \cdot 1,600,000$$

$$L \cdot (2\pi \cdot 540e3)^2 \leq \frac{1}{C} \leq L \cdot (2\pi \cdot 1600e3)^2$$

$$\frac{1}{365 \cdot 4\pi^2 \cdot 1600^2} \leq C \leq \frac{1}{365 \cdot 4\pi^2 \cdot 540^2}$$

$$27.1 \text{ pF} \leq C \leq 238 \text{ pF}$$

Problem 10.2 (continued)

8

(D) $\frac{V(\omega)}{V(\omega_0)} = \frac{1}{4}$ where ω_0 is the center frequency
 $\omega_0 = 2\pi \cdot 1\text{MHz}$ and $V(\omega_0) = IR$

$L = 365\text{mH}$, $C = \frac{1}{\omega_0^2 L} \approx 69.4\text{pF}$

$$\frac{V(\omega)}{V(\omega_0)} = \frac{I\omega LR}{IR \sqrt{R^2(1-\omega^2 LC)^2 + (\omega L)^2}} = \frac{1}{4}$$

$$\frac{1}{16} = \frac{\omega^2 L^2}{R^2(1-\omega^2 LC)^2 + \omega^2 L^2} \text{ OR } R^2(1-\omega^2 LC)^2 = 15\omega^2 L^2$$

$R^2 = \frac{15\omega^2 L^2}{(1-\omega^2 LC)^2}$ and $R = \pm \frac{\omega L \sqrt{15}}{(1-\omega^2 LC)}$ with the sign chosen to give a positive R

Using $L = 365\text{mH}$, $C = 69.4\text{pF}$ and $\omega = 2\pi \cdot 1.005\text{MHz}$

gives $R \approx 888\text{ }\Omega$ can check that $\omega = 2\pi \cdot 0.995\text{MHz}$ gives same

(E) $\left. \frac{V(\omega)}{V(\omega_0)} \right|_{\omega = 1.010\text{MHz} \cdot 2\pi \text{ or } \omega = 0.990\text{MHz} \cdot 2\pi} = \frac{\omega L}{\sqrt{R^2(1-\omega^2 LC)^2 + (\omega L)^2}} \approx 0.13$

For Q - from (A) replace $j\omega \rightarrow \Delta$ or $\frac{d}{dt}$ to find the Parallel RLC

$Q \equiv \frac{\omega}{2\alpha}$ Characteristic equation: $\tilde{V}(\Delta^2 + \Delta \cdot \frac{1}{RC} + \frac{1}{LC}) = \frac{I \cdot \Delta}{C}$


So $2\alpha = \frac{1}{RC}$ and $Q = 2\pi f \cdot RC \Rightarrow Q \approx 387$

Problem 10.2 (continued)

9

(F) As $v(t)$ decays proportionally to $e^{-\alpha t}$ after 3 time constants, $\tau = \frac{1}{\alpha} = 2RC \approx 123 \mu\text{sec}$, the voltage from the first station will have decayed to $\approx 5\%$ of the original value. Also, Q is the number of oscillations before the energy in the transient has decayed to practically zero, so the time is $Q \cdot T = Q \cdot \frac{1}{f_{\text{first station}}} \approx \frac{Q}{1 \cdot 10^6} \approx 387 \mu\text{sec}$.

Problem 10.3

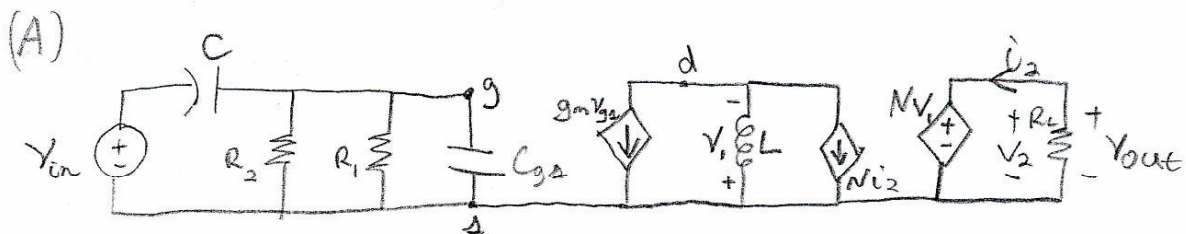

(B)
$$V_{gs} = V_{in} \left(\frac{\frac{1}{j\omega C_{gs} + \frac{1}{R_1} + \frac{1}{R_2}}}{\frac{1}{j\omega C_{gs} + \frac{1}{R_1} + \frac{1}{R_2}} + \frac{1}{j\omega C}} \right) = \frac{j\omega C}{j\omega C + j\omega C_{gs} + \frac{1}{R_1} + \frac{1}{R_2}}$$

$$V_{gs} = V_{in} = \frac{j\omega C}{j\omega(C + C_{gs}) + \frac{R_1 + R_2}{R_1 R_2}} = V_{in} \frac{j\omega C R_{eq}}{j\omega R_{eq}(C + C_{gs}) + 1} \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{out} = N \cdot V_2, \quad V_1 = i_2 \cdot j\omega L = (g_m V_{gs} + N i_2) j\omega L \quad i_2 = -\frac{V_{out}}{R_L}$$

$$\frac{V_{out}}{N} \left(g_m V_{gs} - \frac{N V_{out}}{R_L} \right) j\omega L; \quad V_{out} \left(1 + \frac{N^2 j\omega L}{R_L} \right) = N j\omega L g_m V_{gs}$$

$$V_{out} = V_{gs} \left(\frac{j\omega L \cdot N \cdot g_m \cdot R_L}{R_L + jN^2 \omega L} \right) \text{ combine with } V_{gs}$$

Problem 10.3 (continued)

10

(B) Combining $v_{gs} = f(v_{in})$ with $v_{out} = f(v_{gs})$

and (C)

$$V_{out} = V_{in} \left(\frac{j\omega C R_{eq}}{1 + j\omega R_{eq} (C + C_{gs})} \right) \left(\frac{j\omega L \cdot N \cdot g_m R_L}{R_L + jN^2 \omega L} \right)$$

$$G = \frac{V_{out}}{V_{in}} = \frac{-\omega^2 L C R_{eq} R_L N \cdot g_m}{(1 + j\omega R_{eq} (C + C_{gs})) (R_L + jN^2 \omega L)}$$

where $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

$G \rightarrow 0$ as $\omega \rightarrow 0$

$$G \rightarrow \frac{-\omega^2 L C R_{eq} R_L N g_m}{-\omega^2 R_{eq} N^2 L (C + C_{gs})} = \frac{g_m R_L C}{N (C + C_{gs})}$$

as $\omega \rightarrow \infty$


(B)

$$V_{out} = V_{in} \frac{-\omega^2 L C R_{eq} R_L N \cdot g_m}{\sqrt{(1 + \omega^2 R_{eq}^2 (C + C_{gs})^2) (R_L^2 + \omega^2 N^4 L^2)}}$$

$$\phi = 180^\circ - \left[\tan^{-1} \left(\frac{\omega R_{eq} (C + C_{gs})}{1} \right) + \tan^{-1} \left(\frac{\omega L N^2}{R_L} \right) \right]$$

(D) L and C should be made as large as possible to increase the low frequency gain and extending the bandwidth by decreasing the value of low frequency points for a particular value of gain

Problem 10.4

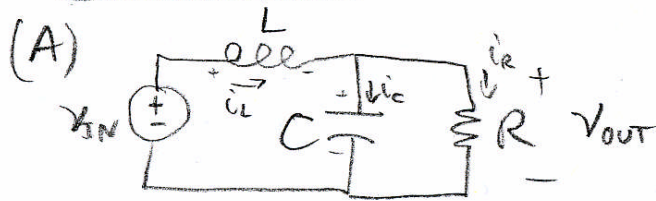

KCL at unknown Node:

$$i_L = i_C + i_R$$

with constitutive relations

$$i_C = C \frac{dV}{dt} \quad \text{and} \quad V_L = L \frac{di_L}{dt}$$

where the inductor

$$\text{voltage } V_L = V_{IN} - V_{OUT}$$

$$\left(\frac{\sqrt{V_L}}{L} = C \frac{dV_{OUT}}{dt} + \frac{V_{OUT}}{R} \right)$$

differentiating gives

$$\frac{V_{IN} - V_{OUT}}{L} = C \frac{d^2 V_{OUT}}{dt^2} + \frac{dV_{OUT}}{dt} \cdot \frac{1}{R}$$

OR

$$\boxed{\frac{d^2 V_{OUT}}{dt^2} + \frac{1}{RC} \frac{dV_{OUT}}{dt} + \frac{V_{OUT}}{LC} = \frac{V_{IN}}{LC}}$$

(B) Can be solved using impedances or by substituting $V_{IN} = \text{Re} \{ V_{in} e^{j\omega t} \}$ and $V_{OUT} = \text{Re} \{ \tilde{V}_o e^{j\omega t} \}$

$$- \omega^2 \tilde{V}_o + \frac{j\omega \tilde{V}_o}{RC} + \frac{\tilde{V}_o}{LC} = \frac{V_{in}}{LC}$$

OR

$$\tilde{V}_o (-\omega^2 RLC + j\omega L + R) = V_{in} \cdot R$$

$$\boxed{G \equiv \frac{V_{out}}{V_{in}} = \left| \frac{\tilde{V}_o}{V_{in}} \right| = \frac{R}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2}}}$$

$$\boxed{\phi = -\tan^{-1} \left(\frac{\omega L}{R(1 - \omega^2 LC)} \right)}$$

Problem 10.4 (continued)

12

(C) To maximize $G = \frac{R}{\sqrt{R(1-\omega^2 LC) + (\omega L)^2}}$

Need to minimize the denominator by

letting $\omega^2 LC = 1$ so $C = \frac{1}{\omega^2 L}$

and $G = \frac{R}{\omega L}$

(D) With $v_{in}(t) = 0$, the homogeneous response of the damped, second order system will be a sinusoid decaying at $e^{-\alpha t}$ where

$2\alpha = \frac{1}{RC}$ from the differential eqn. in (A)

so $\tau = \frac{1}{\alpha} = 2RC$ with $C = \frac{1}{\omega^2 L}$ and $G = \frac{R}{\omega L}$

$\tau = \frac{2R}{\omega^2 L} = \frac{2G}{\omega}$

(E) Since the time constant is proportional to the gain, the greater the boost in voltage, the longer the circuit will oscillate after any change in v_{in} . There is a trade off between response time and voltage gain.