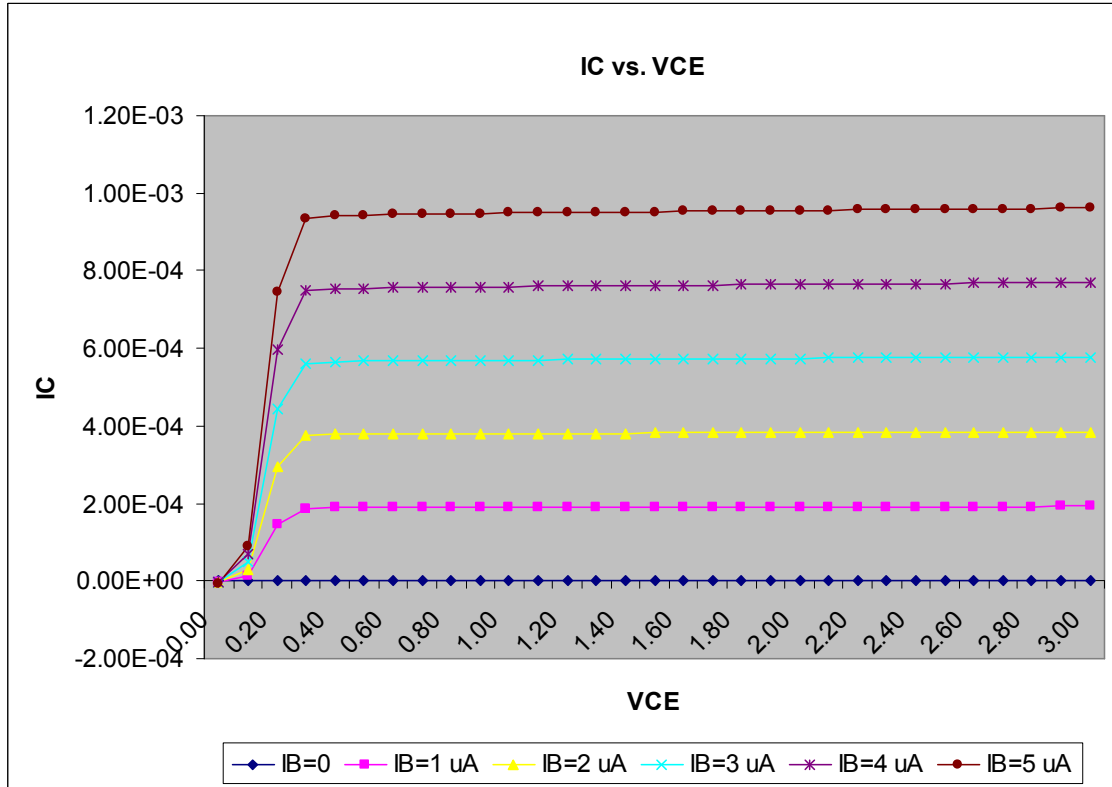


Note: The specified current range of 50 μ A – 1mA was essential to be taken into account when representing the graphs.


Graph 1)

I_C vs. V_{CE} for different values of I_B :




Graph 2)

I_D vs. V_{DS} for different values of V_{GS} :

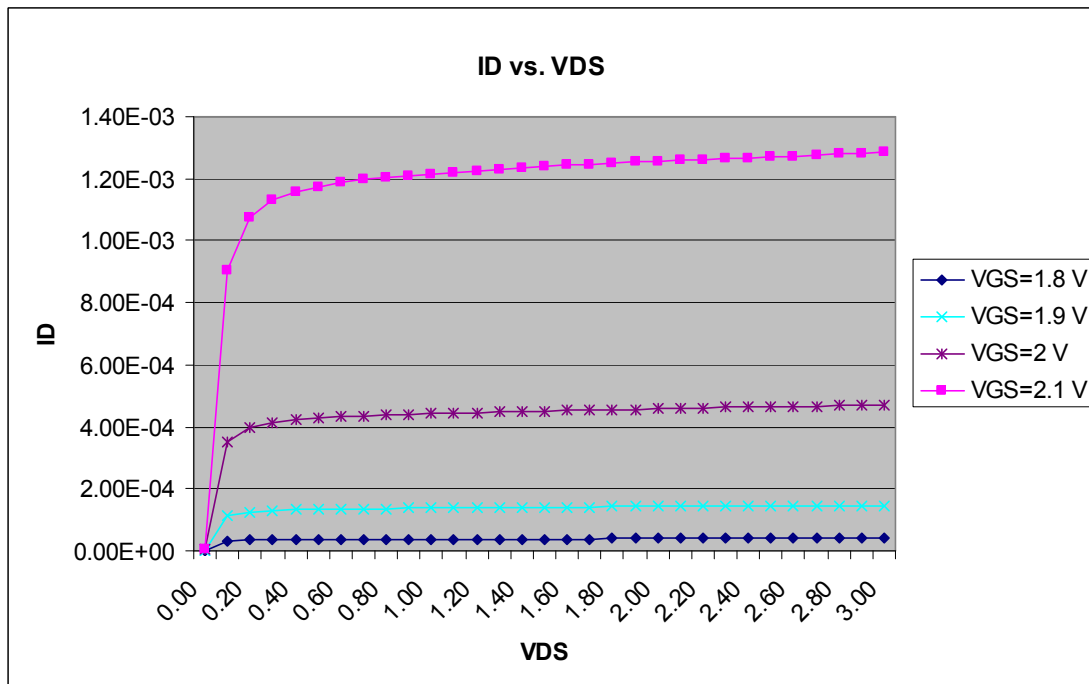


Graph 3)

I_C vs. V_{BE} for $V_{CE}=1.5$ V:

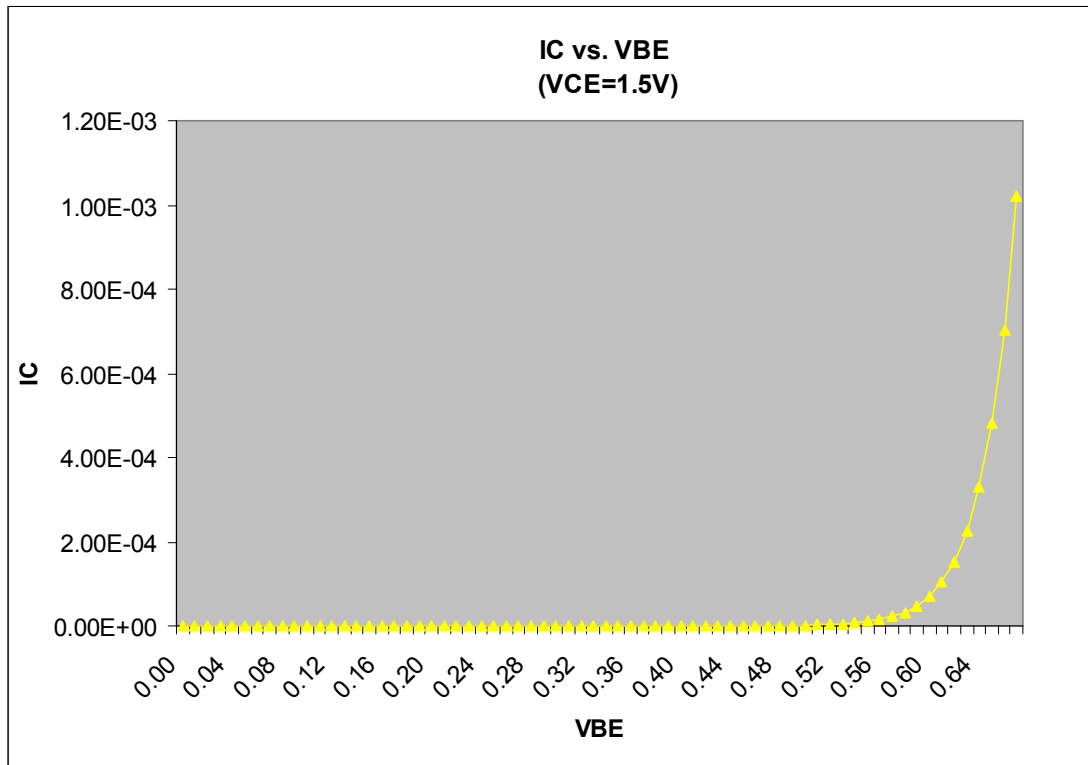


Graph 4)

I_B vs. V_{BE} for $V_{CE}=1.5$ V:

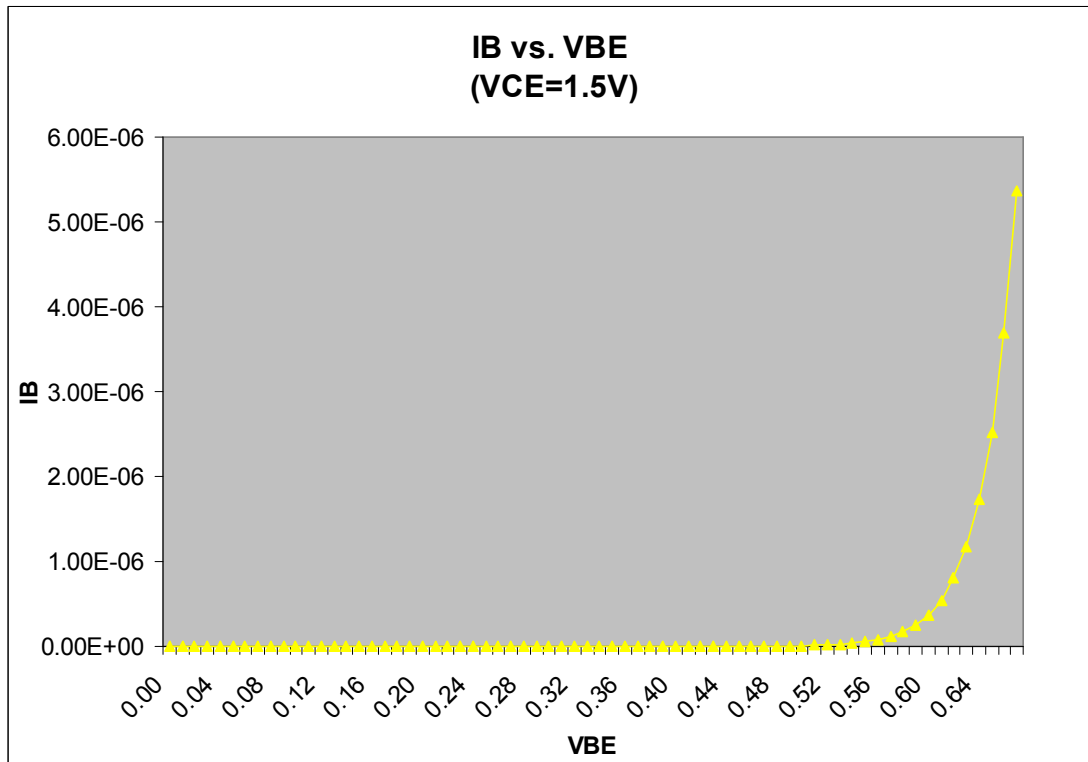


Graph 5)

$r_{o(NMOS)}$ as a function of V_{DS} for different values of I_D (or V_{GS}):

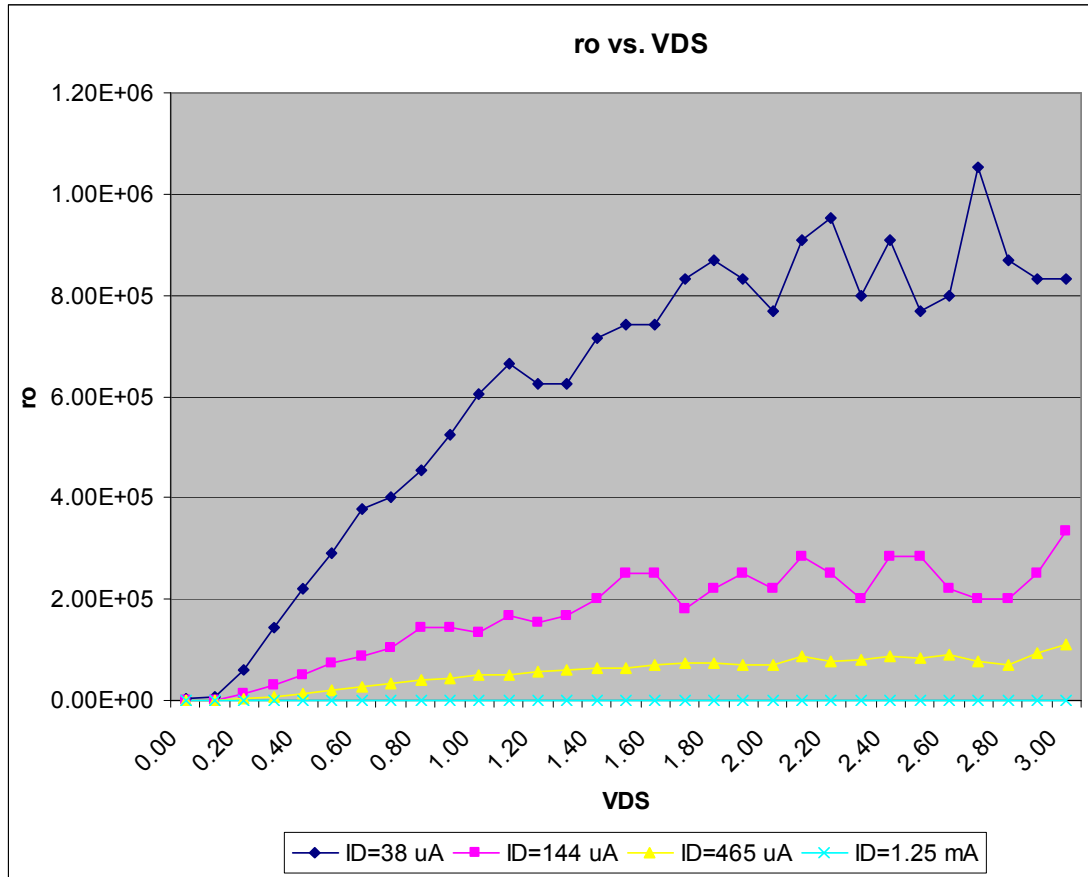


Graph 6)

$r_{o(BJT)}$ as a function of V_{CE} for different values of I_C (or V_{BE}):

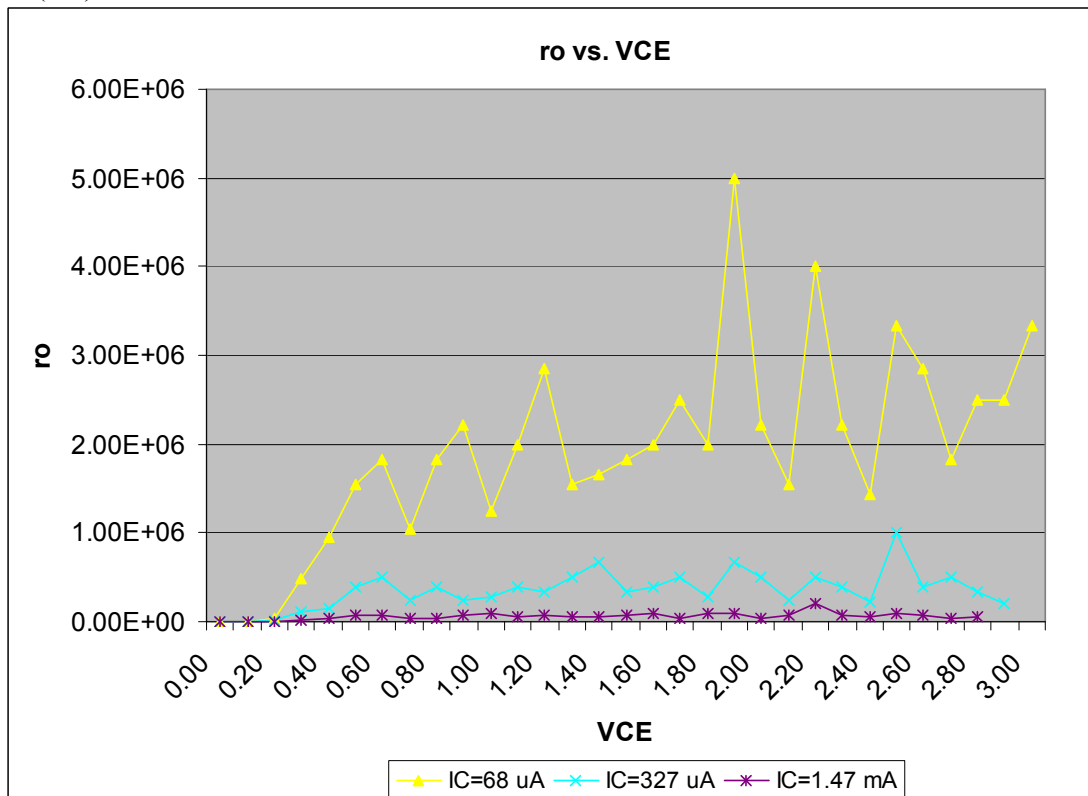


Graph 7)

$r_{o(NMOS)}$ as a function of I_D for $V_{DS}=1.5V$:

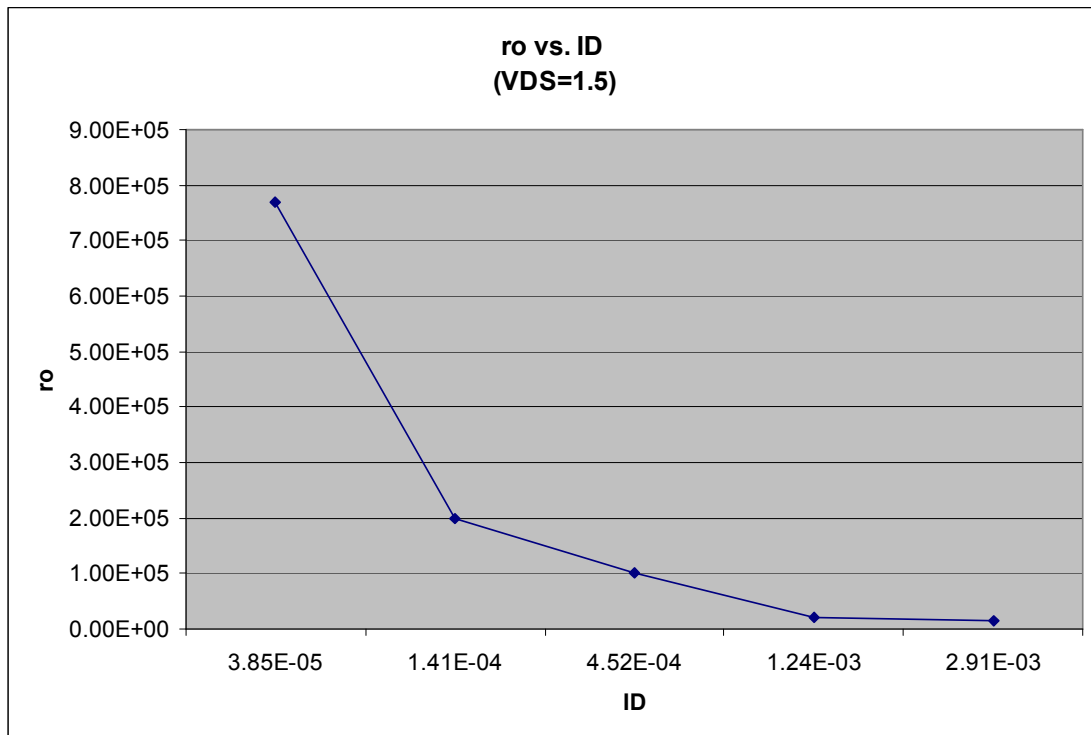


Graph 8)

$r_{o(BJT)}$ as a function of I_C for $V_{CE}=1.5V$:

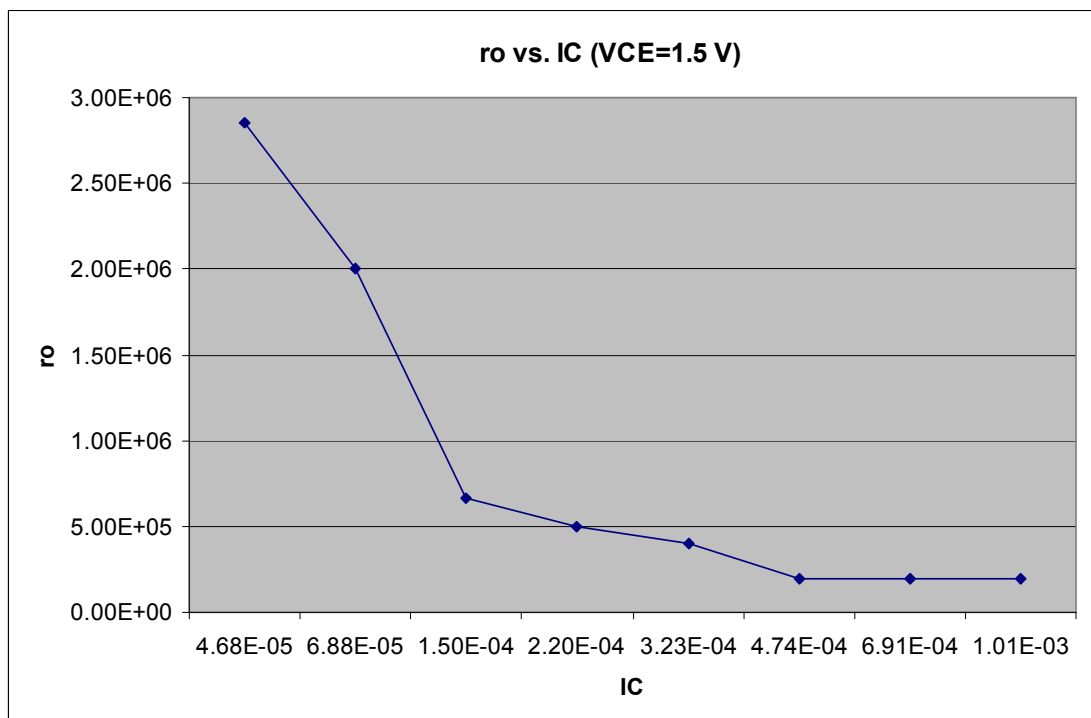


Graph 9)


$g_{m(BJT)}$ as a function of I_C for $V_{CE}=1.5V$:

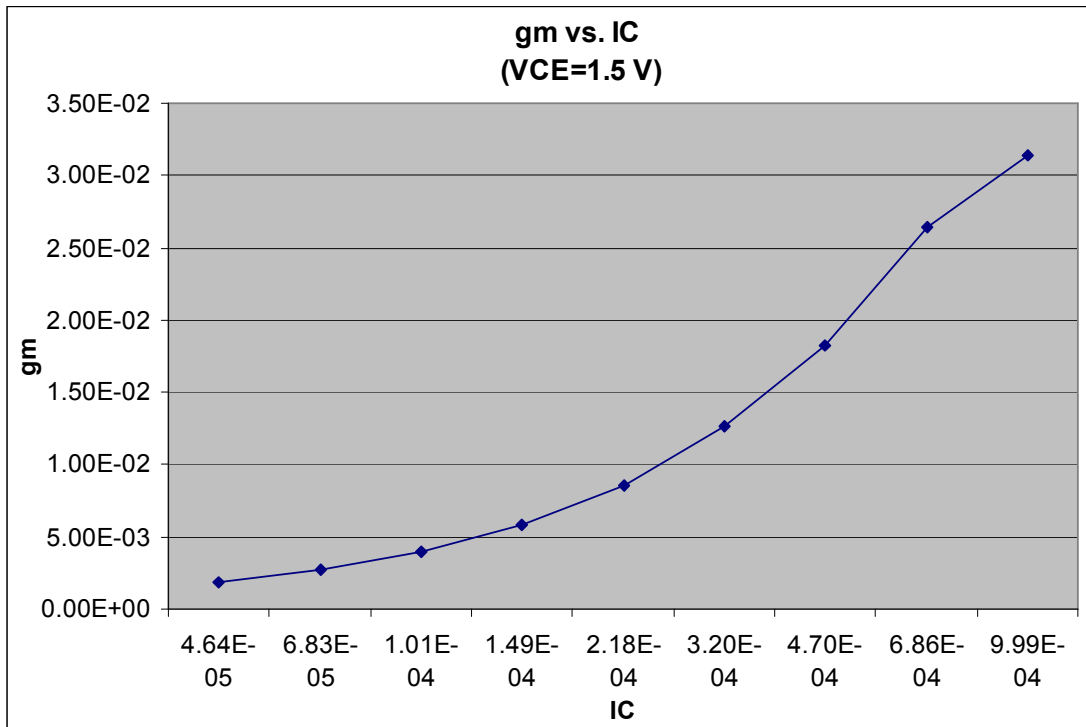


Graph 10)

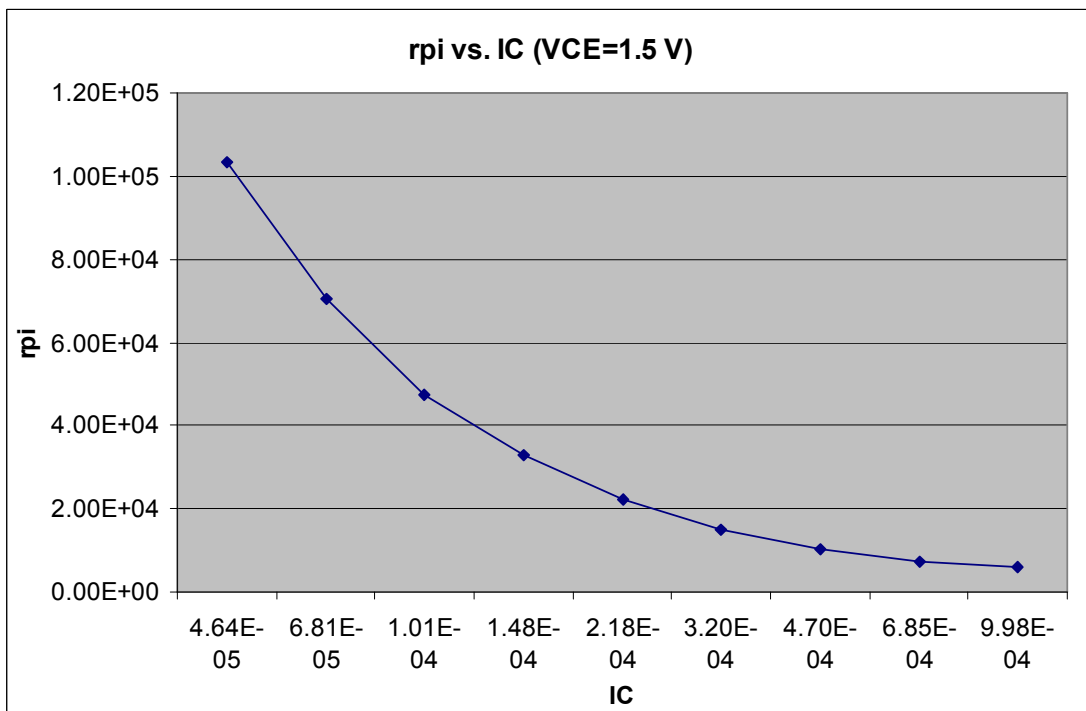r_{π} as a function of I_C for $V_{CE}=1.5V$:




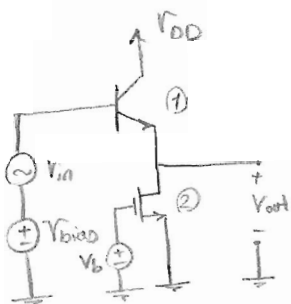

Small Signal circuit:
(from scratch)

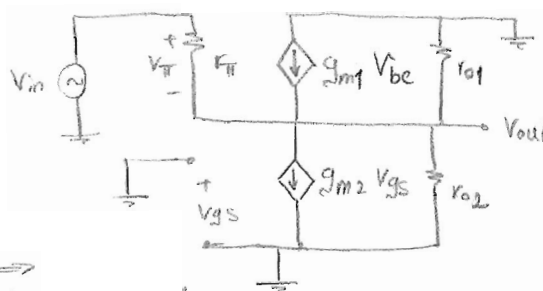

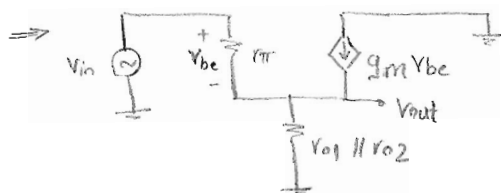$V_s \Rightarrow V_g = 0 \Rightarrow V_{gs} = 0 \Rightarrow$
Only r_{oNMOS} remains in small signal.
($g_m = g_{m1}$)



$V_{be} = V_{in} - V_{out}$

KCL @ V_{out} node:

$$-g_m V_{be} + V_{out} (g_{o1} + g_{o2}) + (V_{out} - V_{in}) g_{\pi} = 0$$


$$V_{out} (g_m + g_{o1} + g_{o2} + g_{\pi}) = V_{in} (g_{\pi} + g_m)$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_{o1} + g_{o2}}$$

$$I_{in} = (V_{in} - V_{out}) g_{\pi} = g_{\pi} V_{in} \left[1 - \frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_{o1} + g_{o2}} \right] = \frac{g_{\pi} (g_{o1} + g_{o2})}{g_m + g_{\pi} + g_{o1} + g_{o2}} V_{in}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{g_m + g_{\pi} + g_{o1} + g_{o2}}{g_{\pi} (g_{o1} + g_{o2})}$$

$$V_{in} = 0 \Rightarrow R_{out} = r_{o1} || r_{o2} || \frac{1}{g_m} || r_{\pi} = \frac{1}{g_m + g_{\pi} + g_{o1} + g_{o2}}$$

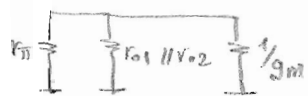

Since usually $\{g_m \gg g_{\pi} \gg g_o\}$, simplifications can be made to A_v, R_{in} & R_{out} specifications:

$$A_v = \frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_{o1} + g_{o2}} \approx \frac{g_m}{g_m + g_{o1} + g_{o2}} = \frac{I_C / V_{th}}{I_C / V_{th} + \frac{I_C}{V_{A1}} + \frac{I_D}{V_{A2}}} = \frac{1}{1 + V_{th} \left(\frac{1}{V_{A1}} + \frac{1}{V_{A2}} \right)}$$

$$R_{in} = \frac{g_m + g_{\pi} + g_{o1} + g_{o2}}{g_{\pi} (g_{o1} + g_{o2})} \approx \frac{g_m + g_{\pi}}{g_{\pi} (g_{o1} + g_{o2})} = \beta (r_{o1} || r_{o2})$$

$$R_{out} = \frac{1}{g_m + g_{\pi} + g_{o1} + g_{o2}} \approx \frac{1}{g_m}$$

Specs: $R_{in} > 5M\Omega$, $R_{out} < 100\Omega$, $A_v > 0.98$, $Swing \pm 1V$

• $R_{out} < 100 \Omega \Rightarrow g_m > 10 \frac{mA}{V} \xrightarrow{\text{Theoretically}} \frac{I_c}{V_{th}} > 0.01 \Rightarrow I_c > 250 \mu A \Rightarrow I_{min} = 250 \mu A$

measurement $I_c = 149 \mu A, g_m = 6 \frac{mA}{V}$
 $I_c = 320 \mu A, g_m = 12.6 \frac{mA}{V} \Rightarrow \checkmark$

• $A_v > 0.98 \Rightarrow \frac{1}{1 + V_{th} \left(\frac{1}{V_{A1}} + \frac{1}{V_{A2}} \right)} > 0.98 \Rightarrow 0.05 > 0.98 \frac{V_{th}}{V_{A_{eff}}} \Rightarrow \frac{\sqrt{A_{eff}}}{V_{th}} > 19.6$
 $\Rightarrow V_{A_{eff}} > 0.49 V \Rightarrow$ This would happen most probably.
 \Rightarrow Voltage gain doesn't impose a hard to meet factor on specs.

• $R_{in} = \beta (r_{o1} \parallel r_{o2})$; plotting $\frac{I_c}{I_B}$ ratio, shows $\beta = 190$ in the current range of interest.
 $= 190 (r_{o1} \parallel r_{o2}) > 5 M\Omega$

$r_{o, BJT}$	$I_{C, max}$
200 k	1 mA
67 k	1.5 mA

$r_{o, MOS}$	$I_{D, max}$
100 k	450 μA
20 k	1.24 mA
14 k	3 mA

$\Rightarrow r_{o1} \parallel r_{o2} > 26.3 k\Omega$
 $\Rightarrow r_{o, MOS}$ is the limiting factor.
 (By creating a trendline on the available data or making finer measurements $\Rightarrow V_{A_{MOS}} = 40$
 $\Rightarrow r_{o2} > 80 k\Omega \Rightarrow I_D < 1.3 mA$
 $r_o = \frac{V_A}{I_D}$
 (This can be different for you, based on your measurements.)

$\Rightarrow I_{max} = 1.3 mA < 1 mA$
 $\Rightarrow I_{max} = 1 mA$

$\Rightarrow \boxed{250 \mu A < I_{sup} < 1 mA}$

• Design: Choose $I_{sup} = 320 \mu A \Rightarrow r_{o1} = 400 k\Omega$; $r_{o2} = 125 k\Omega$
 $V_{BE} = 0.64 \Rightarrow V_{bias} = 1.5 + 0.64 = 2.14 V$
 $V_{GS} = 1.93 \Rightarrow V_D = 1.93$
 $g_m = 12.6 \frac{mA}{V}$
 $r_{\pi} = 15 k\Omega$

$\Rightarrow \left\{ \begin{aligned} A_v &= \frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_{o1} + g_{o2}} = 0.999 > 0.98 \checkmark \quad (\text{As we expected } A_v \text{ is not a tight spec.}) \\ R_{in} &= \beta (r_{o1} \parallel r_{o2}) = 190 (95 k\Omega) = 18.1 M\Omega > 5 M \checkmark \\ R_{out} &= \frac{1}{g_m} = 79.4 \Omega < 100 \Omega \checkmark \end{aligned} \right.$

All specs are met

• Voltage swing: We need $\pm 1 V$ swing around $V_{out, DC} = 1.5 V$.
 (a) $I_{sup} = 320 \mu A$
 (b) $320 \mu A = I_{sup} \Rightarrow$ Should check if specs are met (c) $V_{out} = 0.5 \text{ to } 2.5 V$
 Corresponding to $V_{DS} = 0.5, V_{CE} = 2.5$ and $V_{DS} = 2.5, V_{CE} = 0.5 V$ respectively.

- Lower swing: $V_{out} = 0.5, V_{DS} = 0.5, V_{CE} = 2.5 \Rightarrow r_{o1} = 1 M\Omega$
 $r_{o2} = 38 k\Omega$
 $\checkmark R_{out} (exact) = 78.7$; $A_v = 0.9977 > 0.98 \checkmark$; $7.2^{dB} = R_{in} > 5 M\Omega$

- Upper swing: $V_{out} = 2.5; V_{DS} = 2.5, V_{CE} = 0.5 \Rightarrow r_{o1} = 400 k\Omega$; $r_{o2} = 162 k\Omega \Rightarrow R_{in} = 22 M\Omega > 5 M \checkmark$
 $A_v = 0.999 \checkmark$; $R_{out} = 79 \Omega \checkmark$