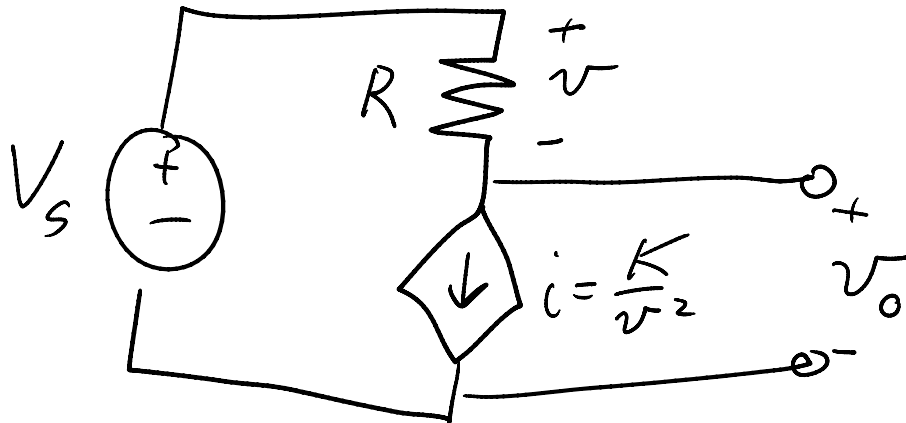


Exercise 1):




$$i(v) = \frac{K}{v^2}$$

$$V_s - v - v_0 = 0$$

$$v = iR = \frac{KR}{v^2} \rightarrow v = \sqrt[3]{KR}$$

$$v_0 = V_s - \sqrt[3]{KR}$$

Exercise 2:

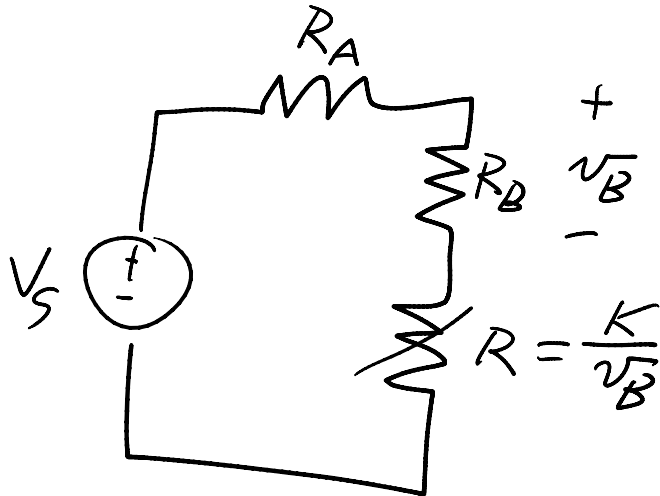


$$i = \frac{V_s}{R_A + R_B + R}$$

$$v_B = i R_B = \frac{V_s R_B}{R_A + R_B + \frac{K}{v_B}}$$

$$v_B = \frac{V_s R_B - K}{R_A + R_B}$$

Exercise 3:

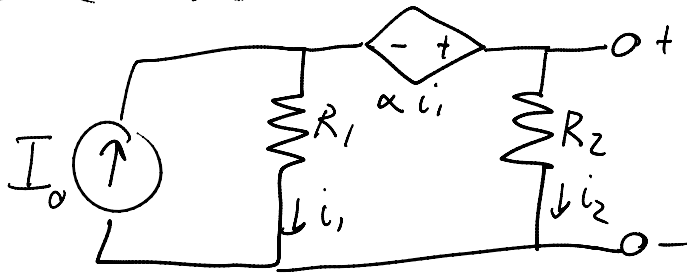

Open Circuit:

$$v_{oc} - \alpha i_1 - R_1 i_1 = 0$$

$$v_{oc} = i_2 R_2 = (I_0 - i_1) R_2$$

$$I_0 R_2 - R_2 i_1 - \alpha i_1 - R_1 i_1 = 0 \rightarrow i_1 = \frac{I_0 R_2}{R_1 + R_2 + \alpha}$$

$$V_{th} = \frac{(\alpha + R_1) R_2 I_0}{R_1 + R_2 + \alpha}$$

R_{th} : Remove **INDEPENDENT** sources, then apply test source.

$$R_{th} = \frac{v_{test}}{i_{test}}$$

$$i_1 R_1 + \alpha i_1 - v_{test} = 0 \rightarrow i_1 = \frac{v_{test}}{R_1 + \alpha}$$

$$v_{test} = i_2 R_2 \rightarrow i_2 = \frac{v_{test}}{R_2}$$

$$i_{test} = i_1 + i_2 = \left(\frac{1}{R_1 + \alpha} + \frac{1}{R_2} \right) v_{test}$$



$$R_{th} = \frac{R_2 (R_1 + \alpha)}{R_1 + R_2 + \alpha}$$

Problem 1:

$$a) i_d = \begin{cases} 0 & v_a < V_T \\ G(v_a - V_T) & v_a > V_T \end{cases}$$

$$v_{out} = V_s - i_d R$$
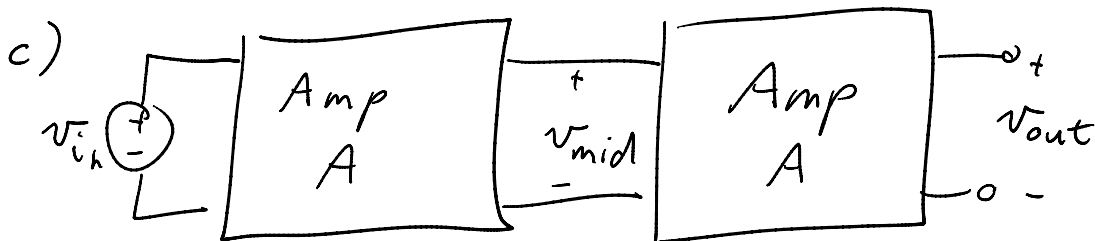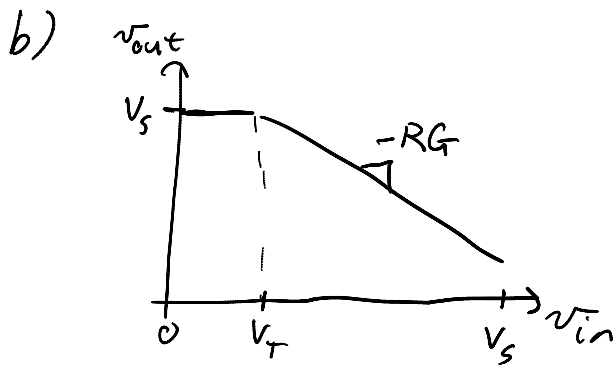
$$v_{out} = \begin{cases} V_s & v_{in} < V_T \\ V_s - R G (v_{in} - V_T) & v_{in} > V_T \end{cases}$$



$$v_{mid} = \begin{cases} V_s & v_{in} < V_T \\ V_s - R G (v_{in} - V_T) & v_{in} > V_T \end{cases}$$

$$v_{out} = \begin{cases} V_s & v_{mid} < V_T \\ V_s - R G (v_{mid} - V_T) & v_{mid} > V_T \end{cases}$$

Problem 1 (cont):

c) $v_{mid} < V_T$: $v_{out} = V_S$

$$V_T = V_S - R_G(v_{in} - V_T)$$


$$v_{in} = V_T + \frac{V_S - V_T}{R_G}$$

$$v_{out} = \begin{cases} V_S - R_G(V_S - V_T) \\ V_S - R_G(V_S - R_G(v_{in} - V_T)) - V_T \\ 0 \end{cases}$$

$$\begin{aligned} v_{in} &< V_T \\ V_T &< v_{in} < V_T + \frac{V_S - V_T}{R_G} \\ V_T + \frac{V_S - V_T}{R_G} &< v_{in} \end{aligned}$$

$$v_{out} = \begin{cases} V_S - R_G(V_S - V_T) \\ (1 - R_G)(V_S + R_G V_T) + (R_G)^2 v_{in} \\ V_S \end{cases}$$
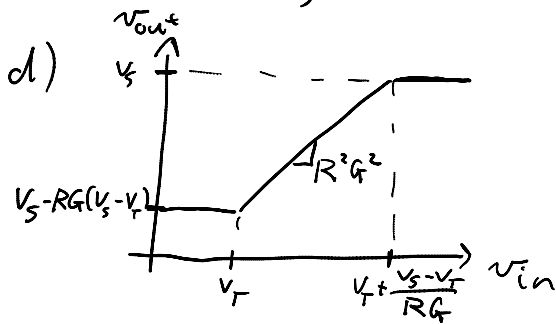
$$\begin{aligned} v_{in} &< V_T \\ V_T &< v_{in} < V_T + \frac{V_S - V_T}{R_G} \\ V_T + \frac{V_S - V_T}{R_G} &< v_{in} \end{aligned}$$



e) $P_{diss} = v_{out} \cdot i_d$

i_d is always in same direction,
 so $P_{diss} > 0$ when $v_{out} > 0$ (sinking power)
 and $P_{diss} < 0$ when $v_{out} < 0$ (sourcing power)

Problem 1 (cont):

f)

single amplifier:

$$v_{out} \geq 0$$

$$v_{out} = 0 = V_s - R_G(v_{in} - V_T) \rightarrow v_{in} = V_T + \frac{V_s}{R_G}$$

$$v_{out} = \begin{cases} V_s - R_G(v_{in} - V_T) & v_{in} < V_T \\ V_s & V_T < v_{in} < V_T + \frac{V_s}{R_G} \\ 0 & V_T + \frac{V_s}{R_G} < v_{in} \end{cases}$$

for $G \rightarrow \infty$: $V_T = V_T + \frac{V_s}{R_G}$

$$v_{out} = \begin{cases} V_s & v_{in} < V_T \\ 0 & v_{in} > V_T \end{cases}$$


* looks like inverter!

chained amplifiers:

$$v_{out} = \begin{cases} 0 & v_{in} < V_T \\ V_s & v_{in} > V_T \end{cases}$$

* looks like logic buffer

Problem 2:

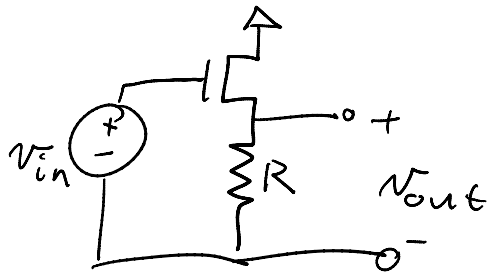

$$a) v_{GS} = v_{in} - v_{out}$$

$$v_{out} = i_d \cdot R = \frac{RK}{2} (v_{in} - V_T - v_{out})^2$$

$$(v_{in} - V_T)^2 - 2v_{out} \left[(v_{in} - V_T) + \frac{2}{RK} \right] + v_{out}^2 = 0$$

$$v_{out} = (v_{in} - V_T) + \frac{2}{RK} \pm \sqrt{\left[(v_{in} - V_T) + \frac{2}{RK} \right]^2 - (v_{in} - V_T)^2}$$

$$= (v_{in} - V_T) + \frac{2}{RK} - \sqrt{\frac{4}{RK} (v_{in} - V_T) + \frac{4}{RK^2}}$$

$$v_{out} = \left[\frac{\sqrt{\frac{2}{RK} + (v_{in} - V_T)} - \sqrt{\frac{2}{RK}}}{2} \right]^2$$

$$b) v_{DS} = V_S - v_{out}$$

$$v_{DS} \geq v_{GS} - V_T$$

$$V_S - v_{out} \geq v_{in} - v_{out} - V_T$$

$$v_{in} \leq V_S + V_T$$

$$v_{GS} \geq V_T$$

$$v_{in} - v_{out} \geq V_T$$


$$v_{in} = V_T, i_d = 0 \rightarrow v_{out} = 0$$

$$v_{in} \geq V_T$$


$$V_T \leq v_{in} < V_S + V_T$$

$$0 \leq v_{out} \leq V_S + \frac{2}{RK} - \sqrt{\frac{4}{RK} \left(V_S + \frac{1}{RK} \right)}$$

Problem 3:

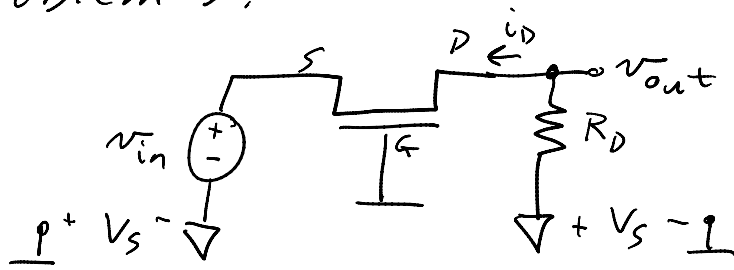

a)

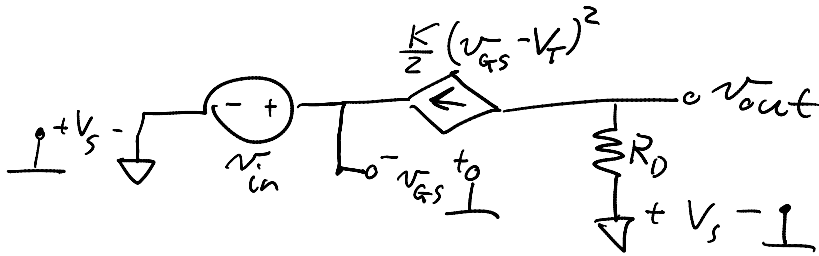

$$b) \quad v_{GS} = 0 - (-V_S + v_{in}) = V_S - v_{in}$$

$$i_D = \frac{K}{2} (V_S - V_T - v_{in})^2$$

$$v_o = V_S - R_D i_D = V_S - \frac{R_D K}{2} (V_S - V_T - v_{in})^2$$

$$c) \quad v_{GS} > V_T: \quad V_S - v_{in} > V_T \rightarrow v_{in} < V_S - V_T$$

$$v_{DS} > v_{GS} - V_T:$$


$$v_{DS} = v_{out} - (-V_S + v_{in}) = V_S + v_{out} - v_{in}$$

$$2V_S - \frac{R_D K}{2} (V_S - V_T - v_{in})^2 - v_{in} > V_S - v_{in} - V_T$$

$$(V_S - V_T - v_{in})^2 < \frac{2(V_S + V_T)}{R_D K} \rightarrow v_{in} > V_S - V_T - \sqrt{\frac{2(V_S + V_T)}{R_D K}}$$

Problem 4:

a)

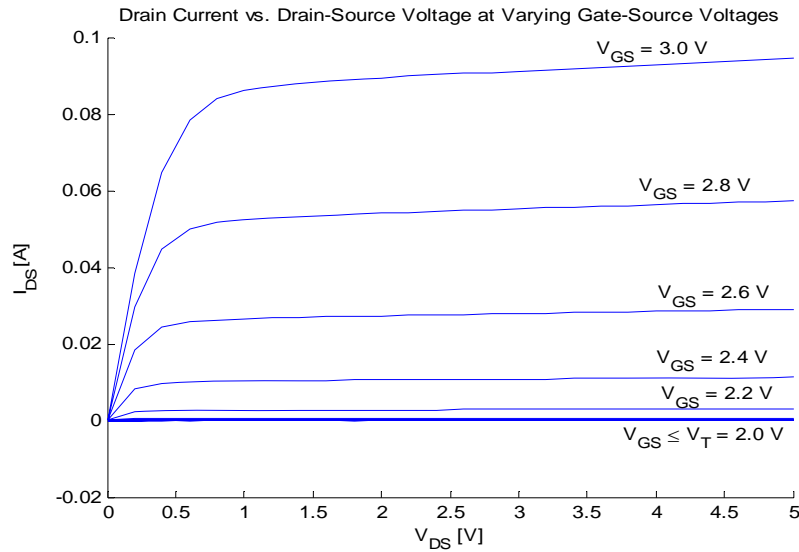

b) $V_T \approx 1.8V$ (note when $I_{DS} \approx 0$ for $V_{DS} > 0$)

K:


$$I_D = \frac{K}{2} (V_{GS} - V_T)^2$$

$$@ V_{GS} = 2.8V, I_D \approx 55mA$$

$$K = 110 mA/V^2$$

Problem 4:

c)

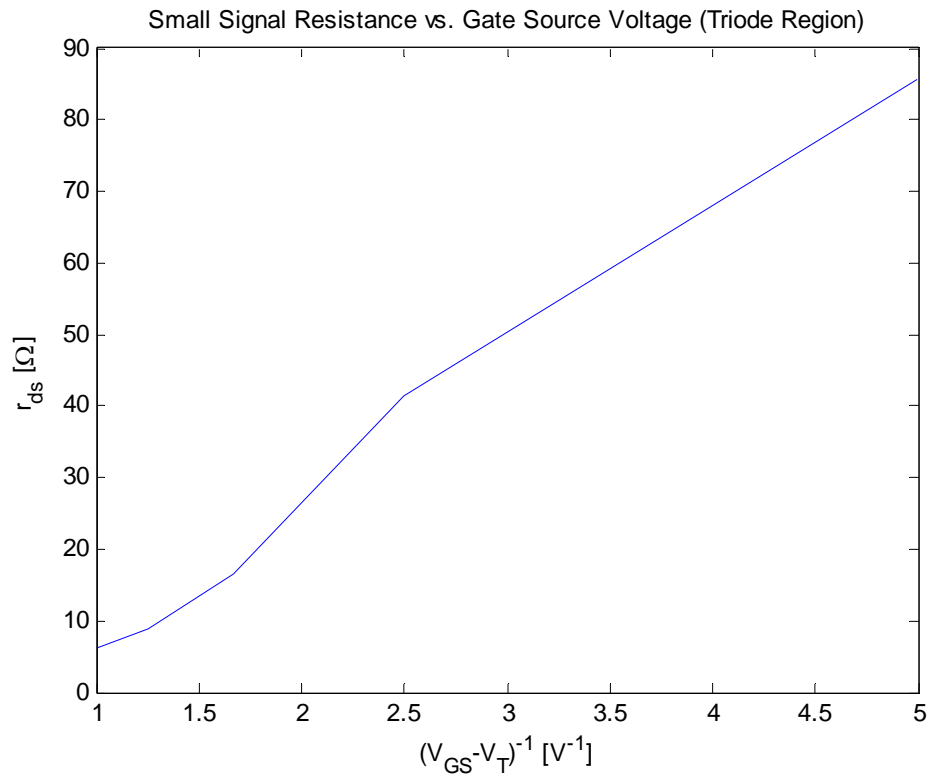

d)

